

Computer arithmetic

Intensive Computation

**Annalisa Massini
2019-2020**

Lecture 16

References


Computer Architecture - A Quantitative Approach

Hennessy Patterson

Appendix J



Half adder and Full adder

 - Adders are usually implemented by combining multiple copies of simple components
- The natural components for addition are **half adders** and **full adders**
- The **half adder** takes two bits a and b as input and produces a sum bit s and a carry bit c_{out} as output
- As logic equations: $s = a\bar{b} + \bar{a}b = a \oplus b$ and $c_{out} = ab$




Half adder and Full adder

- The full adder takes **three bits** a , b and c as input and produces a sum bit s and a carry bit c_{out} as output
- As logic equations: $s = \overline{a}\overline{b}c + \overline{a}b\overline{c} + a\overline{b}\overline{c} + abc = (a \oplus b) \oplus c$ and $c_{out} = (a \oplus b)c + ab$
- The **half adder** is a (2,2) adder:
 - it takes **two inputs** and produces **two outputs**
- The **full adder** is a (3,2) adder:
 - it takes **three inputs** and produces **two outputs**

  


Ripple-Carry Addition

 - The **principal problem** in constructing an adder for n -bit numbers out of smaller pieces is **propagating the carries** from one piece to the next
- The most obvious way to solve this is with a **ripple-carry adder**, consisting of n full adders




Ripple-Carry Addition

 - The **time** a circuit takes to produce an output is **proportional to the maximum number of logic levels** through which a signal travels
- Determining the exact relationship between logic levels and timings is highly technology dependent




Ripple-Carry Addition

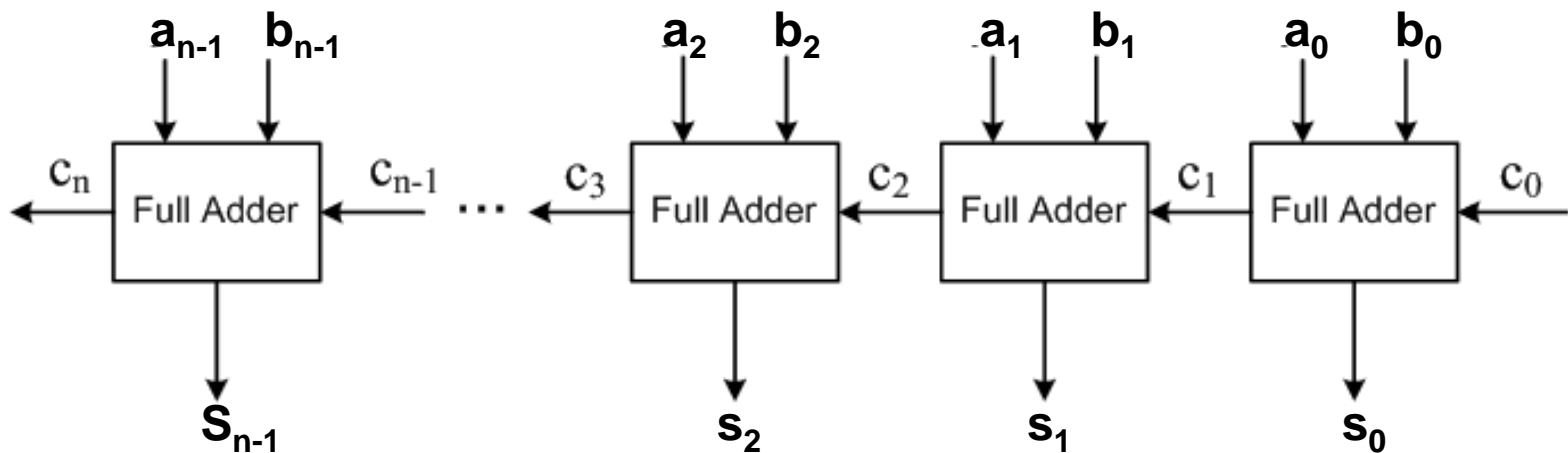- When **comparing adders** we simply **compare the number of logic levels in each one**
- A ripple-carry adder takes:
 - two levels to compute c_1 from a_0 and b_0
 - two more levels to compute c_2 from c_1, a_1, b_1 - *and so on*, up to c_n
- So, there are a total of $2n$ levels




Ripple-Carry Addition

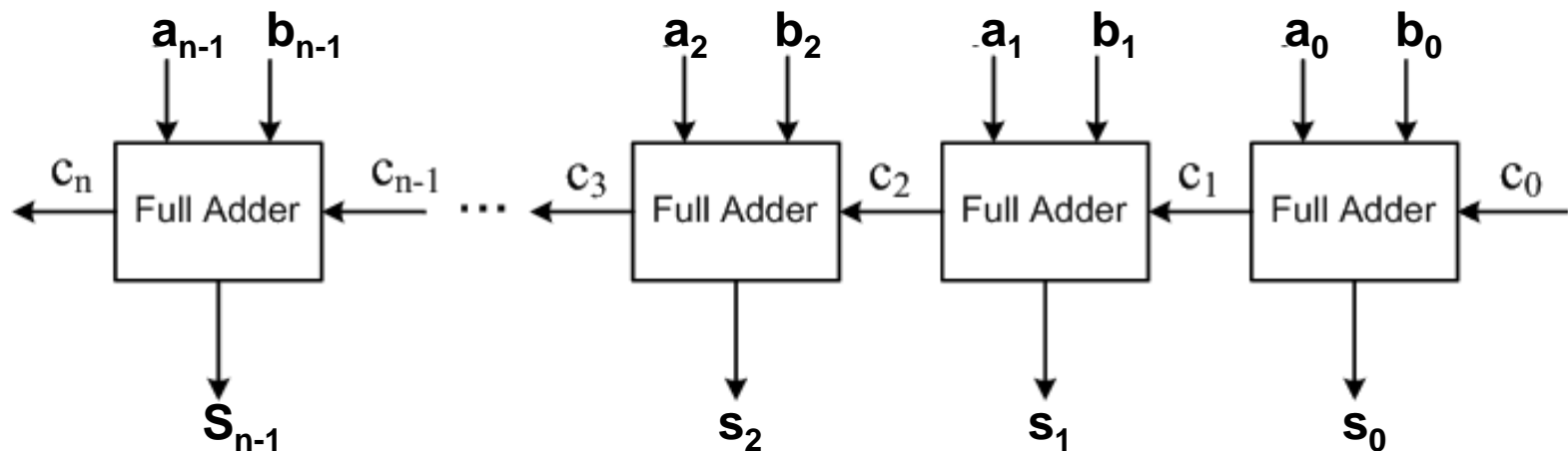- Typical values of n are 32 for integer arithmetic and 53 for double-precision floating point
- The ripple-carry adder is the slowest adder, but also the cheapest
- It can be built with only n simple cells, connected in a simple, regular way



Ripple-Carry Addition

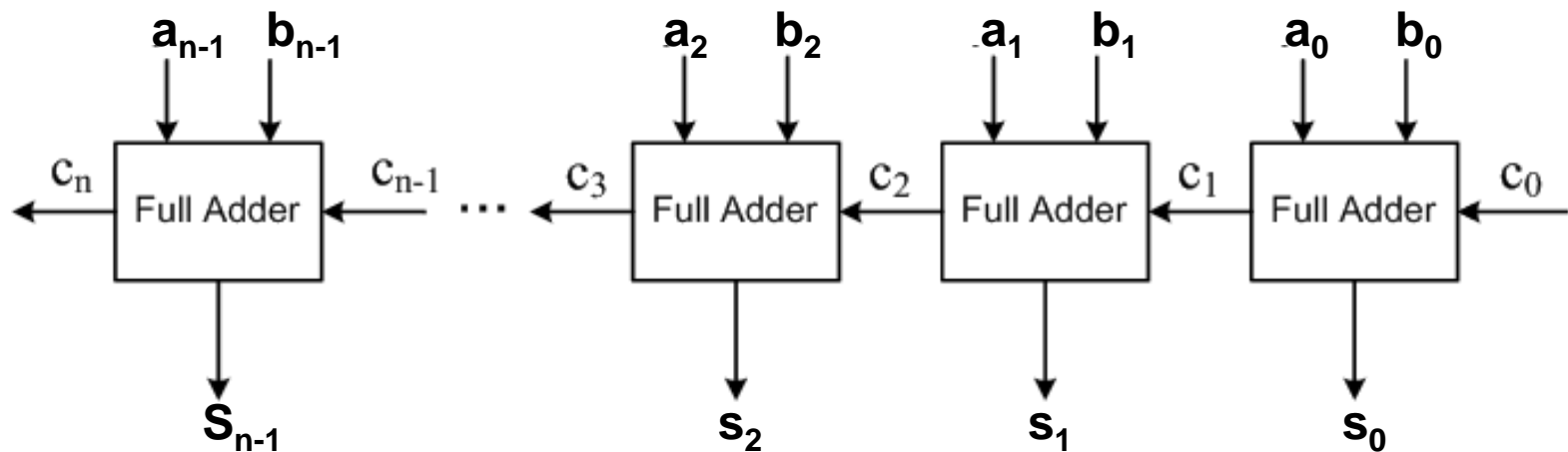
- The ripple-carry adder is relatively slow \rightarrow it takes time $O(n)$
- But it is used because in technologies like CMOS, the constant factor is very small
- Short ripple adders are often used as building blocks in larger adders



Ripple-Carry Addition for Signed Numbers


- The most widely used system for representing integers is the two's complement, where the MSB is considered associated with a negative weight
- The value of a two's complement number $a_{n-1}a_{n-2} \cdots a_1a_0$ is:
 
$$-a_{n-1}2^{n-1} + a_{n-2}2^{n-2} + \cdots + a_12^1 + a_02^0$$




Ripple-Carry Addition for Signed Numbers

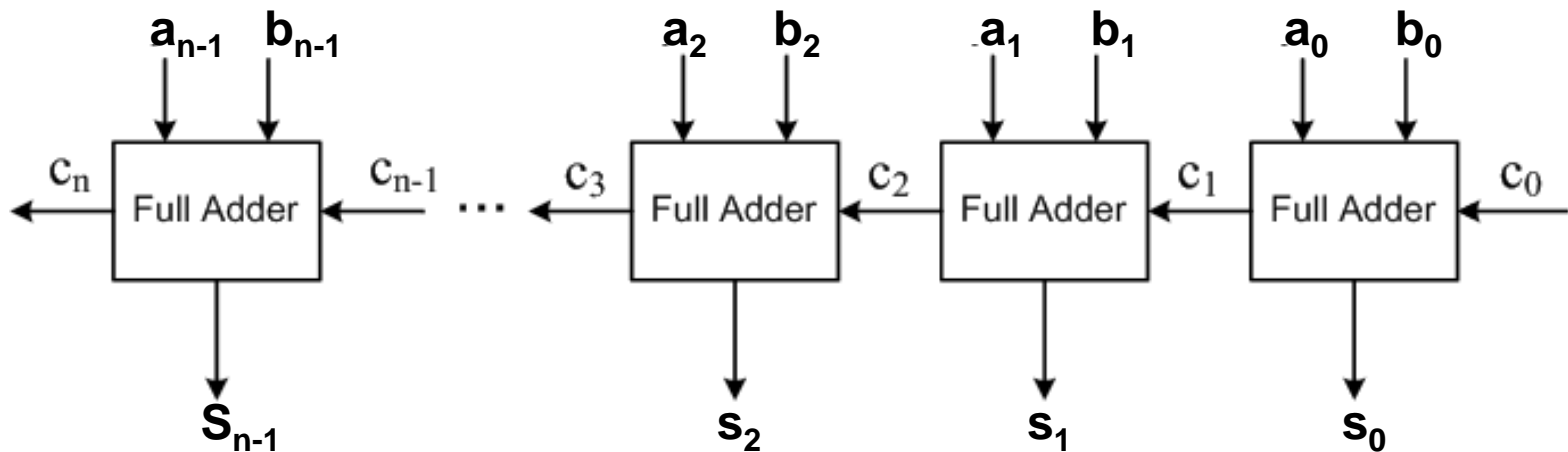- The reasons for the popularity of two's complement are:
 - It makes signed addition easy \rightarrow simply discard the carry-out from the high order bit
 - Subtraction is executed as an addition:
 - $A-B = A+(-B)$, recalling that $-X = \bar{X} + 1$




Ripple-Carry Addition for Signed Numbers

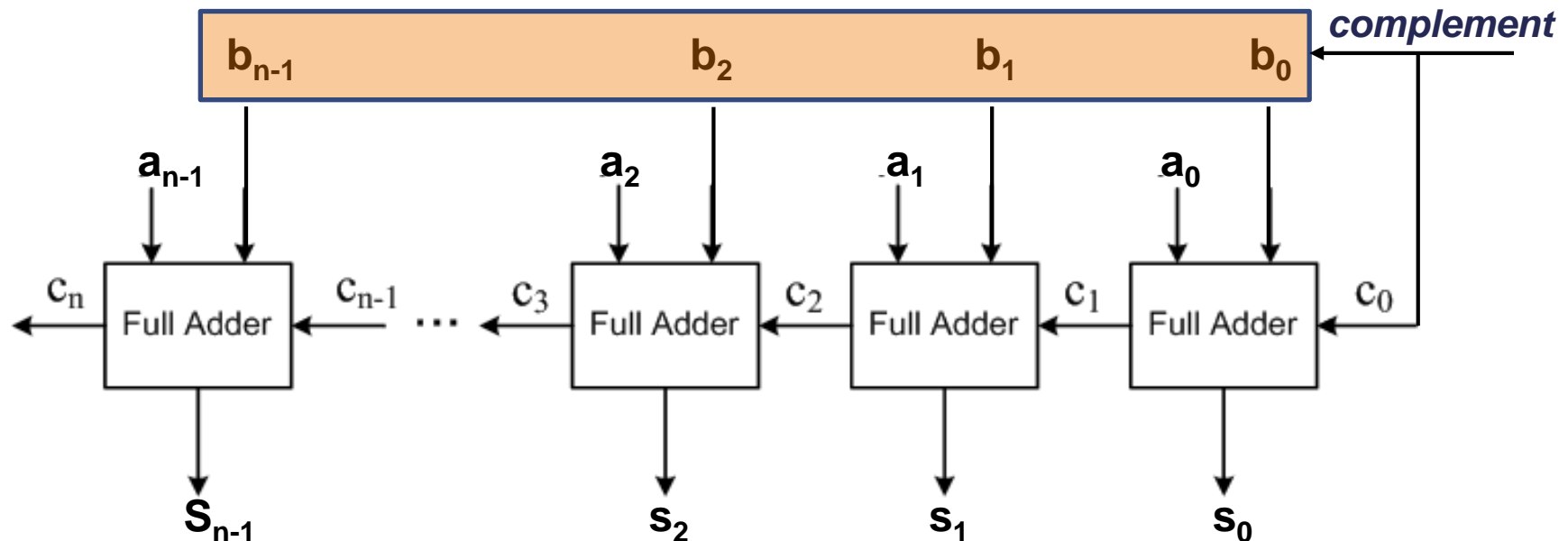- The Ripple-Carry adder is used for subtraction acting on second operand B and on C_0
- If line **complement** is 1 then operand B is complemented bit wise and $C_0=1$




Unsigned Multiplication

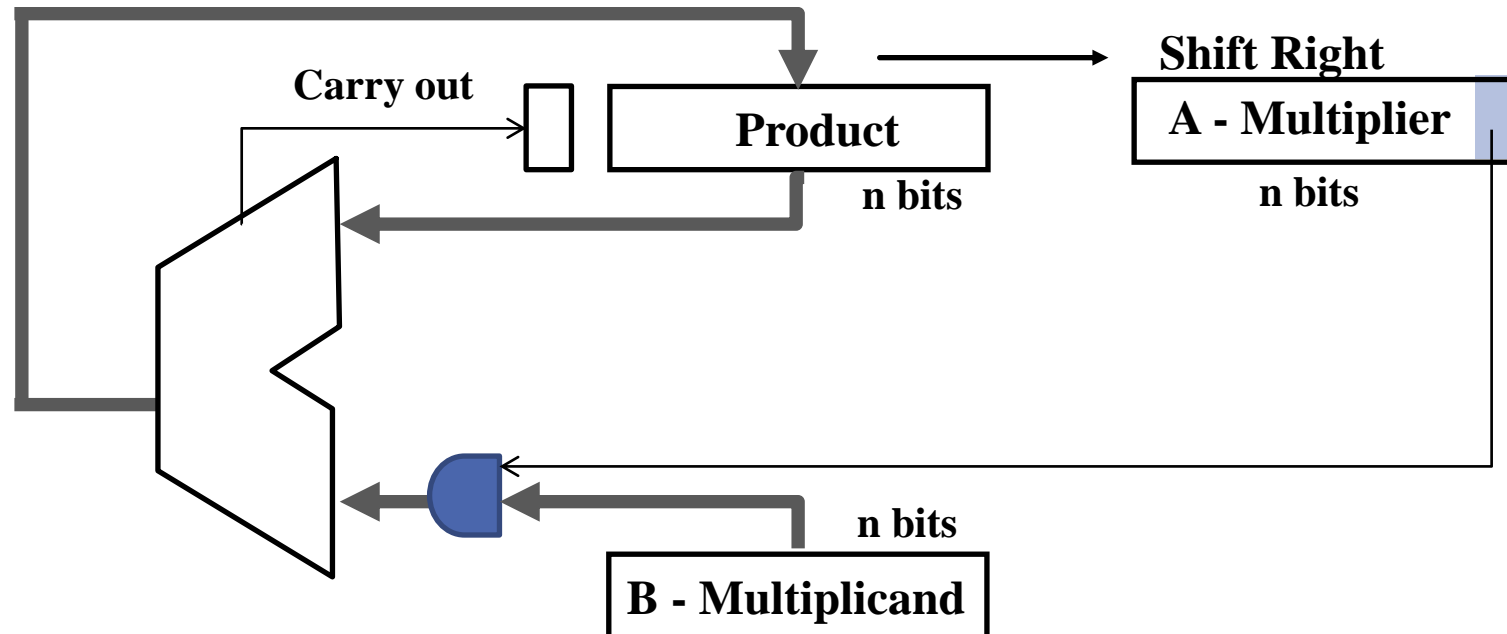- The simplest multiplier computes the product of two unsigned numbers, $a_{n-1}a_{n-2} \cdots a_0$ and $b_{n-1}b_{n-2} \cdots b_0$, one bit at a time
- Register ***Product*** is initially 0



Unsigned Multiplication

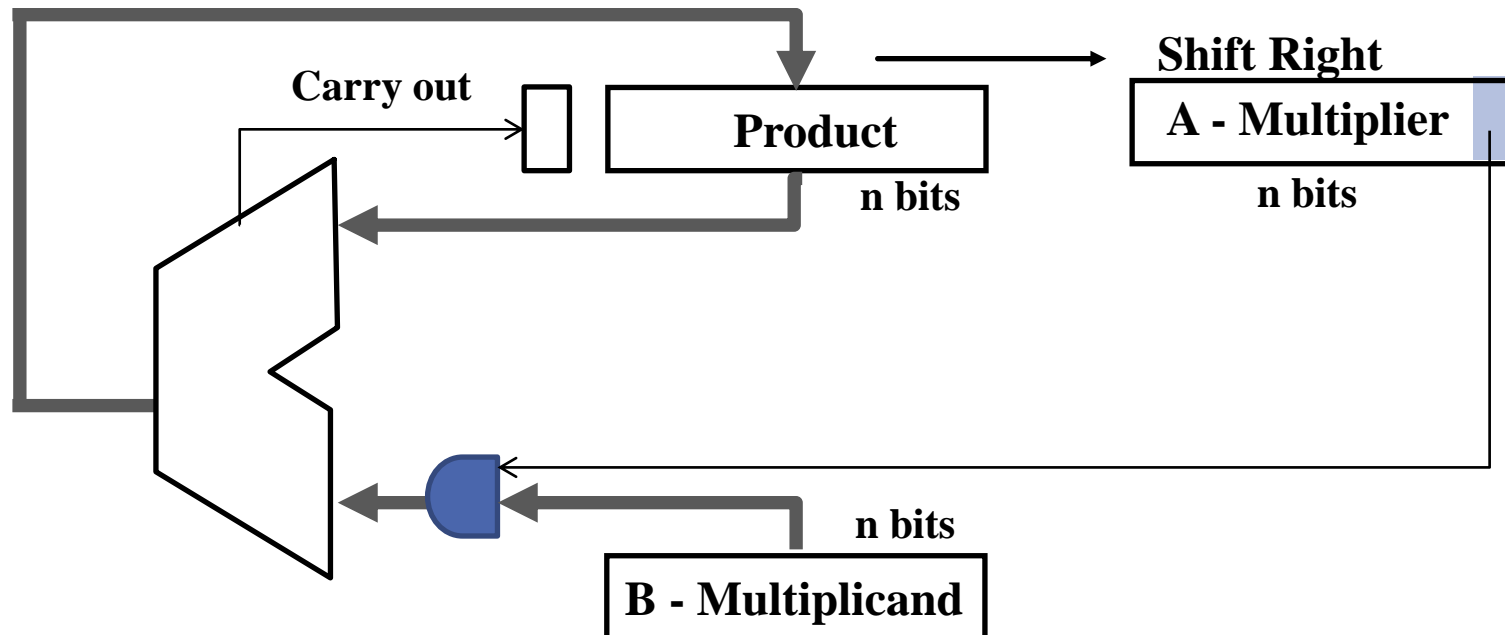
- Each multiply step has two parts:
 - (i) Partial product and accumulation:
 - If the least-significant bit of A is 1, then $b_{n-1}b_{n-2} \cdots b_0$, (in register B) is added to P;
 - else $0 \cdots 00$ is added to P.
 - The sum is placed back into P



Unsigned Multiplication

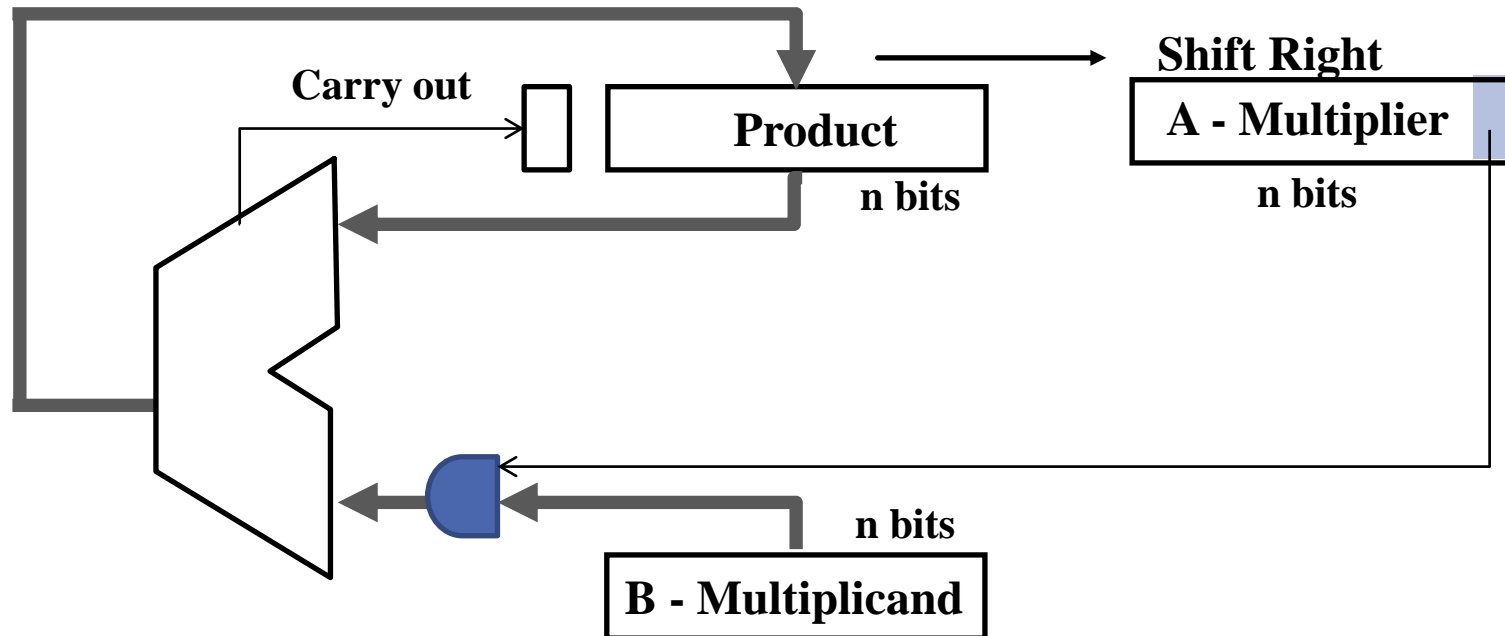
(ii) Registers P and A are shifted right:

- the carry-out of the sum is moved into the high-order bit of P
- the low-order bit of P is moved into register A,
- the rightmost bit of A (not used any more) is shifted out




Unsigned Multiplication

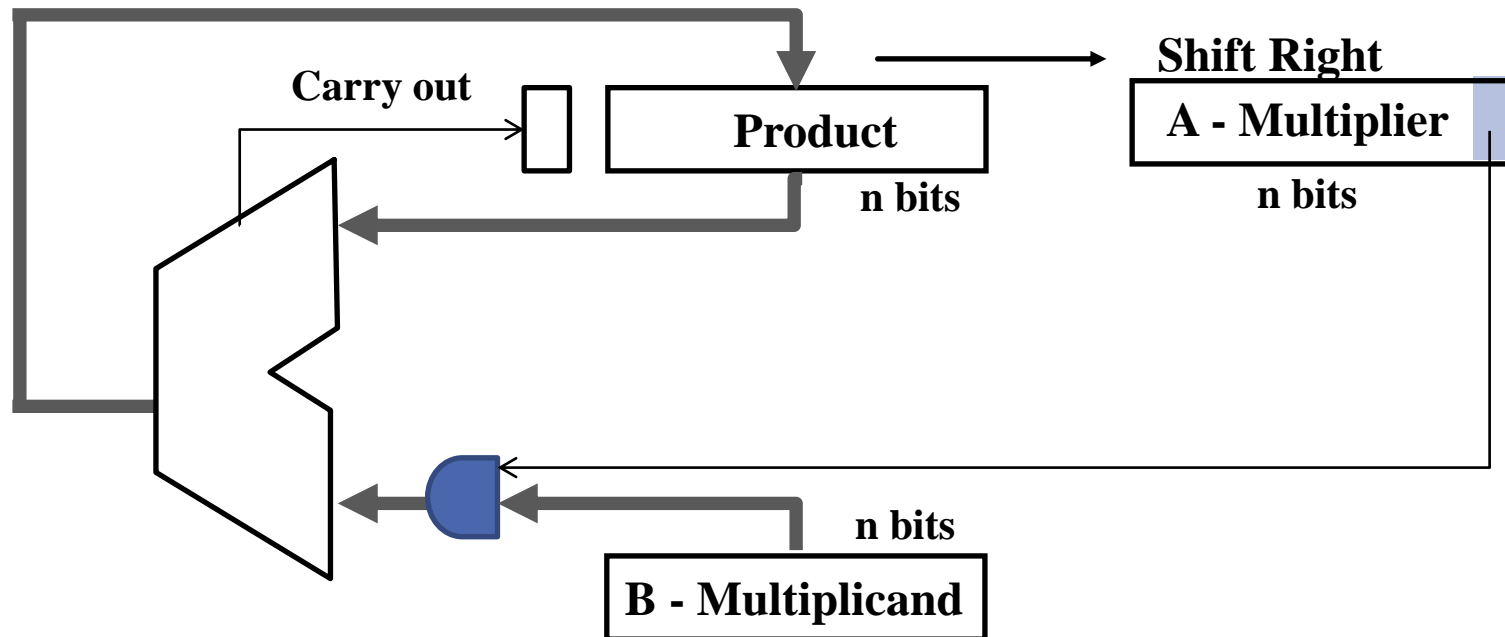- Hence, we add the contents of P to either B or 0 (depending on the low-order bit of A), replace P with the sum, and then shift both P and A one bit right
- After ***n* steps**, the product appears in registers P and A, with A holding the lower-order bits




Signed Multiplication

 - To multiply two's complement numbers, the obvious approach is to convert operands to be nonnegative, do an unsigned multiplication, and then (if the original operands were of opposite signs) negate the result
- This requires **extra time and hardware**




Signed Multiplication

 - A better approach to multiply A and B using the hardware below:
 - If B is potentially negative but A is nonnegative, to convert the unsigned multiplication algorithm into a two's complement one we need that when P is shifted, it is **shifted arithmetically**



Signed Multiplication

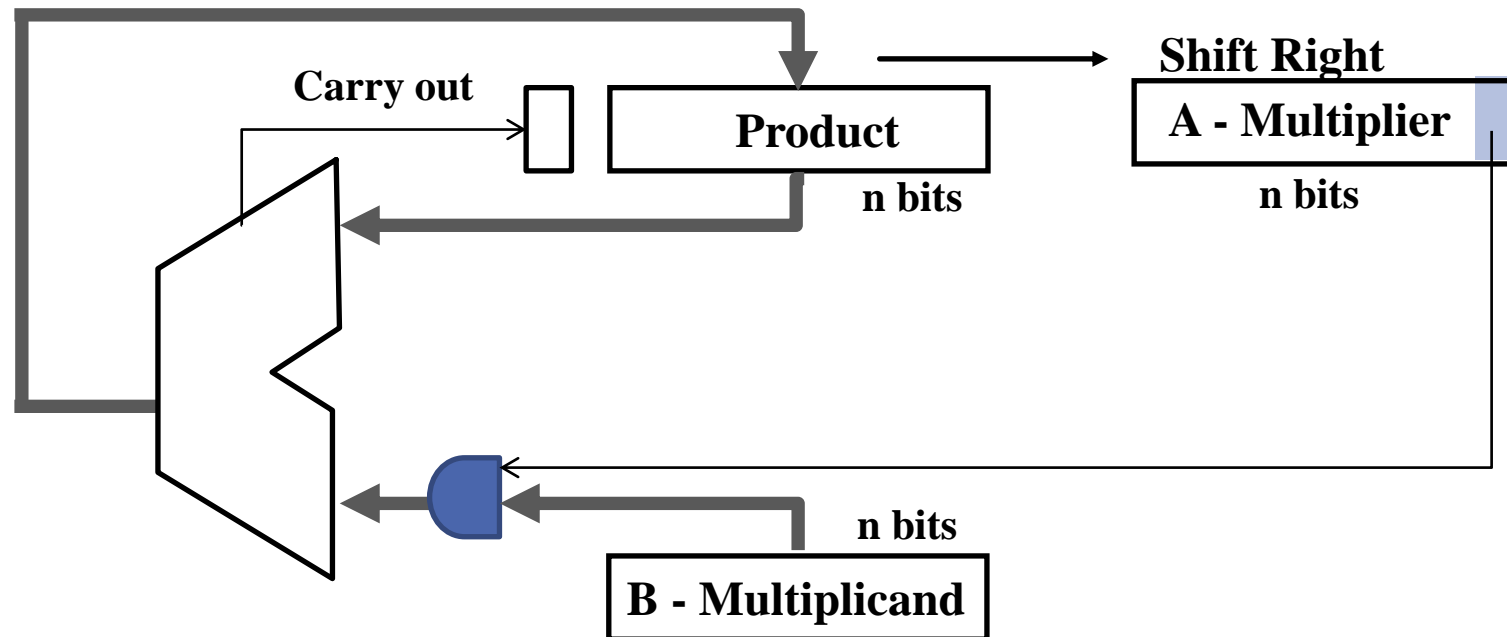- A better approach to multiply A and B using the hardware below:
 - If A is negative, the method is *Booth recoding* that is based on the fact that **any sequence of 1s in a binary number can be written as $011\dots11 = 100\dots00 - 1$**




Signed Multiplication

- Then, we *replace a string of 1s in multiplier* with an initial *subtract* when we first see a one and then later *add for the bit after the last one*

	0010	
x	0110	
<hr/>		
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
<hr/>		
	00001100	

Signed Multiplication

 - Then, we *replace a string of 1s in multiplier* with an initial *subtract* when we first see a one and then later *add for the bit after the last one*



	0010	
x	0110	
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	00001100	

	0010	
x	0110	
<hr/>		
+	0000	shift (0 in multiplier)
-	0010	sub(first 1 in multpl)
+	0000	shift(mid string of 1s)
+	0010	add(prior step had last 1)
<hr/>		
	00001100	

Signed Multiplication

- Hence, to deal with **negative values of A**, all that is required is to sometimes subtract B from P, instead of adding either B or 0 to P
- Rules: If the initial content of A is $a_{n-1} \cdot \cdot \cdot a_0$, then step (i) in the multiplication algorithm becomes:
 - If $a_i = 0$ and $a_{i-1} = 0$, then add 0 to P
 - If $a_i = 0$ and $a_{i-1} = 1$, then add B to P
 - If $a_i = 1$ and $a_{i-1} = 0$, then subtract B from P
 - If $a_i = 1$ and $a_{i-1} = 1$, then add 0 to P
 - For the first step, when $i = 0$, take a_{i-1} to be 0

Speeding Up Integer Multiplication

- ▶ Integer addition is the simplest operation and the most important
- ▶ Even for programs that don't do explicit arithmetic, addition must be performed to increment the program counter and to calculate addresses
- ▶ The delay of an N-bit ripple-carry adder is:

$$t_{\text{ripple}} = Nt_{FA}$$

where t_{FA} is the delay of a full adder

- ▶ There are different techniques to increase the speed of integer operations (that lead to faster floating point), as the Carry Look-ahead Adder (CLA)

Speeding Up Integer Multiplication


- Methods that increase the speed of multiplication can be divided into two classes:
 - single adder
 - multiple adders
- In the simple multiplier we described, each multiplication step passes through the single adder
- The amount of computation in each step depends on the used adder
- If the space for many adders is available, then multiplication speed can be improved

Pipelined arithmetic

- Consider the instruction pipelining:
 - The processor goes through a repetitive cycle of fetching and processing instructions
 - In the absence of hazards, the processor is continuously fetching instructions from sequential locations → the pipeline is kept full and a savings in time is achieved
- Similarly, a **pipelined ALU** will save time if it is fed **a stream of data** from sequential locations
- A single, isolated operation is not speeded up by pipeline
- The speedup is achieved when a vector of operands is presented to the units in the ALU


Pipelined Addition

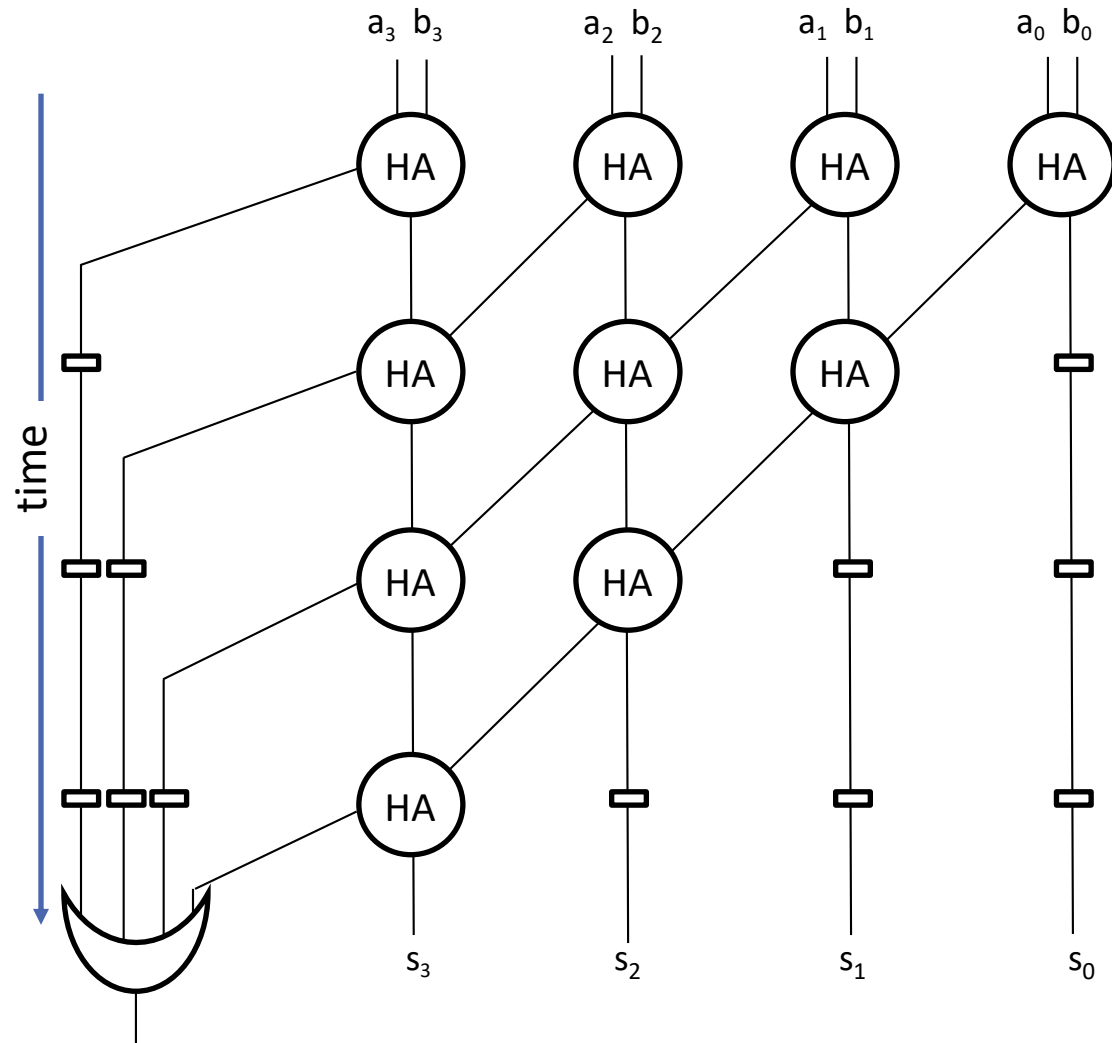- For n bits operands, a **pipeline adder** consists of n stages of half adders
- Registers (FF D) are inserted at each stage to synchronize the computation
- At each clock cycle a new pair of operands is applied to the inputs of the adder




Pipelined Addition

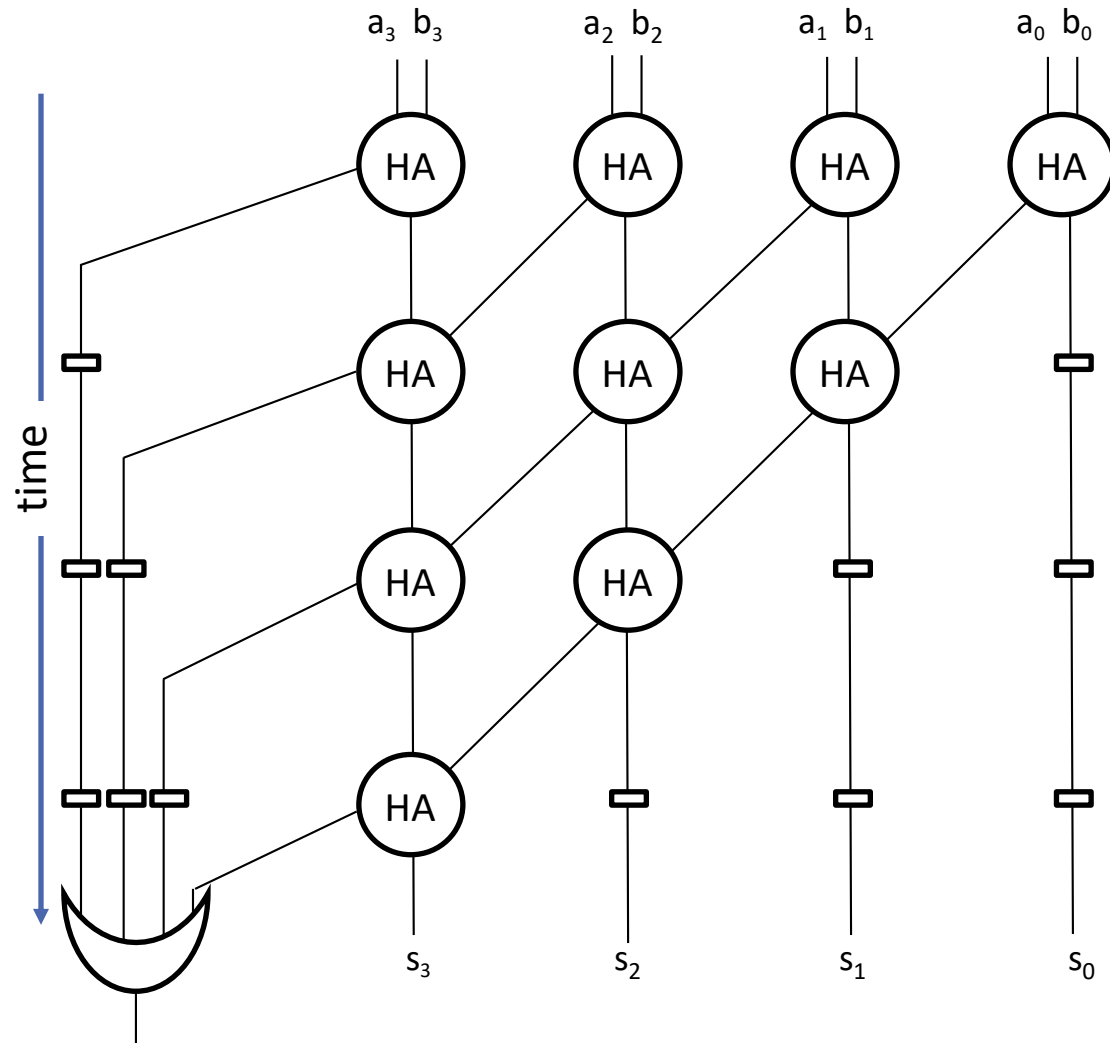- After n clock cycles, the sum of the first pair of operands is obtained
- The computing time for a single sum is the same of the carry-ripple adder
- A new sum is obtained at each clock cycle starting from the $(n+1)$ -th clock cycle




Pipelined Addition

 
- The number of **HA** is $O(n^2)$, whereas the circuit complexity of the carry-ripple adder is $O(n)$
- The added circuit complexity pays off if long sequences of numbers are being added



Pipelined Unsigned Multiplication

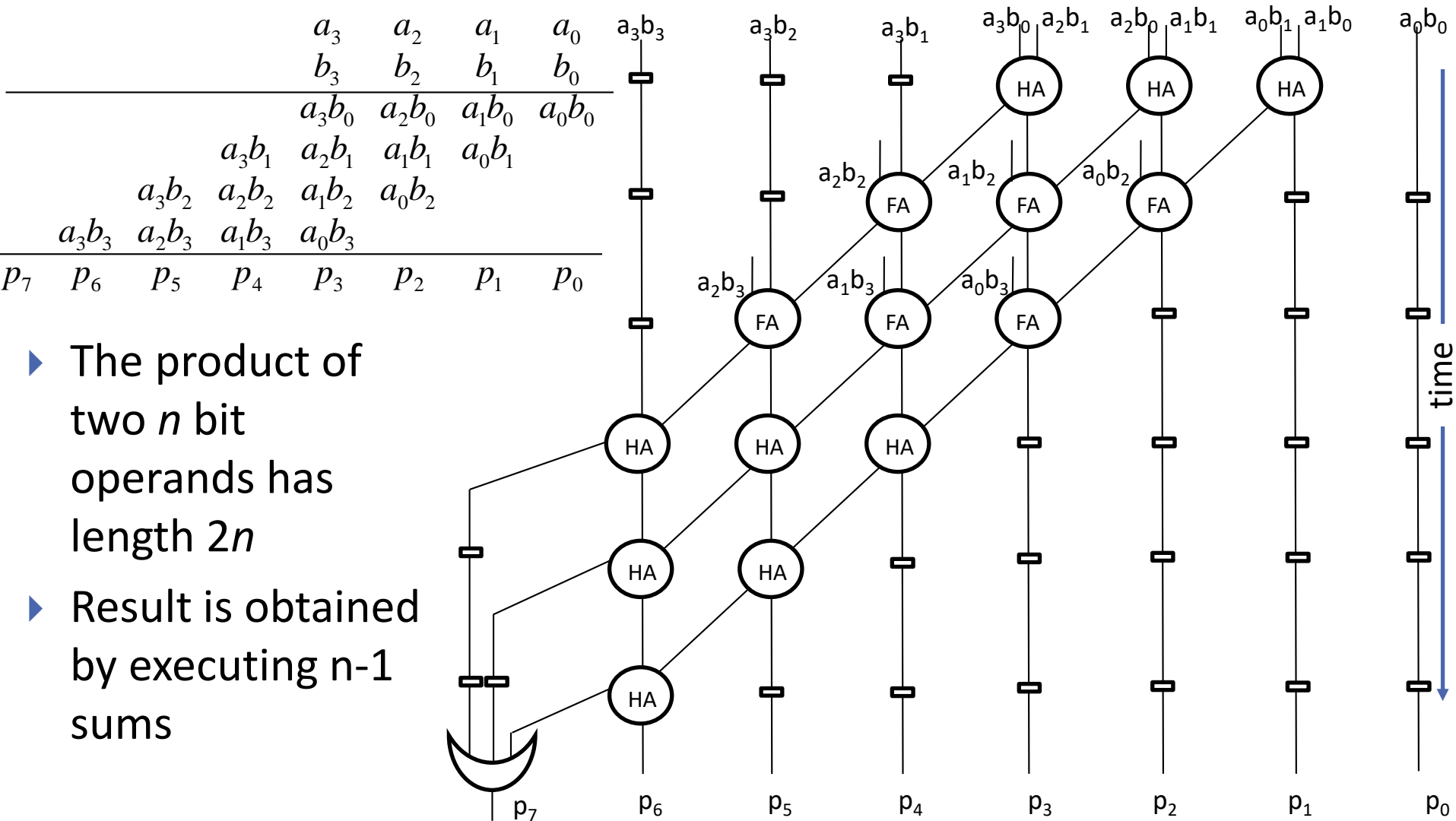


Pipelined Unsigned Multiplication

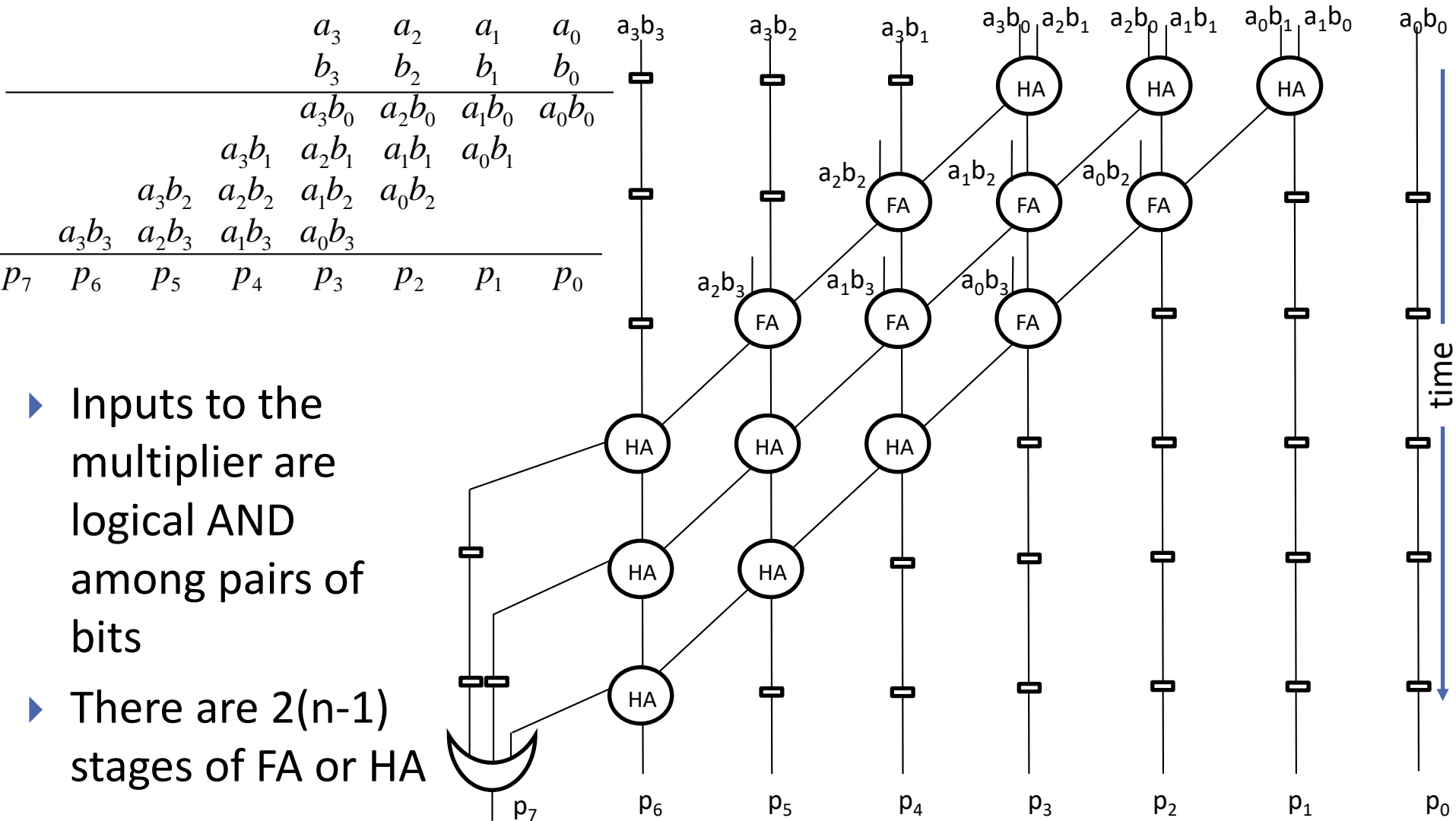


Pipelined Unsigned Multiplication

 - ▶ After stage $(n-1)$ all bit products (AND) are added
- ▶ Last $(n-1)$ stages represent a pipelined adder
- ▶ Bit p_{2n-1} of the result is obtained as OR among the carries generated by the most left HA of each stage




Pipelined Unsigned Multiplication

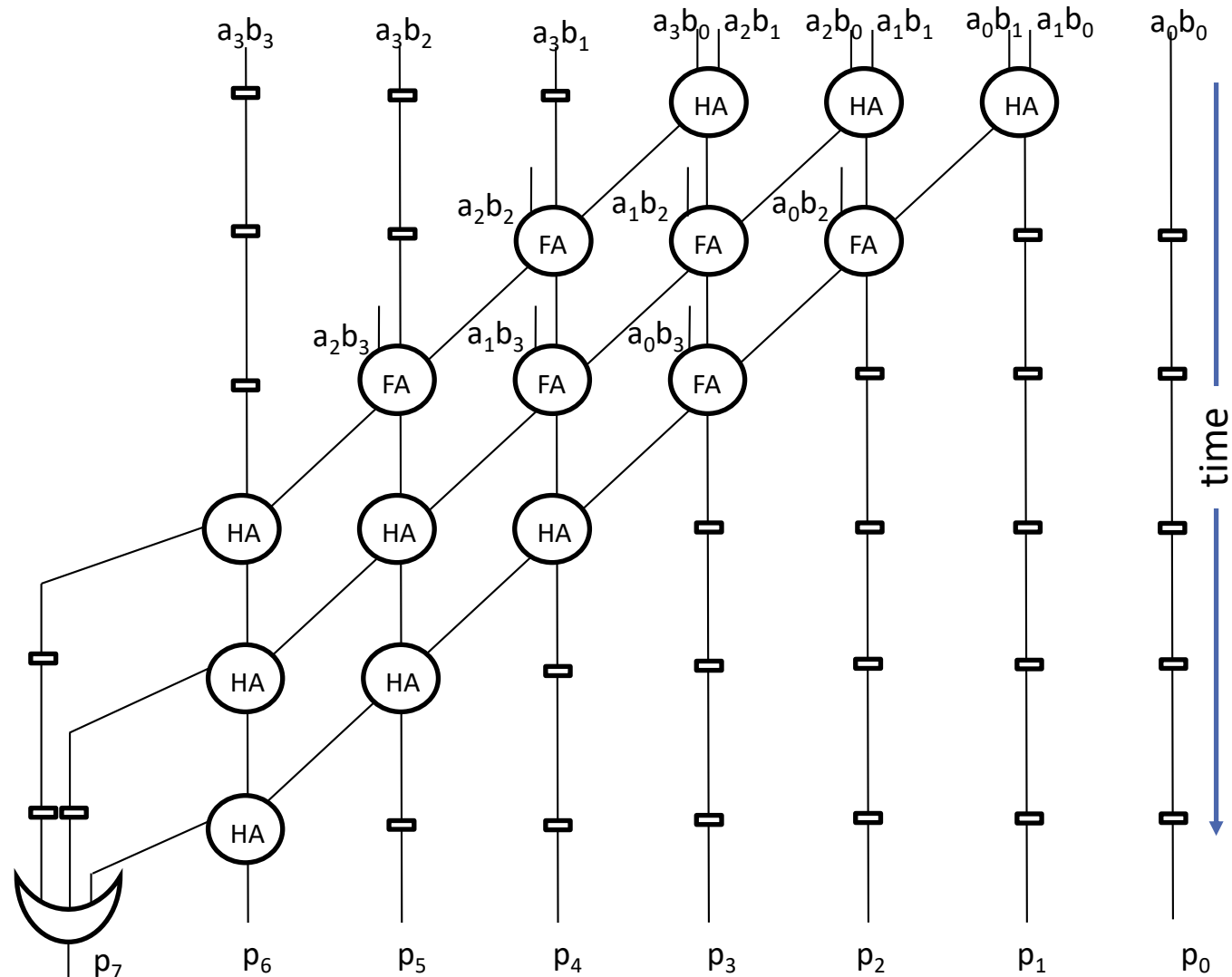- ▶ After $2(n-1)$ clock cycles, the product of the first pair of operands is obtained
- ▶ A new result is obtained at each clock cycle starting from the **$(2n-1)$ -th** clock cycle




Pipelined Signed Multiplication

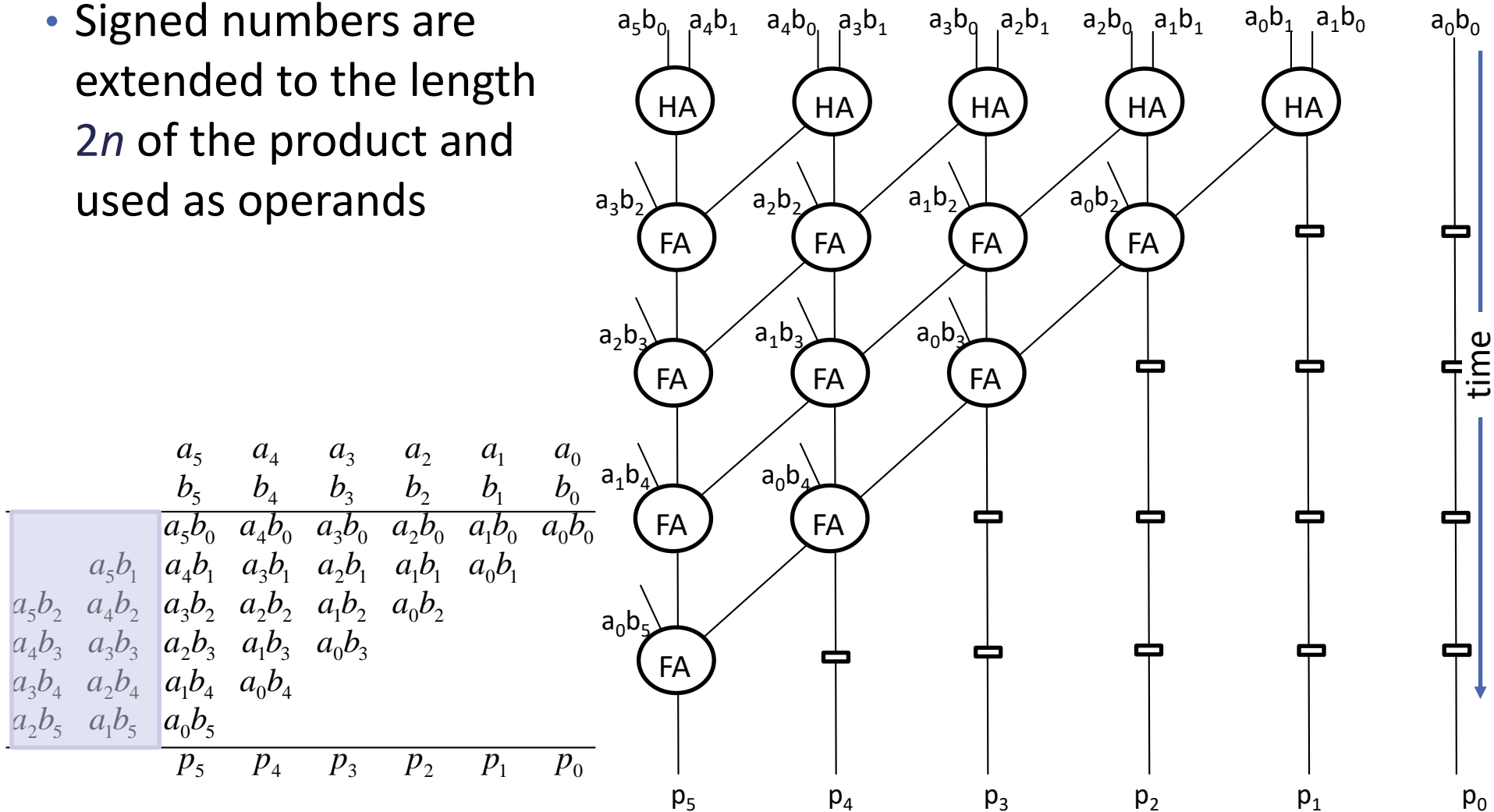- Signed numbers are extended to the length $2n$ of the product and used as operands



Pipelined Signed Multiplication

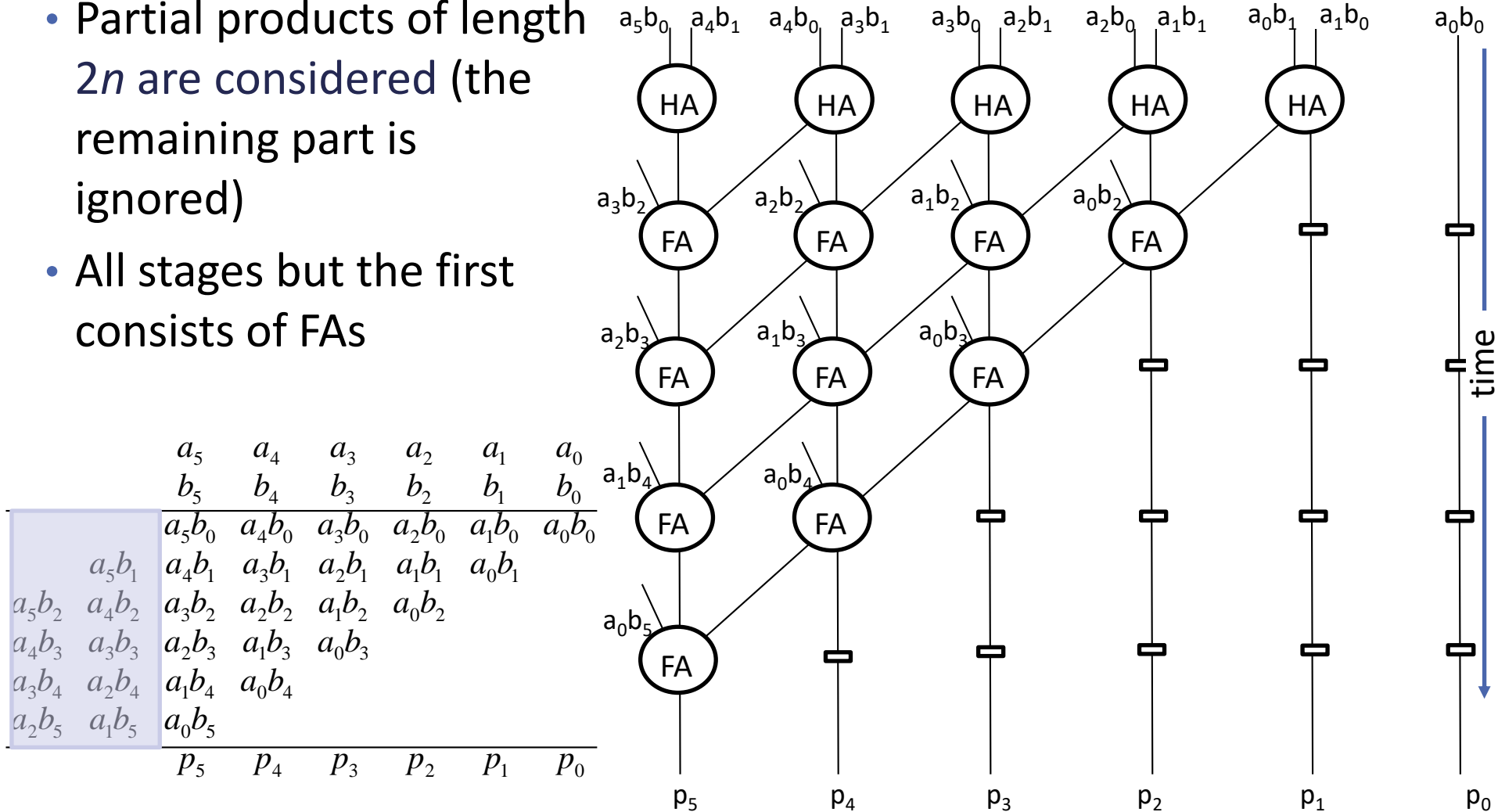- Partial products of length $2n$ are considered (the remaining part is ignored)
- All stages but the first consists of FAs



CIRCUIT AREA AND TIME EVALUATION

Circuit area and time

- To discuss about the time and area, it is useful the analytical model (unit-gate model) presented in
 - A. Tyagi, *A reduced-area scheme for carry-select adders*, IEEE Trans. Comput., 1993
- They use a simplistic model for **gate-count** and **gate-delay**:
 - Each gate except **EX-OR** counts as **one elementary gate**
 - An **EX-OR gate** is counted as **two elementary gates**, because in static (restoring) CMOS, an **EX-OR** gate is implemented as two elementary gates (**NAND**)
 - The **delay** through **an elementary gate** is counted as **one gate-delay unit**, but an **EX-OR gate** is two **gate-delay units**

Circuit area and time


- In this model we are **ignoring the *fanin* and *fanout*** of a gate
- This can lead to unfair comparisons for circuits containing gates with a large difference in *fanin* or *fanout*
 - For instance, gates in the CLA adder have different *fanin*
 - A carry-ripple adder has no gates with *fanin* and *fanout* greater than 2
- The best comparison for a VLSI implementation is actual area and time
- The gate-count and gate-delay comparisons may not always be consistent with the area-time comparisons

Circuit area and time

- To simplify we consider:
 - **Any gate** (but the EX-OR) counts as **one gate** for both area and delay $\rightarrow A_{\text{gate}}$ and T_{gate}
 - An **exclusive-OR gate** counts as **two elementary gates** for both area and delay $\rightarrow A_{\text{EX-OR}} = 2A_{\text{gate}}$ and $T_{\text{EX-OR}} = 2T_{\text{gate}}$
 - An **m -input gate** counts as **$m - 1$ gates** for area and **$\log_2 m$ gates** for delay $\rightarrow A_{m\text{-gate}} = (m-1)A_{\text{gate}}$ and $T_{m\text{-gate}} = \log_2 m T_{\text{gate}}$



Circuit area and time

 - A half adder (HA) has:
 - delay 2 unit gates – $T_{HA} = 2 T_{gate}$
 - area 3 unit gates – $A_{HA} = 3 A_{gate}$





Circuit area and time

  - A **half adder** (HA) has:
 - delay 2 unit gates – $T_{HA} = 2 T_{gate}$
 - area 3 unit gates – $A_{HA} = 3 A_{gate}$
- A **full adder** (FA) has:
 - delay 4 unit gates – $T_{FA} = 4 T_{gate}$
 - area 7 unit gates – $A_{FA} = 7 A_{gate}$



Circuit area and time

  - A **half adder** (HA) has:
 - delay 2 unit gates – $T_{HA} = 2 T_{gate}$
 - area 3 unit gates – $A_{HA} = 3 A_{gate}$
- A **full adder** (FA) has:
 - delay 4 unit gates – $T_{FA} = 4 T_{gate} = 2 T_{HA}$
 - area 7 unit gates – $A_{FA} = 7 A_{gate} = 2 A_{HA} + A_{gate}$



Circuit area and time

- A carry-ripple adder for n-bits operands has:

- delay $T_{\text{CR-adder}} \rightarrow T_{\text{CR-adder}} = n T_{\text{FA}} = 2n T_{\text{HA}} = 4n T_{\text{gate}}$

- area $A_{\text{CR-adder}} \rightarrow A_{\text{CR-adder}} = n A_{\text{FA}} = 2n A_{\text{HA}} + n A_{\text{gate}} = 7n A_{\text{gate}}$

