

ADVANCED ARCHITECTURE

INTENSIVE COMPUTATION

COMPUTER ARITHMETIC

Annalisa Massini

2023-2024

Lecture 3-4

References

Computer Architecture - A Quantitative Approach


Hennessy Patterson – *Fifth Edition*

Appendix J – *Computer arithmetic* - David Goldberg

ADDITION AND ADDERS

Half adder and Full adder

 - Adders are usually implemented by combining multiple copies of simple components
- The natural components for addition are **half adders** and **full adders**
- The **half adder** takes two bits a and b as input and produces a sum bit s and a carry bit c_{out} as output
- Logic equations: $s = a\bar{b} + \bar{a}b = a \oplus b$ and $c_{out} = ab$





Half adder and Full adder

- The full adder takes **three bits** a , b and c as input and produces a sum bit s and a carry bit c_{out} as output

- Logic equations:




$$s = \overline{a}\overline{b}c + \overline{a}b\overline{c} + a\overline{b}\overline{c} + abc = (a \oplus b) \oplus c$$
  
$$\text{and } c_{out} = (a \oplus b)c + ab$$




Half adder and Full adder

   - The **half adder** is a (2,2) adder:
 - it takes **two inputs** and produces **two outputs**
- The **full adder** is a (3,2) adder:
 - it takes **three inputs** and produces **two outputs**




Ripple-Carry Addition

 - The **principal problem** in constructing an adder for n -bit numbers out of smaller pieces is **propagating the carries** from one module to the next
- The most obvious way to solve this is with a **ripple-carry adder**, consisting of n full adders




Ripple-Carry Addition

 - Note that the low-order carry-in could be wired to 0, hence the **low-order adder** could be a half adder
- However, setting the low-order carry-in bit to 1 is useful for performing **subtraction**




Ripple-Carry Addition

 - The **time** a circuit takes to produce an output is **proportional to the maximum number of logic levels** through which a signal travels
- Determining the exact relationship between logic levels and timings is highly technology dependent




Ripple-Carry Addition

 - When **comparing adders** we simply **compare the number of logic levels in each one**
- A ripple-carry adder takes:
 - two levels to compute c_1 from a_0 and b_0
 - two more levels to compute c_2 from c_1, a_1, b_1 - *and so on*, up to c_n
- So, there are a total of $2n$ levels




Ripple-Carry Addition

 - Typical values of n are **32 for integer arithmetic** and **53 for double-precision floating point**
- The ripple-carry adder is the slowest adder, but also the cheapest
- It can be built with only n simple cells, connected in a simple, regular way



Ripple-Carry Addition

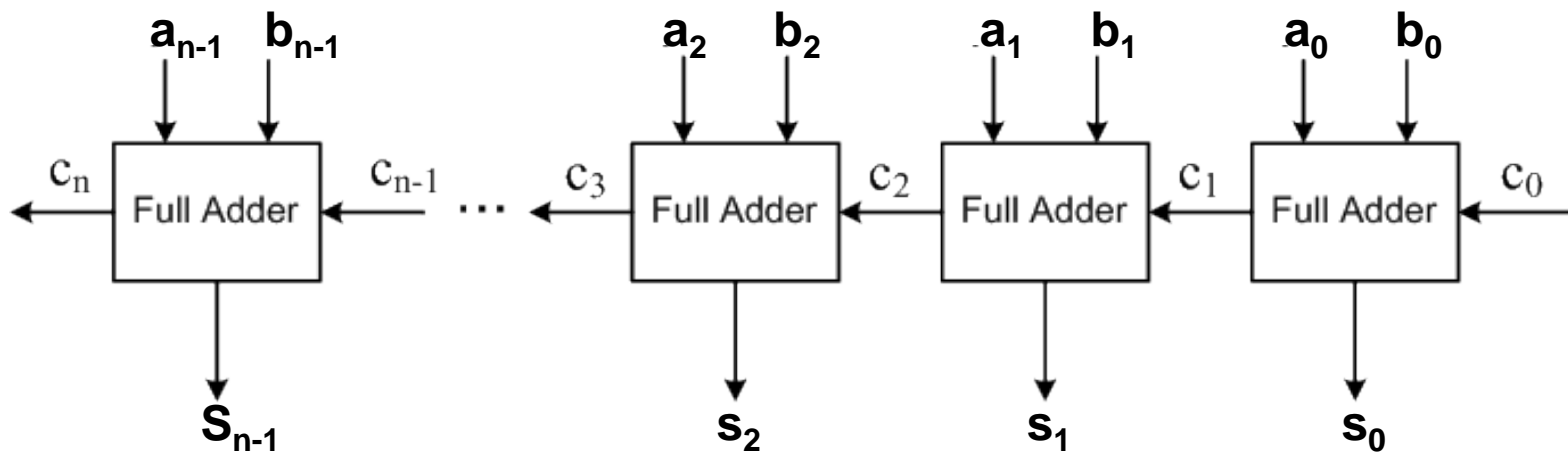
- The ripple-carry adder is relatively slow \rightarrow it takes time $O(n)$
- But it is used because in technologies like CMOS, the constant factor is very small
- **Short ripple adders** are often used as **building blocks** in larger adders



Ripple-Carry Addition for Signed Numbers


- The most widely used system for representing integers is the **two's complement**, where the **MSB** is considered associated with a **negative weight**
- The value of a two's complement number $a_{n-1}a_{n-2} \cdots a_1a_0$ is:
 
$$-a_{n-1}2^{n-1} + a_{n-2}2^{n-2} + \cdots + a_12^1 + a_02^0$$




Ripple-Carry Addition for Signed Numbers

 - The reasons for the popularity of two's complement are:
 - It makes **signed addition easy** → simply discard the carry-out from the high order bit
 - **Subtraction is executed as an addition:**
 - $A - B = A + (-B)$, recalling that $-X = \bar{X} + 1$



Ripple-Carry Addition for Signed Numbers

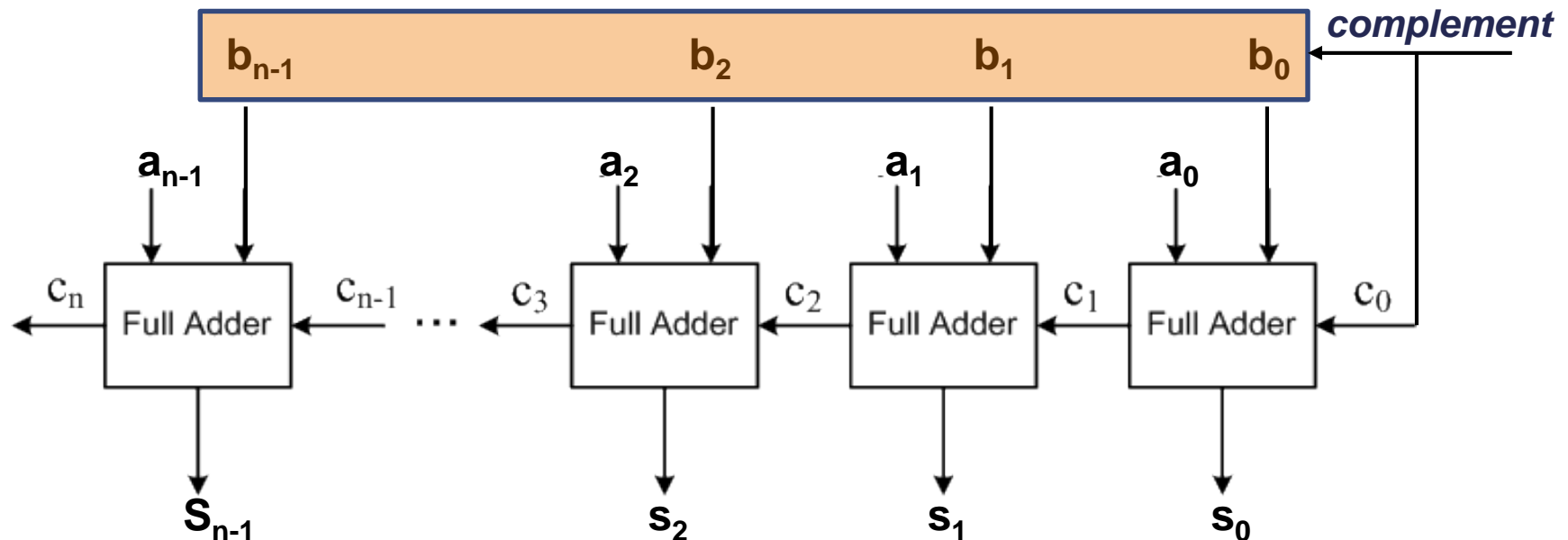
- The Ripple-Carry adder is used for subtraction acting on second operand B and on c_0
- If line **complement** is 1 then operand B is complemented bit wise and $c_0=1$



MULTIPLICATION AND MULTIPLIERS


Unsigned Multiplication

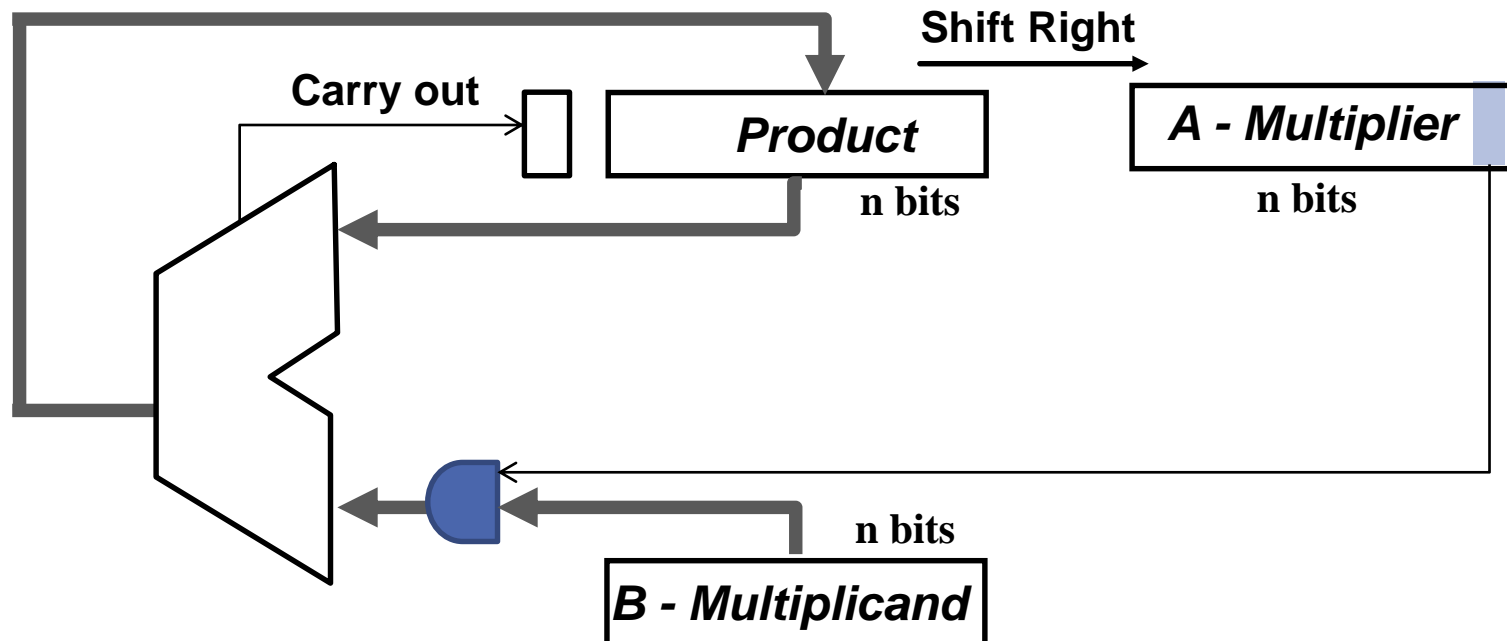- The **simplest multiplier** computes the product of two unsigned numbers, $a_{n-1}a_{n-2} \cdots a_0$ and $b_{n-1}b_{n-2} \cdots b_0$ one bit at a time
- Register **Product** is initially 0



Unsigned Multiplication

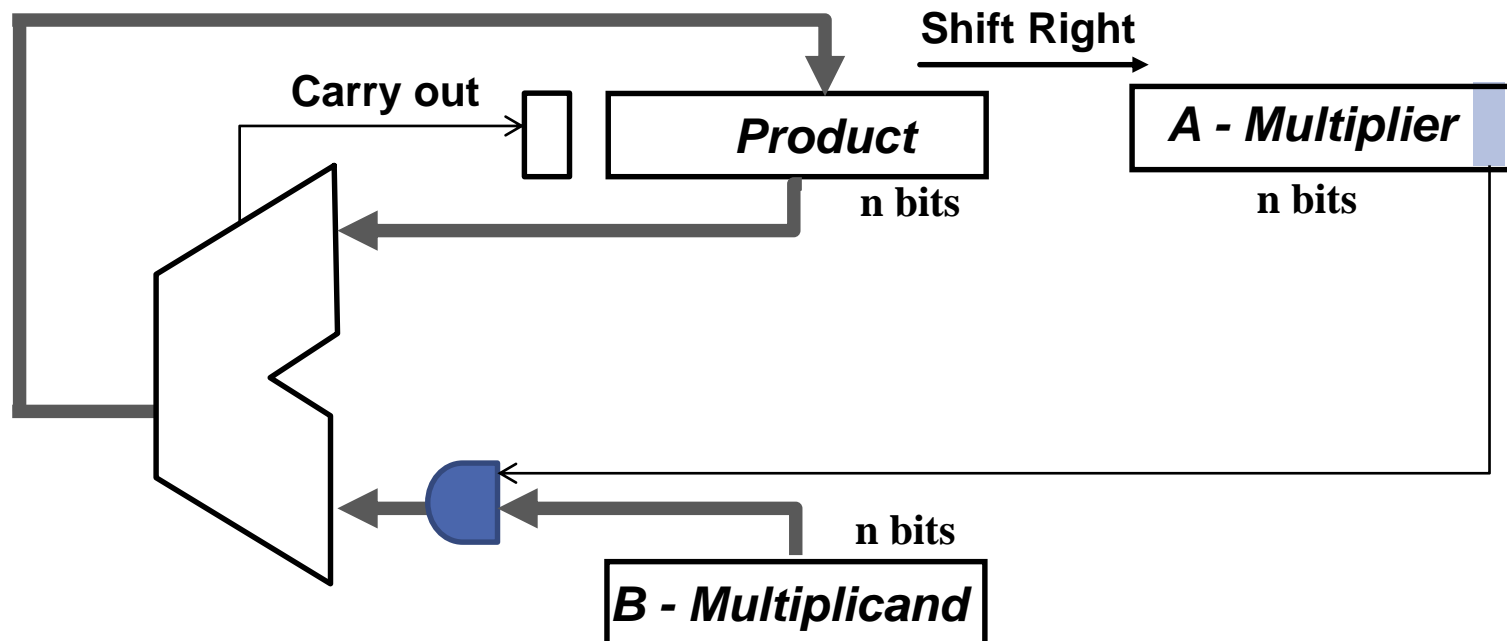
- Each multiply step has two parts:
 - (i) Partial product and accumulation:
 - If the lsb of A is 1, *then* register B ($b_{n-1}b_{n-2} \cdots b_0$) is added to P; *else* $0 \cdots 00$ is added to P
 - The **sum** is placed back **into P**



Unsigned Multiplication

 
(ii) Registers **P** and **A** are **shifted right**:

- the **carry-out** of the sum is moved into the **high-order bit** of **P**
- the **low-order bit** of **P** is moved into **register A**,
- the **rightmost bit** of **A** (not used any more) is **shifted out**




Unsigned Multiplication

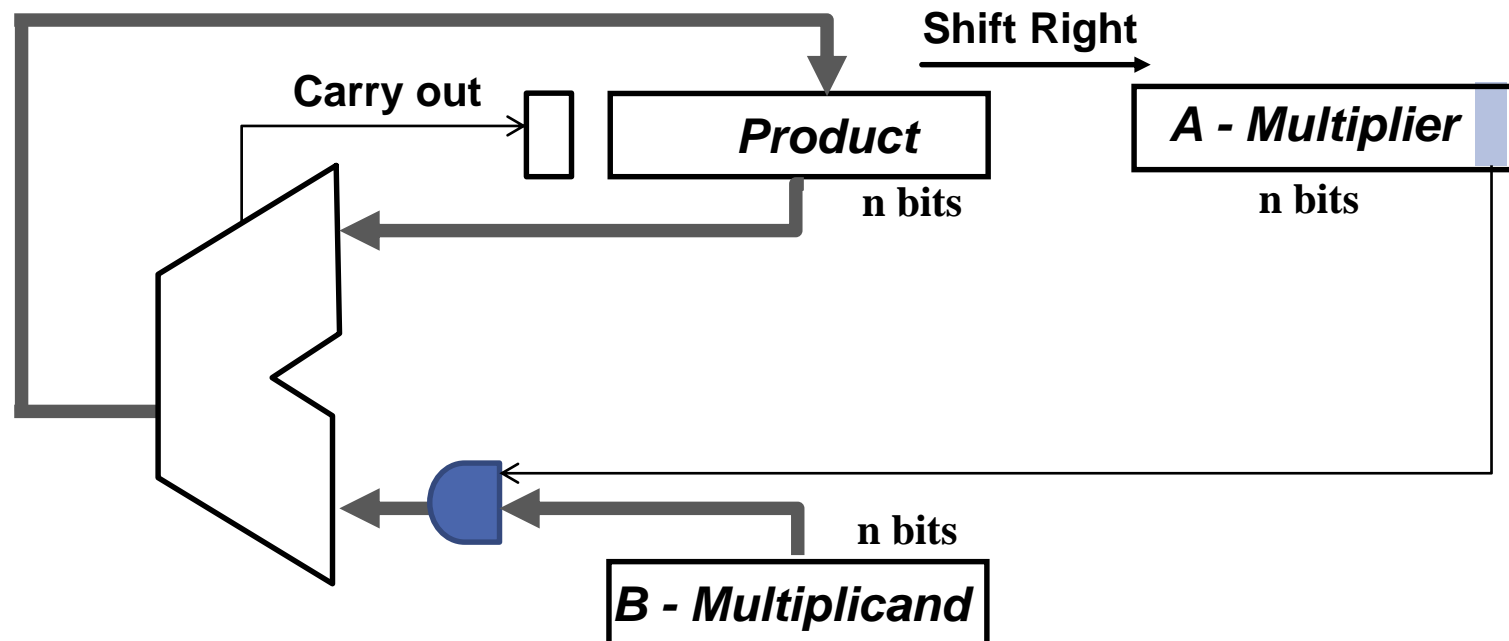- In summary, each multiplication step consists of: **adding** the contents of P to **either B or 0** (depending on the low-order bit of A), **replace** P with the sum, then **shift both P and A** one bit right
- After ***n* steps**, the product appears in registers P and A, with A holding the lower-order bits




Signed Multiplication

 - To multiply two's complement numbers, the **obvious approach** is to convert operands to be nonnegative, do an unsigned multiplication, and then (if the original operands were of opposite signs) negate the result
- This requires **extra time** and **hardware**



Signed Multiplication

 - A better approach to multiply A and B using the hardware below:
 - If A is nonnegative and B is potentially negative, to convert the unsigned multiplication algorithm into a two's complement one we need that when P is shifted, it is shifted arithmetically
 - Our adder will now be adding n -bit two's complement numbers between -2^{n-1} and $2^{n-1} - 1$



Signed Multiplication

- If **A is negative**, the method of *Booth recoding* is used
- It is based on the fact that **any sequence of 1s** in a **binary number** can be written as: **$011\dots11 = 100\dots00 - 000\dots01$**
- **Example** If $A = 7 = 0111_2$, then we will successively
 - add B, add B, add B, and add 0
 - Booth recoding “recodes” the number 7 as $8 - 1 = 1000_2 - 0001_2$

		Multiplication	
	0010		
x	0111		
+	0010	add	(1 in multiplier)
+	0010	add	(1 in multiplier)
+	0010	add	(1 in multiplier)
+	0000	shift	(0 in multiplier)
	00001110		


Signed Multiplication

- The idea is that:
 - we **subtract** when we first see a 1 to **replace a string of 1s in multiplier**
 - then later we **add** for the bit **after the last one**

	0010		
x	0111		
<hr/>			
+	0010	add	(1 in multiplier)
+	0010	add	(1 in multiplier)
+	0010	add	(1 in multiplier)
+	0000	shift	(0 in multiplier)
<hr/>			
	00001110		

Signed Multiplication

 - The idea is that:
 - we **subtract** when we first see a 1 to **replace a string of 1s in multiplier**
 - then later we **add** for the bit **after the last one**




	0010	
x	0111	
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	00001110	

	0010	
x	0111	
-	0010	sub (first 1 in multpl)
+	0000	shift (0 in multiplier)
+	0000	shift (0 in multiplier)
+	0010	add (prior step had last 1)
	00001110	

Signed Multiplication

 - The idea is that:
 - we **subtract** when we first see a 1 to **replace a string of 1s in multiplier**
 - then later we **add** for the bit **after the last one**



	0010	
x	0111	
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	00001110	

	0010	
x	0111	
+	11111110	sub(first 1 in multpl)
+	0000	shift (0 in multiplier)
+	0000	shift (0 in multiplier)
+	0010	add(prior step had last 1)
	00001110	

Signed Multiplication

- Hence, to deal with **negative values of A**, all that is required is to sometimes **subtract B from P**, instead of adding either B or 0 to P
- **Rules:** If the initial content of A is $a_{n-1} \cdot \cdot \cdot a_0$, then step (i) in the multiplication algorithm becomes:
 - If $a_i = 0$ and $a_{i-1} = 0$, then **add 0** to P
 - If $a_i = 0$ and $a_{i-1} = 1$, then **add B** to P
 - If $a_i = 1$ and $a_{i-1} = 0$, then **subtract B** from P
 - If $a_i = 1$ and $a_{i-1} = 1$, then **add 0** to P

For the first step, when $i = 0$, take a_{i-1} to be 0

SPEEDING UP OPERATIONS

Speeding Up Operations

- ▶ Integer **addition** is the simplest operation and the most important
- ▶ Even for programs that do not do explicit arithmetic, addition must be performed to increment the program counter and to calculate addresses
- ▶ The delay of an N-bit ripple-carry adder is:


$$t_{\text{ripple}} = Nt_{FA}$$

where t_{FA} is the delay of a full adder

- ▶ There are different techniques to increase the speed of integer operations (which also lead to faster floating point operations), as the Carry Select Adder (CSA) and Carry Look-ahead Adder (CLA)


Carry-Select Adder

 - The **carry-select adder** improves speed dividing operands bits in blocks
- A **carry-select adder** consists of:
 - short ripple carry adders acting on blocks of bits
 - multiplexers
- The two blocks of bits is added with **two ripple-carry adders**, one with the carry-in equal to 0 and the other with the carry-in equal to 1



Carry-Select Adder

 - In the figure below **two** 4-bit **ripple-carry adders** are **multiplexed** together
- The resulting carry and sum bits are selected by the carry-in
- The correct result is selected by the actual carry-in which selects which adder had the correct assumption



Carry-Select Adder


Uniform-sized adder

A 16-bit carry-select adder with a uniform block size of 4 has:

- three of these blocks
- a 4-bit ripple-carry adder

A carry select block is **not needed** for the four **LSBs**

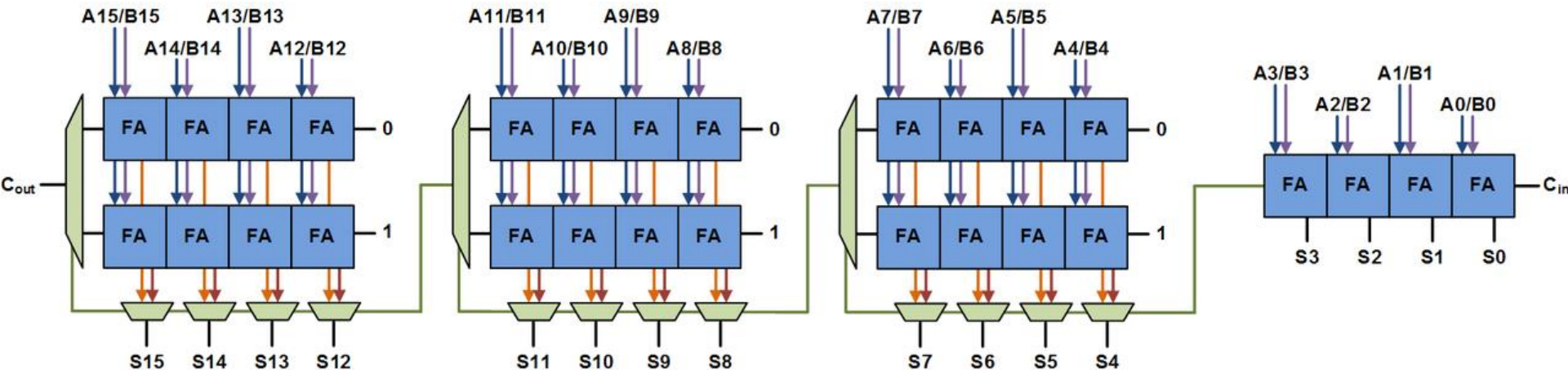The **delay** of this adder will be **four full adder delays plus three 2-to-1 MUX delays**




Carry-Select Adder

Variable-sized adder

A 16-bit carry-select adder with variable size can be created using block sizes of 2-2-3-4-5

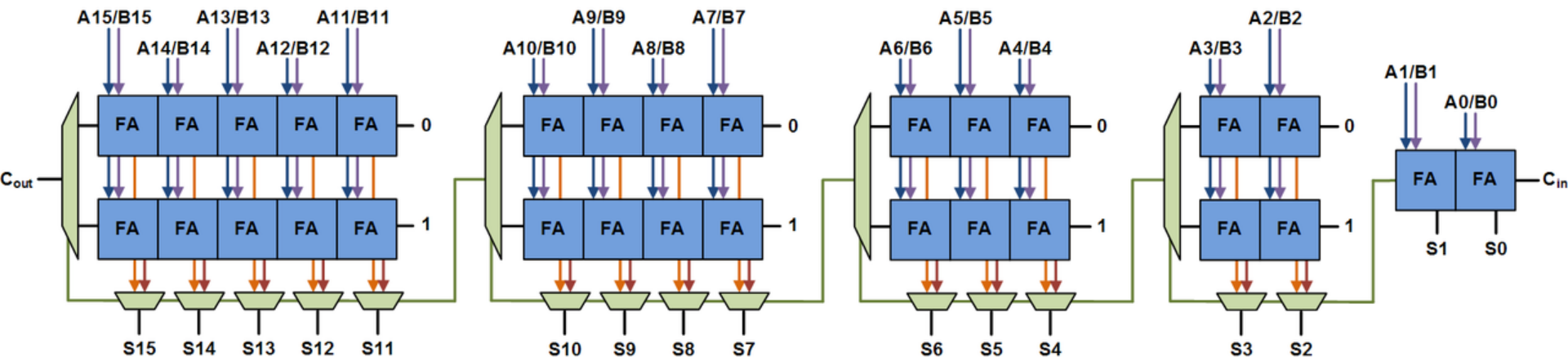- This break-up is ideal when **the full-adder delay is equal to the MUX delay**
- The total **delay** is **two full adder delays plus four mux delays**



Carry-Lookahead Adder

- A **carry-lookahead adder** improves speed by reducing the amount of time required to **determine carry bits**
- The carry-lookahead adder calculates **one or more carry bits** before the sum, which reduces the wait time to calculate the result of the larger-value bits of the adder
- Remember that:

$$c_{i+1} = a_i b_i + (a_i \oplus b_i) c_i$$

$$s_i = \overline{a_i} \overline{b_i} c_i + \overline{a_i} b_i \overline{c_i} + \overline{a_i} \overline{b_i} c_i + a_i b_i c_i = (a_i \oplus b_i) \oplus c_i$$

Carry-Lookahead Adder

We define:


- **Carry Generate** $g_i = a_i b_i$
- **Carry propagate** $p_i = a_i \oplus b_i$ or $p_i = a_i + b_i$

Then the **expression of the carry** is:

$$c_{i+1} = a_i b_i + (a_i \oplus b_i) c_i = g_i + p_i c_i$$

and the **expression of the sum** is:
 
$$s_i = (a_i \oplus b_i) \oplus c_i = p_i \oplus c_i$$



Carry-Lookahead Adder


If we consider 4 bits, we have c_1, c_2, c_3, c_4 , depend only on c_0 :

$$c_1 = a_0b_0 + (a_0+b_0)c_0 = g_0 + p_0c_0$$

$$c_2 = a_1b_1 + (a_1+b_1)c_1 = g_1 + p_1c_1 = g_1 + p_1g_0 + p_1p_0c_0$$


$$c_3 = a_2b_2 + (a_2+b_2)c_2 = g_2 + p_2c_2 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0$$
 
$$c_4 = a_3b_3 + (a_3+b_3)c_3 = g_3 + p_3c_3 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0$$



Carry-Lookahead Adder

 - So, a carry-lookahead adder on n bits requires a **fan-in of $n + 1$** at the **OR gate** as well as at the **rightmost AND gate**
- The irregular structure and long wires make it impractical to build a full carry-lookahead adder when n is large




Carry-Lookahead Addition

- Structure of a **4-bit CLA**


$$s_i = (a_i \oplus b_i) \oplus c_i = p_i \oplus c_i$$

 - A CLA requires:
 - one logic level to form p and g
 - two levels to form the carries
 - two for the sum
 - for a total of **five logic levels**
- Improvement** over the $2n$ levels required for the ripple-carry adder



Carry-Lookahead Addition

 - A **16-bit adder** can be built from four 4-bit CLAs and a 4-bit Look-ahead Carry Unit (LCU) at the second level



- A **64-bit adder** can be built from four **16-bit adder** shown above, and an additional LCU that accepts bits from each LCU above and generates carry bits fed back to
- https://en.wikipedia.org/wiki/Lookahead_carry_unit

Carry-Lookahead Addition



We can use the carry-lookahead idea to build an adder that has about $\log_2 n$ logic levels, as in a tree

Starting from

- $G_{01} = g_1 + p_1 g_0$
- $P_{01} = p_1 p_0$

In general, for any j with $i < j$ and $j + 1 < k$, we have the **recursive relations**:

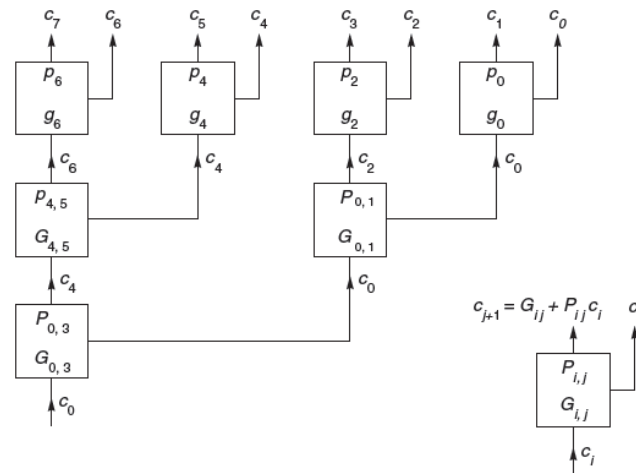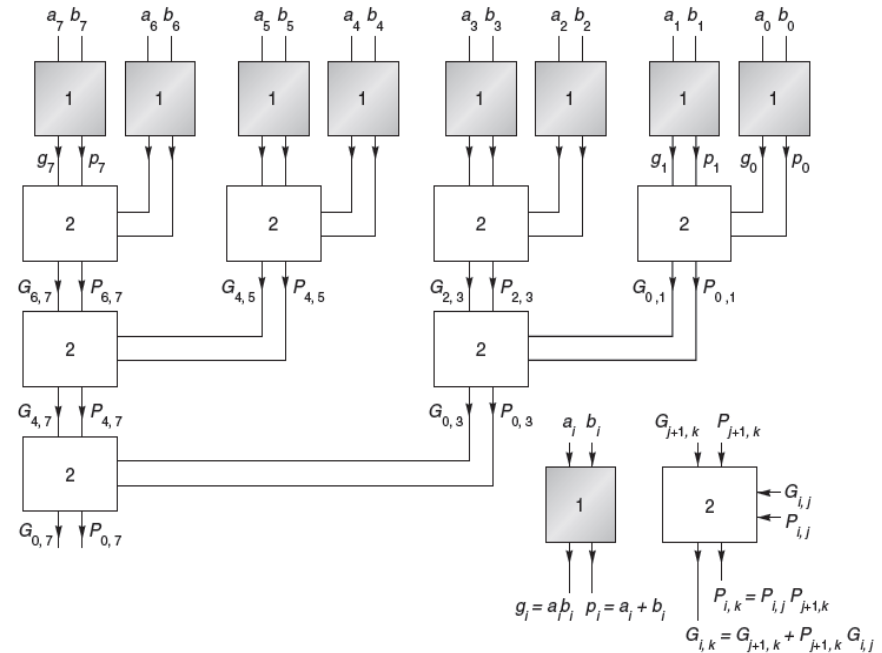- $c_{k+1} = G_{ik} + P_{ik} c_i$
- $G_{ik} = G_{j+1,k} + P_{j+1,k} G_{ij}$
- $P_{ik} = P_{ij} P_{j+1,k}$




Carry-Lookahead Addition

First part of carry-lookahead tree:

- signals flow **from the top to the bottom**
- various values of P and G are computed


Second part of carry-lookahead tree:

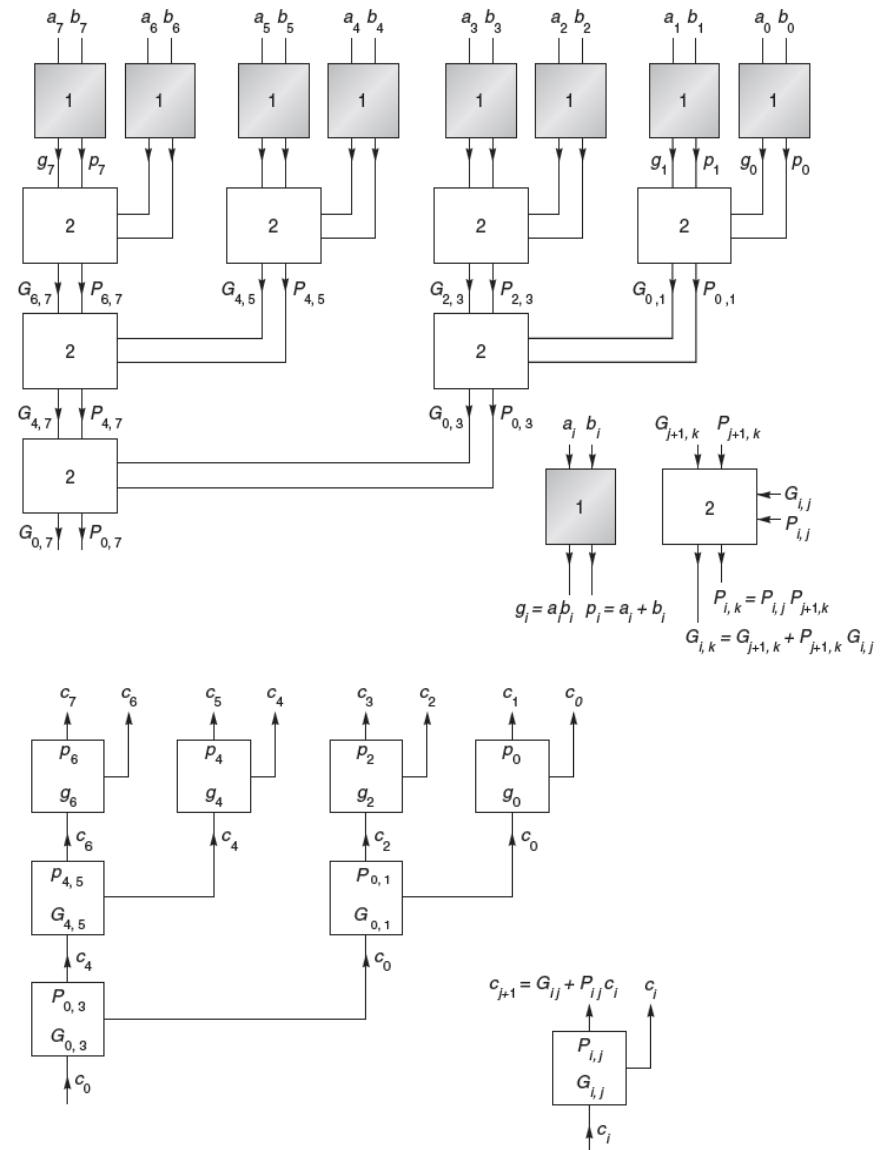- signals flow **from the bottom to the top**, combining with P and G to form the carries




Carry-Lookahead Addition

 - Using the **recursive** relations, practical CLAs are designed by combining cells in a **binary tree structure**
- The numbers to be added flow into the **top** and go downward through the tree, combining with **c0** at the **bottom** and **flowing back up** the tree to form the carries



Carry-Lookahead Addition

 - The bits in a CLA pass through about $\log_2 n$ logic levels, compared with $2n$ for a ripple-carry adder
- But** the ripple-carry adder has n cells and the CLA has $2n$ cells, even if they will take $n \log n$ space
- Speed improvement** especially for a large n



Speeding Up Multiplications

- Methods that increase the speed of **multiplication** can be divided into two classes:
 - single adder
 - multiple adders
- In the simple multiplier we described, each multiplication step passes through the **single adder**
- The amount of computation in each step depends on the used adder (consider the difference between an RCA and a CLA)
- If the space for **many adders** is available, then multiplication speed can be increased thanks to the replication of resources

PIPELINED ARITHMETIC OPERATIONS

Pipelined arithmetic


- Consider the instruction pipelining:
 - The processor goes through a repetitive cycle of fetching and processing instructions
 - In the absence of hazards:
 - the processor is continuously fetching instructions from their locations
 - the pipeline is kept full
 - a savings in time is achieved
- Similarly, a **pipelined ALU** will save time if it is **fed a stream of data** from sequential locations
- A single, isolated operation is not speeded up by pipeline
- The speedup is achieved when **a vector of operands** is presented to the units in the ALU

Pipelined arithmetic

- The relative simplicity of two-operand adders usually does not justify their implementation as pipelines
- In special-purpose design, when **many successive additions** are needed, such implementations are justifiable
- Some adders can be implemented as pipeline, such as the conditional-sum adder or the *carry-save adder* (for multiple operands)
- But, for example, some design of the *carry look-ahead adder* cannot be pipelined because some carry signals propagate backward
- There are very simple schemes for the **pipelined adders** and **multipliers** along the lines of the ripple-carry adder


Pipelined Addition

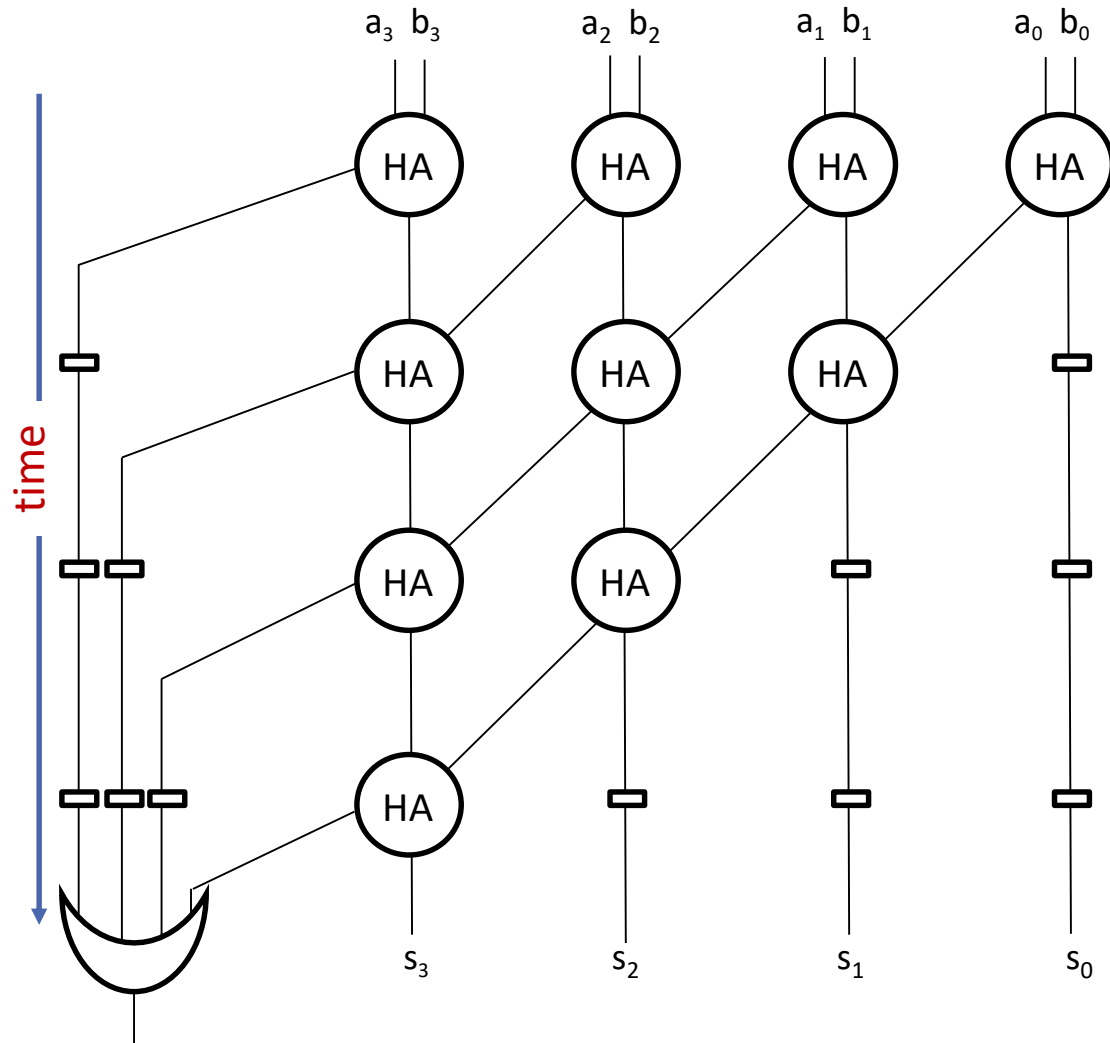- For n bits operands, a **pipeline adder** consists of n stages of half adders
- Registers (FF D) are inserted at each stage to synchronize the computation
- At each clock cycle a new pair of operands is applied to the inputs of the adder




Pipelined Addition

 - After **n clock cycles**, the **sum of the first pair of operands** is obtained
- The computing time for a single sum is the same of the carry-ripple adder
- A **new sum** is obtained at **each clock cycle** starting from the **$(n+1)$ -th clock cycle**




Pipelined Addition

 
- The number of **HA** is **$O(n^2)$** , whereas the circuit complexity of the carry-ripple adder is $O(n)$
- The added circuit complexity pays off if long sequences of numbers are being added



Pipelined Unsigned Multiplication

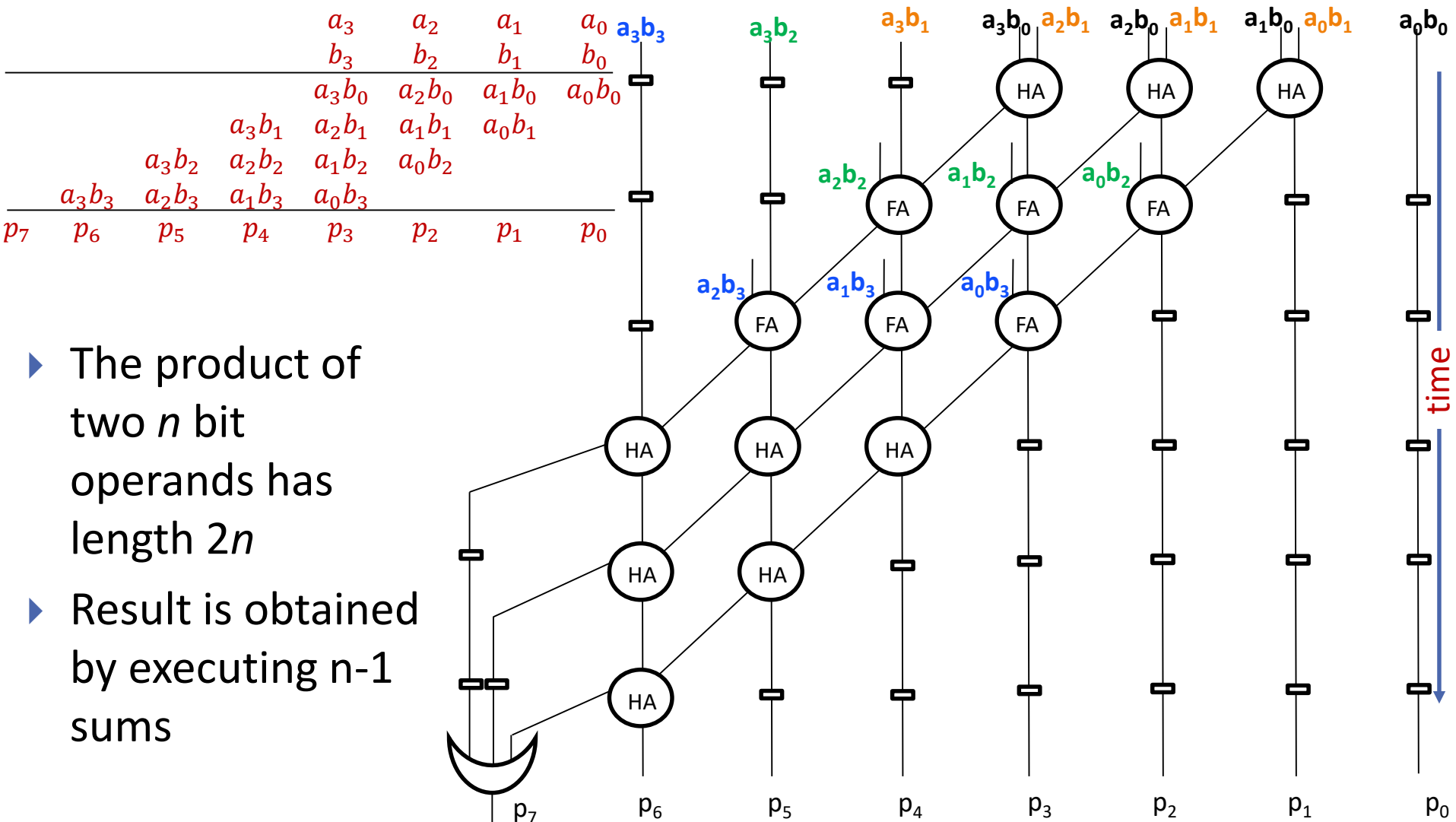


Pipelined Unsigned Multiplication

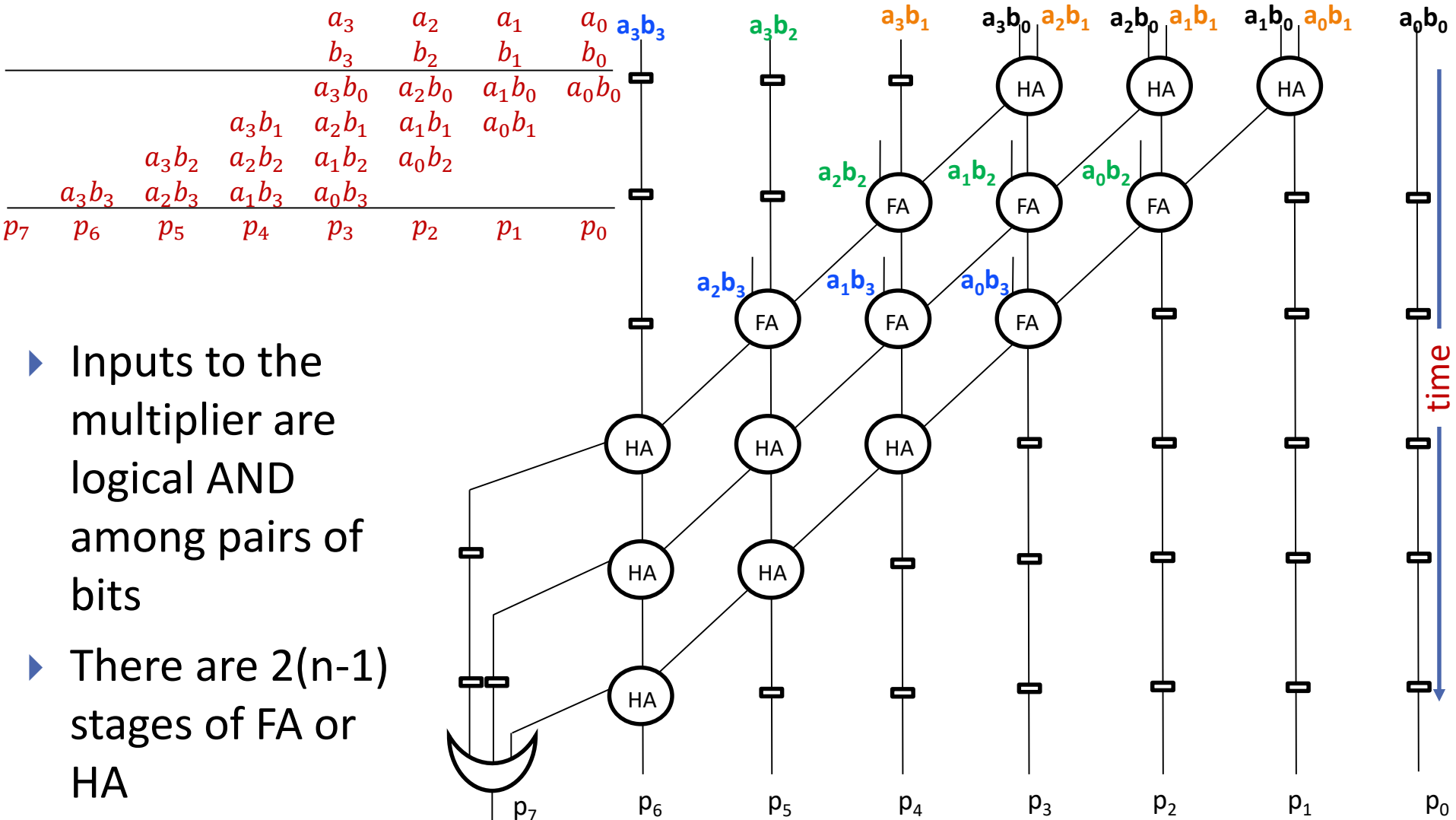

- Inputs to the multiplier are logical AND among pairs of bits
- There are $2(n-1)$ stages of FA or HA


Pipelined Unsigned Multiplication

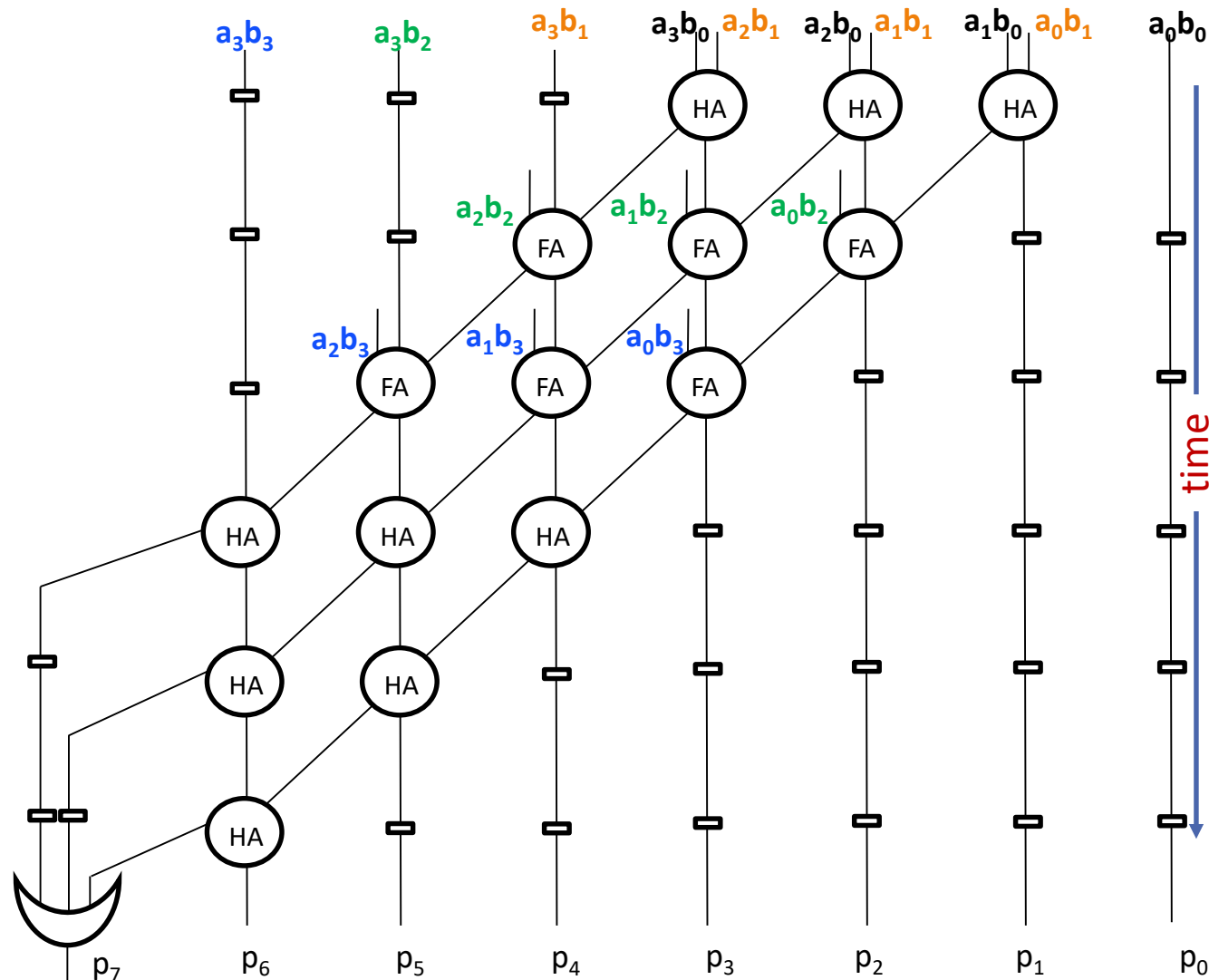- ▶ After stage (n-1) all bit products (AND) are added
- ▶ Last (n-1) stages represent a pipelined adder
- ▶ Bit p_{2n-1} of the result is obtained as OR among the carries generated by the most left HA of each stage



Pipelined Unsigned Multiplication

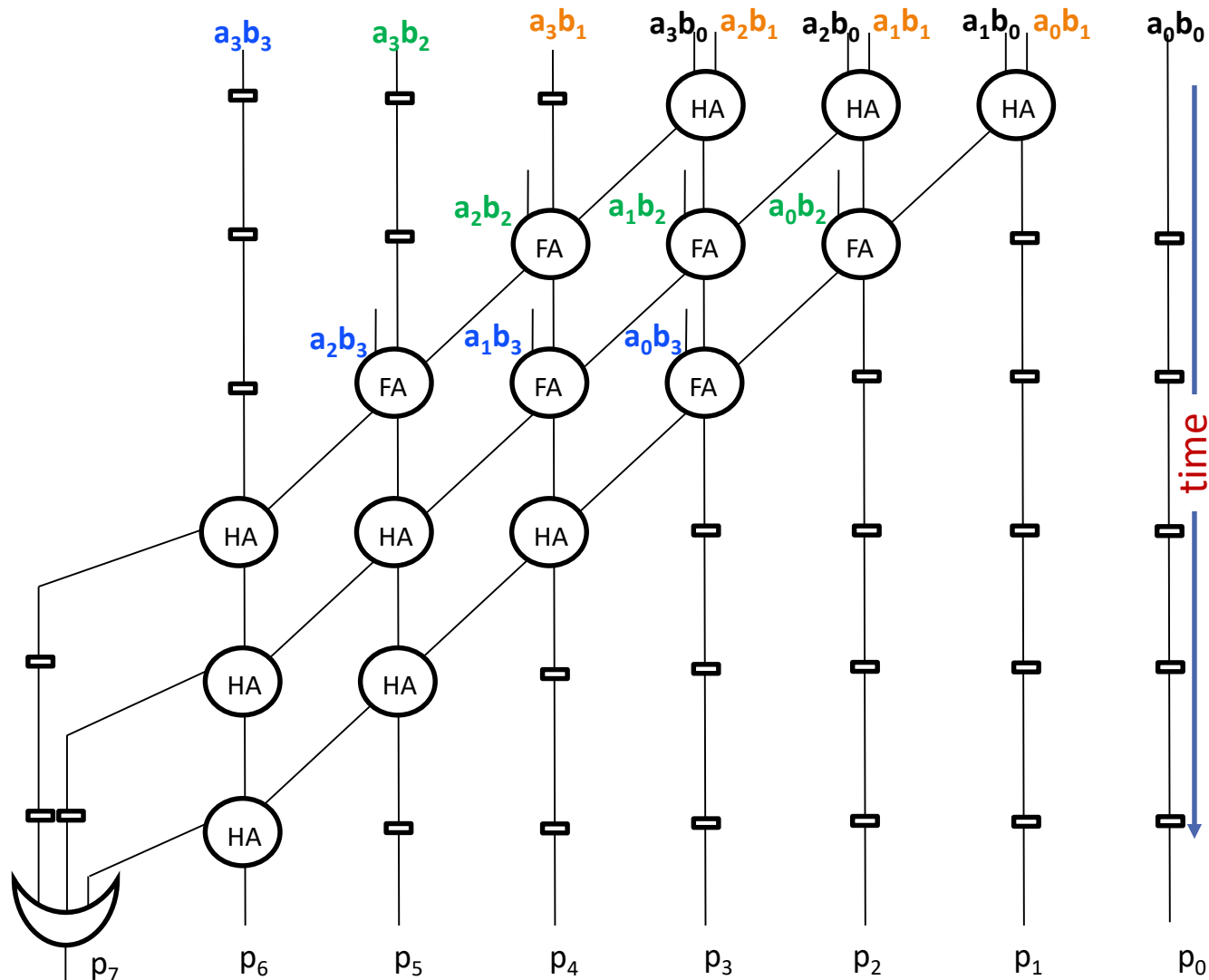- ▶ After $2(n-1)$ clock cycles, the product of the first pair of operands is obtained
- ▶ A new result is obtained at each clock cycle starting from the $(2n-1)$ -th clock cycle




Pipelined Signed Multiplication

- Signed numbers** are arithmetically extended to the **length $2n$** of the product

- Example with 3-bit operands**

	a_5	a_4	a_3	a_2	a_1	a_0
	b_5	b_4	b_3	b_2	b_1	b_0
a_5b_1	a_5b_0	a_4b_0	a_3b_0	a_2b_0	a_1b_0	a_0b_0
a_4b_2	a_4b_1	a_3b_1	a_2b_1	a_1b_1	a_0b_1	
a_3b_3	a_3b_2	a_2b_2	a_1b_2	a_0b_2		
a_2b_4	a_2b_3	a_1b_3	a_0b_3			
a_1b_5	a_1b_4	a_0b_4				
a_0b_5	a_0b_5					
	p_5	p_4	p_3	p_2	p_1	p_0

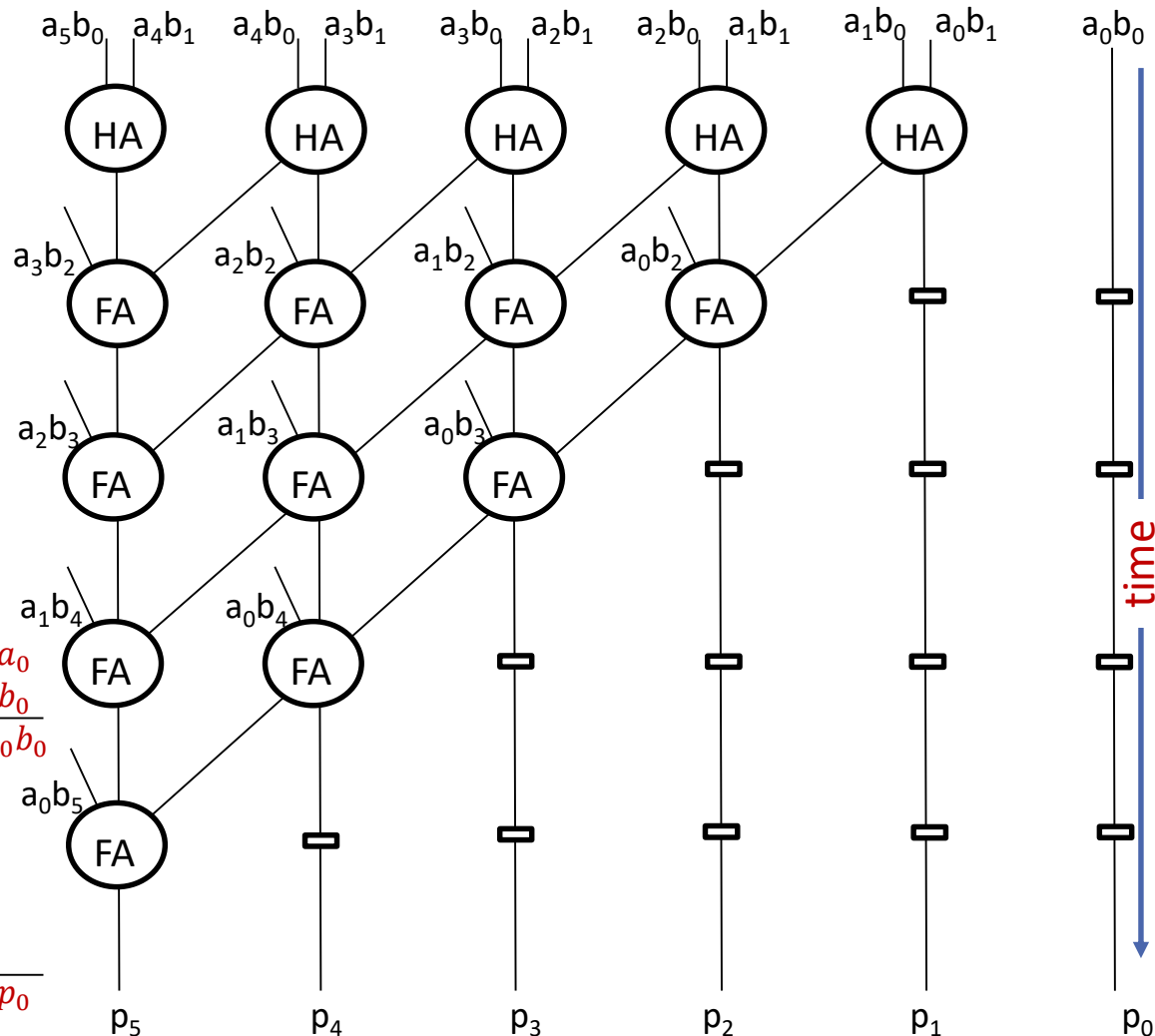


Pipelined Signed Multiplication

- Partial products of length $2n$ are considered (the remaining part is ignored)
- All stages except the first consist of FAs

- Example with 3-bit operands**

	a_5	a_4	a_3	a_2	a_1	a_0
	b_5	b_4	b_3	b_2	b_1	b_0
	a_5b_0	a_4b_0	a_3b_0	a_2b_0	a_1b_0	a_0b_0
a_5b_1	a_4b_1	a_3b_1	a_2b_1	a_1b_1	a_0b_1	
a_5b_2	a_4b_2	a_3b_2	a_2b_2	a_1b_2	a_0b_2	
a_4b_3	a_3b_3	a_2b_3	a_1b_3	a_0b_3		
a_3b_4	a_2b_4	a_1b_4	a_0b_4			
a_2b_5	a_1b_5	a_0b_5				
	p_5	p_4	p_3	p_2	p_1	p_0

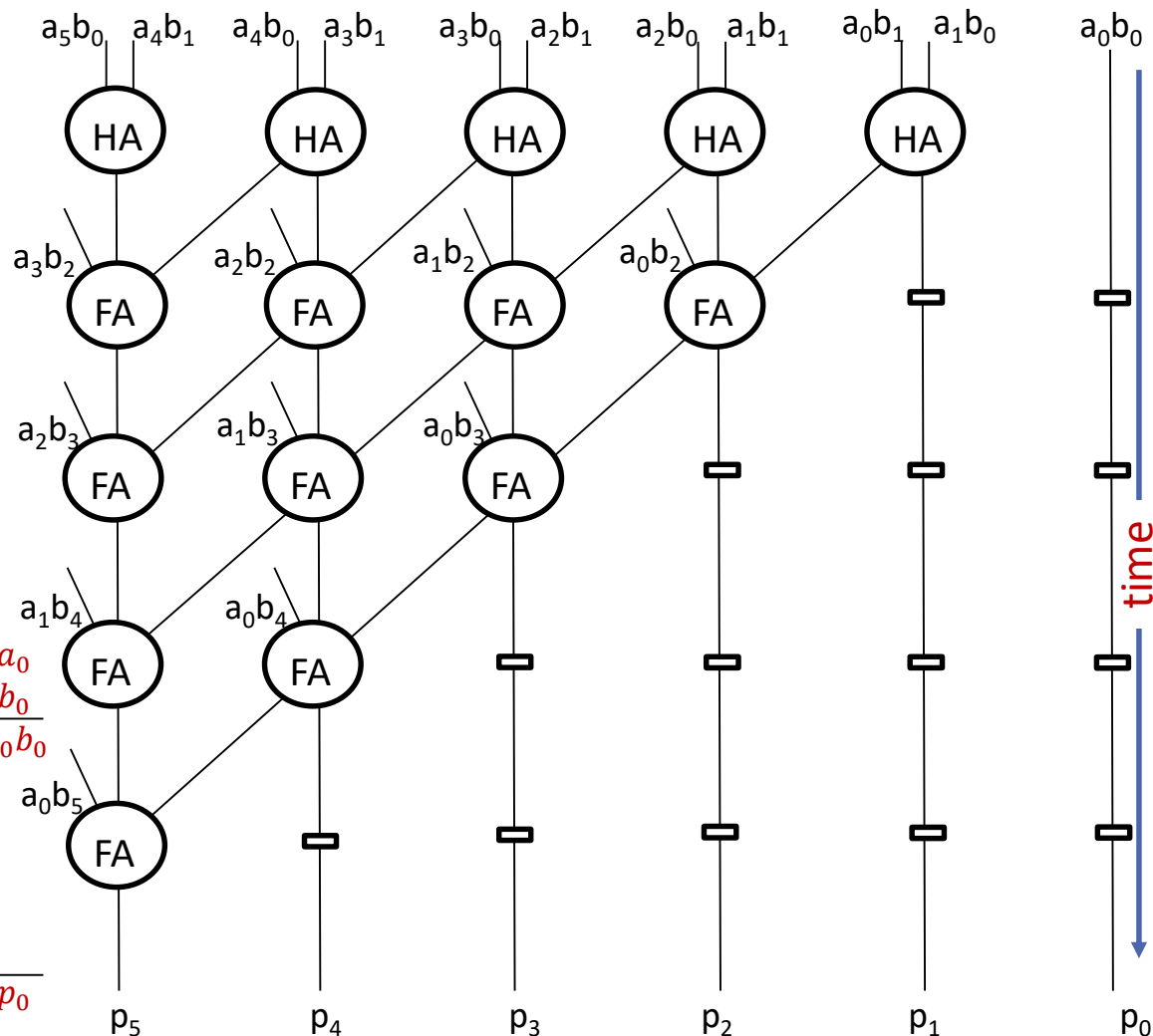

CIRCUIT AREA AND TIME EVALUATION

Circuit area and time

- To discuss about the time and area, it is useful the analytical model called **unit-gate model** presented in
 - A. Tyagi, *A reduced-area scheme for carry-select adders*, IEEE Trans. Comput., 1993is commonly used
- They propose a simplistic model for **gate-count** and **gate-delay**:
 - Each gate except **EX-OR** counts as **one elementary gate**
 - An **EX-OR gate** is counted as **two elementary gates**, because in static CMOS, an **EX-OR** gate is implemented as two elementary gates (**NAND**)
 - The **delay** through an elementary gate is counted as **one gate-delay unit**, but an **EX-OR gate** is **two gate-delay units**

Circuit area and time


- If the ***fan-in*** and ***fan-out*** of the gates are ignored, unfair comparisons are produced for circuits containing gates with a large difference in *fan-in* or *fan-out*
 - For example, gates in the **CLA adder** have different *fan-in*
 - A **carry-ripple adder** has no gates with *fan-in* and *fan-out* greater than 2
- The **gate-count** and **gate-delay** comparisons may not always be consistent with the area-time comparisons if the *fan-in* of gates is not taken into account
- The best comparison for a VLSI implementation is **actual** area and time

Circuit area and time

- In summary, we consider:
 - **Any gate** (but the EX-OR) counts as **one gate** for both area and delay $\rightarrow A_{\text{gate}}$ and T_{gate}
 - An **exclusive-OR gate** counts as **two elementary gates** for both area and delay $\rightarrow A_{\text{EX-OR}} = 2A_{\text{gate}}$ and $T_{\text{EX-OR}} = 2T_{\text{gate}}$
- To **take into account the fan-in and fan-out**, we consider that an **m-input gate** counts as:
 - **m - 1 gates** for area $\rightarrow A_{\text{m-gate}} = (m-1)A_{\text{gate}}$
 - **$\log_2 m$ gates** for delay $\rightarrow T_{\text{m-gate}} = \log_2 m T_{\text{gate}}$



Circuit area and time

 - A half adder (HA) has:
 - **Delay:** 2 unit gates – $T_{HA} = 2 T_{gate}$
 - **Area:** 3 unit gates – $A_{HA} = 3 A_{gate}$





Circuit area and time

  - A **half adder** (HA) has:
 - **Delay:** 2 unit gates – $T_{HA} = 2 T_{gate}$
 - **Area:** 3 unit gates – $A_{HA} = 3 A_{gate}$
- A **full adder** (FA) has:
 - **Delay:** 4 unit gates – $T_{FA} = 4 T_{gate}$
 - **Area:** 7 unit gates – $A_{FA} = 7 A_{gate}$



Circuit area and time

  - A **half adder** (HA) has:
 - **Delay:** 2 unit gates – $T_{HA} = 2 T_{gate}$
 - **Area:** 3 unit gates – $A_{HA} = 3 A_{gate}$
- A **full adder** (FA) has:
 - **Delay:** 4 unit gates – $T_{FA} = 4 T_{gate} = 2 T_{HA}$
 - **Area:** 7 unit gates – $A_{FA} = 7 A_{gate} = 2 A_{HA} + A_{gate}$




Circuit area and time

- A ripple-carry adder for n-bits operands has:

- Delay:** $T_{\text{RC-adder}} \rightarrow T_{\text{RC-adder}} = n T_{\text{FA}} = 2n T_{\text{HA}} = 4n T_{\text{gate}}$

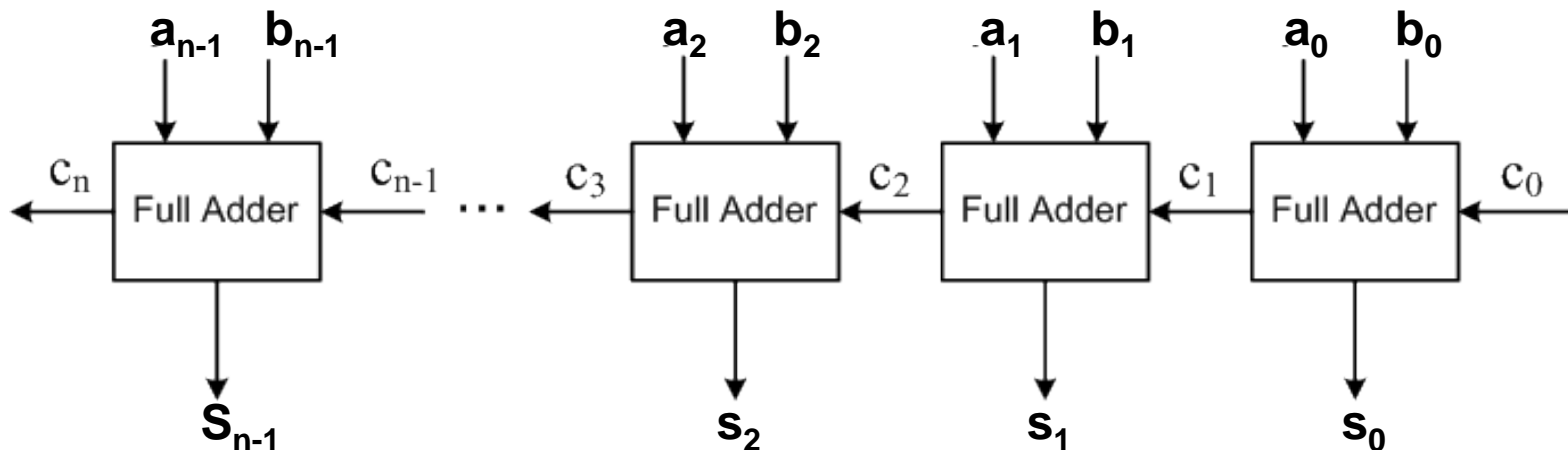- Area:** $A_{\text{RC-adder}} \rightarrow A_{\text{RC-adder}} = n A_{\text{FA}} = 2n A_{\text{HA}} + n A_{\text{gate}} = 7n A_{\text{gate}}$




Circuit area and time

 Exercise

Compute the time (propagation delay) and area required by the 4-bits Carry-Save-Adder, that is an adder for three values A, B and C, shown here below.

Compute the speedup of 4-bits Carry-Save-Adder with respect to the standard binary ripple-carry adder.



Delay and Area for the Ripple-carry adder

- $T_{RC\text{-adder}} = n T_{FA} = 2n T_{HA} = 4n T_{gate}$
- $A_{RC\text{-adder}} = n A_{FA} = 2n A_{HA} + n A_{gate} = 7n A_{gate}$