


SAPIENZA
 UNIVERSITÀ DI ROMA
 DIPARTIMENTO DI INFORMATICA

Combinatorial Nets: analysis and synthesis
 Prof. Daniele Gorla



SAPIENZA
 UNIVERSITÀ DI ROMA
 DIPARTIMENTO DI INFORMATICA


Combinatorial Net

A *combinatorial net* is a digital electronic circuit that can automatically compute a BF.

An *electronic circuit* is a system made up by elementary gates acyclically interconnected.


Lines entering into gates that do not exit from other gates are the *inputs*.

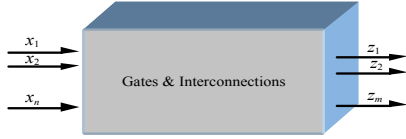Exits of gates that do not enter in other gates are the *outputs*.



$z_i = f_i(x_1 \dots x_n) \quad (i=1 \dots m)$

REMARK: output values in every moment univoquely depend from the input values.



SAPIENZA
 UNIVERSITÀ DI ROMA
 DIPARTIMENTO DI INFORMATICA

Circuitual Schema


A circuitual schema is the interconnection between gates (represented in a graphical way) through lines.

We have 3 kinds of lines:

1. **Input lines**, each labeled by one of the n boolean variables;
2. **Output lines**, each labeled by one of the m output variables (one for every computed BF);
3. **Inner lines**, each connecting the output of a gate with the input of other gates.

Constraints:

- Every input of every gate must be either an input line or an inner line;
- Every output of every gate must be either an output line or an inner line;
- Gates interconnections must NOT generate cycles.




SAPIENZA
 UNIVERSITÀ DI ROMA
 DIPARTIMENTO DI INFORMATICA

Inductive Definition of Combinatorial Net


A **combinatorial net with one output (CN1)** is inductively defined as:

- a line connecting input x to output z
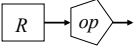
$$x \longrightarrow z$$
 is a CN1;
- if R is a CN1 and op is a unary gate (NOT), then also



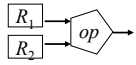
 is a CN1;
- if R_1 and R_2 are CN1 and op is a binary gate (AND, OR, NOR, NAND, XOR, XNOR), then also



 is a CN1, once inputs with the same label are joint together.

A **combinatorial net with m outputs** (simply, **combinatorial net**, CN) is the justapposition of m CN1 obtained by joining inputs with the same label.


 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Relation between Bes and CNs

For every BE there exists a unique CN (actually, CN1) made up by NOT, AND & OR gates that computes it.

Procedure:

- Given a BE, write it in a hierarchical way, by putting at the top level the last operators (out-most); variables will be at the bottom level
→ pay attention to the precedence rules for operators
($\bar{\quad} > \cdot > +$)
- Clockwise turn this representation by 90°; this gives you the structure of the CN, with inputs at left and outputs at right
- Turn every operator in the corresponding gate and link every gate of every level to a gate of the next level by a line

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA


Example

$x + \overline{y \cdot z}$

-
-
-

REMARK: by using NAND, NOR, XOR and XNOR gates, we loose unicity!

Ex.:

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Relation between CNs and BEs


For every CN with m outputs there exists a m -tuple of BEs that describes it; such an m -tuple is unique up-to variables renaming (associated to the inputs of the CN)

Procedure:


- Label every input with a different variable
- For every gate (with inputs already labeled by a BE), label the output with the BE resulting from the operation of the gate over the inputs
- Iterate until all outputs are labeled with a BE

Ex.:

$\bar{x} \cdot y +$
 $x \cdot z \cdot t +$
 $\bar{t} \cdot y \cdot z +$
 $y \cdot z$

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Summing up: relations between BFs, Tts, BEs and CNs

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Analysis of CNs

AIM: given a CN, find the computed BF


STEPS: CN \rightarrow^1 BE \rightarrow^2 TT (= BF)

Step 1 has been just considered in this class


Step 2 can be done by using one of the many methods for passing from a BE to a TT:

- Perfect induction: consider all the possible truth values to the variables and incrementally build the TT
- By using DNFs, DCFs, CNFs or CCFs

9

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Example

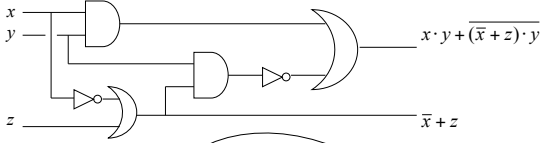

$$x \cdot y + (\bar{x} + z) \cdot \bar{y}$$


$$\bar{x} + z = \bar{x} + z + y\bar{y} = (\bar{x} + y + z)(\bar{x} + \bar{y} + z) = M_4 \cdot M_6$$

DNF

x	y	z	f ₁	f ₂
0	0	0	1	1
0	0	1	1	1
0	1	0	0	1
0	1	1	0	1
1	0	0	1	0
1	0	1	1	1
1	1	0	1	0
1	1	1	1	1

CCF

10

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Synthesis of CNs

AIM: given a verbal description of a BF, find a CN that computes it


STEPS: Verbal description \rightarrow^1 BF (= TT) \rightarrow^2 BE \rightarrow^3 CN

Step 1 is the only one for which we cannot give a “mechanical” procedure (it depends on the verbal description: we shall see many examples!)

Step 2 is done by using one of the ways for passing from a TT to a BE. Since we’d like to have the smallest possible CN, we shall usually rely on the KMs for finding a minimal DNF/CNF and then we shall simply as much as possible, by using Boole axioms and/or NAND/NOR/XOR/XNOR gates

Step 3 is the way we saw in this class for having a CN starting from a BE

11

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Example (1)

Design the control circuit of a tap that controls the amount of water in a chemical solution. The tap must be closed if:

1. The tank is full; or
2. The drain valve is closed, the reagents concentration is enough and the water level is not low.

SOLUTION:

We associate a (input) variable to every event:

- Tk = 1 if the tank is full, 0 otherwise;
- V = 1 if the drain valve is open, 0 if closed;
- C = 1 if the reagents concentration is enough, 0 otherwise;
- L = 1 if the water level is low, 0 otherwise.

Also the function to be computed is an event, hence it is a (output) variable:

- T = 1 if the tap is open, 0 otherwise.

12

Example (2)

From the verbal description to the TT:

Tk	V	C	L	T
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$T = 0$ if $V = 0, C = 1$ and $L = 0$

$T = 0$ if $Tk = 1$

The tap must be closed if:
 1. the tank is full; or
 2. the drain valve is closed, the reagents concentration is enough and the water level is not low.

$Tk = 1$ iff the tank is full;
 $V = 1$ iff the valve is open;
 $C = 1$ iff the concentration is enough;
 $L = 1$ iff the water level is low;
 $T = 1$ iff the tap is open.

Example (3)

Karnaugh Map:

Tk	V	00	01	11	10
00	00	1	1	0	0
01	00	1	1	0	0
11	00	1	1	0	0
10	00	0	1	0	0

Minimal DNF: $T = \overline{Tk}V + \overline{Tk}\overline{C} + \overline{Tk}L$

Minimal BE: $T = \overline{Tk}(V + \overline{C} + L)$

Circuit:

OBS.: this is a minimal POS that we'd have obtained from the KM by covering the 0s

Example (4)

OBS.: in this example, we could have derived the minimal BE directly from the verbal description, without passing through the TT and the KM:

Once defined the boolean variables, we have that
 "The tap must be closed if: (1) the tank is full; or (2) the drain valve is closed, the reagents concentration is enough and the water level is not low"

can be directly translated to $\overline{T} = Tk + \overline{V}C\overline{L}$

from which $T = \overline{\overline{Tk + \overline{V}C\overline{L}}} = \overline{Tk}(V + \overline{C} + L)$

Example (5)

REMARK: with a different choice of the variables associated to the events, we'd have had a different TT (and hence also the BE)!!

Ex.: $Tk = 0$ if the tank is full, 1 otherwise;
 $L = 0$ if the water level is low, 1 otherwise.

Would lead to $\overline{T} = \overline{Tk} + \overline{V}C\overline{L}$

and hence $T = Tk(V + \overline{C} + \overline{L})$

A second example (1)



Design a combinatorial circuit that receives in input bit quadruples with an even number of "1s" and returns 1 if the number of "1s" equals the number of "0s".

SOLUTION:

In this case, we have 4 input variables, one for every bit of the quadruple;

moreover, configurations with an odd number of "1s" will never appear; hence, we shall use *don't care* symbols for such quadruples.

$x y z t$	f
0000	0
0001	-
0010	-
0011	1
0100	-
0101	1
0110	1
0111	-
1000	-
1001	1
1010	1
1011	-
1100	1
1101	-
1110	-
1111	0

A second example (2)



KM:

Minimal DNF: $\bar{z}t + \bar{x}z + x\bar{t}$
(8 gates)

Minimal BE: $\bar{z}t + z\bar{t} + \bar{x}z + x\bar{z} = (z \oplus t) + (x \oplus z)$
(3 gates!!!)

Not always the minimal DNF leads to the minimal BE