


Design of remarkable circuits: adder, comparator, completer and subtractor
 Prof. Daniele Gorla





Parallel Adder at n bits

Request: design a binary adder that performs the arithmetical sum of two n bits strings $A = a_{n-1}...a_0$ and $B = b_{n-1}...b_0$, seen as natural numbers.

Idea: compute the sum as we are used to

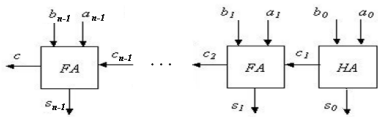
- Sum the less signifying bits a_0 and b_0 ;
- This generates the less signifying bit of the result s_0 and a possible carry c_1 ;
- Now sum a_1 , b_1 and c_1 ; this generates s_1 and c_2 ;
- ...and so on until the most signifying bits;
- If the last sum yields a carry c , then there is an overflow.






The elementary cell HA

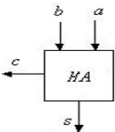
The sum of a_0 and b_0 (here, simply denoted as a and b) does not have to consider any preceding carry (it is the first sum of the sequence); however, it can generate a carry c :



b	a	s	c
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

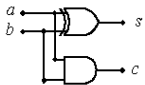


$s = a \oplus b$
 $c = ab$




The elementary cell FA

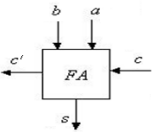If we denote with c the carry coming from the sum of a_{i-1} and b_{i-1} , and with c' the carry from the sum of a_i and b_i , we have the following truth table for the circuit that sums a_i and b_i (here, simply called a and b):



c	b	a	s	c'
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

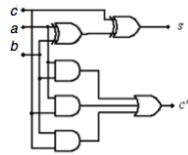

$s = (a \oplus b)\bar{c} + (a \oplus b)c = (a \oplus b) \oplus c$
 $c' = ac + bc + ab$


A Uniform Adder



Having two elementary circuits (HA and FA) makes the project more complex and costly.

To simplify, we can adopt a "uniform" version of the adder that only relies on FAs: it suffices to set the initial carry at 0 in the first elementary cell (that for the less signifying bits).

 REMARK: in this way, we have a few more gates, but I have to produce one single kind of elementary cell!!



Adder for integer numbers



As we saw, for integers represented in 2-complement the sum is done exactly in the same way; hence, the circuit is the same!

The only difference is the overflow condition:

- For naturals, we just have to check the last carry bit (1 → overflow)
- For integers, we have an overflow if
 - Operands have the same sign that is different from the result's sign
 - We obtain the "forbidden" sequence 10...0

Hence, the BE associated to the overflow for integers is

$$a_{n-1}b_{n-1}\bar{s}_{n-1} + \bar{a}_{n-1}\bar{b}_{n-1}s_{n-1} + s_{n-1}\bar{s}_{n-2}\dots\bar{s}_0$$

Opposite and Subtraction




Opposite

Recall that the opposite of $B = b_{n-1}\dots b_0$ is $\bar{b}_{n-1}\dots\bar{b}_0 + 1$, we have that the circuit for calculating the opposite of a number is:



Subtraction

 To compute $A - B$, we can do $A + (-B)$ and so the circuit for the difference is:



Arithmetical Comparator




Problem: given two binary n bits strings A and B representing two natural numbers, establish whether $A > B$, $A = B$ or $A < B$.

The circuit will be something like



- where:
- $c_> = 1$ iff $A > B$
 - $c_< = 1$ iff $A < B$
 - $c_< = 1$ iff $A = B$

 OBS.: $c_< = \text{NOR}(c_>, c_<)$; hence, we shall only design circuits for computing $c_>$ e $c_<$, from which



Structure of the comparator




The idea is similar to the adder, with the circuit made up of n elementary comparator cells put in cascade.

To this aim, we use some partial results defined as follows:

for every $i = 1, \dots, n$

 - $c'_> = 1$ iff $a_{i-1} \dots a_0 > b_{i-1} \dots b_0$
- $c'_= = 1$ iff $a_{i-1} \dots a_0 = b_{i-1} \dots b_0$



9

The elementary comparing cell



The truth table for CMP is

a	b	$c_>$	$c_=>$	$c'_>$	$c'_=>$
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	-	-
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	-	-
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	-	-
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	-	-

10

Synthesis of $c'_>$



The KM is

$a \ b$	00	01	11	10
$c_> \ c_=>$				
00	0	0	0	1
01	0	0	0	1
11	-	-	-	-
10	1	0	1	1

from which $c'_> = a\bar{b} + ac_> + \bar{b}c_> = a\bar{b} + (a + \bar{b})c_>$

11

Synthesis of $c'_=>$



The KM is:

$a \ b$	00	01	11	10
$c_> \ c_=>$				
00	0	0	0	0
01	1	0	1	0
11	-	-	-	-
10	0	0	0	0

from which $c'_=> = \bar{a}\bar{b}c_> + abc_> = (\bar{a}\bar{b} + ab)c_> = (a \oplus b)c_>$

12

Circuit Schema

