




## Latch and Flip-flop

Prof. Daniele Gorla




### Sequential Nets

Up to now, we have only considered *acyclic circuits*.


This was due to the implicit assumption that gates are *ideal*, in the sense that they have a zero crossing time.

Under this assumption, the following circuit is meaningless




because the value of  $y$  depends by itself (ill-founded definition).

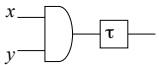In practice, gates have a non-zero crossing time, typically modelled through an ideal gate (with zero crossing time) and a delay  $\tau$ :



This introduces the **time factor** in circuits, and for this reason are called *sequential nets*.




### Variables changing over time

Hence, boolean variables will not have a simple 0/1 assignment, but such an assignment will change in time.


This is represented through a *temporal diagram*, i.e. a graphical representation that shows the variation of values that a variable undergoes over time.


Ex.:  $x$

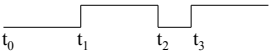

Similarly, a temporal diagram can represent the evolution in time of a whole sequential net:

Ex.:  $x$

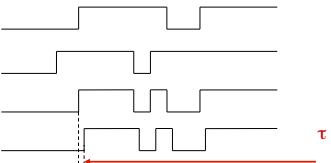



### Temporal Notation

Whereas for combinational circuits the expression  $y = x \cdot y$  was meaningless, now this makes sense because the leftmost  $y$  represents the value of the variable with a delay  $\tau$  w.r.t. the rightmost  $y$ .

→ same line in the temporal diagram, at different moments

For the sake of clarity, we shall write  $Y = x \cdot y$ , to stress that the first occurrence ( $Y$ ) represents the value at time  $t + \tau$ , whereas the second occurrence ( $y$ ) represents the value at time  $t$ .

So, Sequential nets compute boolean functions that vary in time according to:

1. variations of the input values, and
2. Output values of the net in previous time

→ circuits *with memory!!*

### Elementary Memory Circuits



The basic sequential circuit is the Flip Flop (FF), a circuit able to store **one bit** (see later on).



#### Latch SR

This is a preliminary memory circuit with 3 functionalities:





1. Store 1;
  2. Store 0;
  3. Hold the stored bit.
- } Codified through 2 bits (*s* and *r*)

The three functionalities are called *set*, *reset* and *hold*.





s	r	y	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	-	-
1	1	1	-

  





### Set status (*s* = 1, *r* = 0)

    

### Reset status (*s* = 0, *r* = 1)

    

### Hold status (*s* = 0, *r* = 0)

    

 
### The combination $s=r=1$ "flattens" the latch




In all status seen so far,  $z$  is the complement of  $y$  (after a proper delay).

This property is lost whenever  $s = r = 1$ ; moreover, in this case both  $z$  and  $y$  are 0, independently of the initial value of  $y$ .



$s = r = 1$  is a forbidden input for the latch!!

### Latch SR with NOR gates (summing up)

 

Circuit representation

$s r$	$Y$
00	$y$
01	0
10	1
11	-

Characteristic table


$y Y$	$s r$
00	0-
01	10
10	01
11	-0

Excitation table

 
### To avoid $s = r = 1$ (latch D)



A way for ensuring that  $s = r = 1$  never holds is the following:



 This is a new latch, called **latch D** (*delay*), that stores the input  $d$  and produces it on the output  $y$  after crossing the NOT and NOR gates.



Circuit Representation

$d$	$Y$
0	0
1	1

Characteristic table

$y Y$	$d$
00	0
01	1
10	0
11	1

Excitation function

### Use $s = r = 1$



Another way to handle  $s = r = 1$  is to add a new functionality to the latch:


$j k y$	$Y$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	0

like SR

$j k$	00	01	11	10
$y=0$	0	0	1	1
$y=1$	1	0	0	1


$$Y = j\bar{y} + \bar{k}y$$

or, by using an SR latch:

 

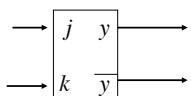**Latch JK**

This is a new latch, called **latch JK**, described by the following:



Circuit representation

$jk$	$Y$
00	$y$
01	0
10	1
11	$\bar{y}$


Characteristic table

$yY$	$jk$
00	0-
01	1-
10	-1
11	-0


Excitation table

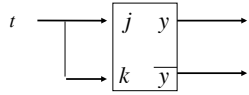**Latch T**

What happens in a latch JK when  $j = k$ ?



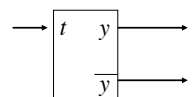This is a new latch, called **latch T (toggle)**, that either maintains the stored value ( $t = 0$ ) or complements it ( $t = 1$ ).



Circuit representation

$t$	$Y$
0	$y$
1	$\bar{y}$

Characteristic function


$yY$	$t$
00	0
01	1
10	1
11	0

Excitation function

**Synchronous and asynchronous systems**

Sequential nets can work in a **synchronous** or in an **asynchronous** way.

- In asynchronous systems, logical circuits change every time that one or more inputs change;
- In synchronous systems, the moment in which inputs are considered is given by a "periodic" signal, called *clock* (a train of square waves):




**Asynchronous systems** have the advantage that instantaneously react to input variations, but this makes their design extremely complex (hence, they are used only when an immediate reaction of the circuit is needed).


Actual computers almost only exploit **synchronous circuits!**

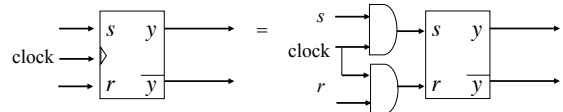**Gated latch**

Given a clock signal, we can put it in AND with the latch's inputs; in this way, inputs are considered only when the clock holds 1.



Ex.:

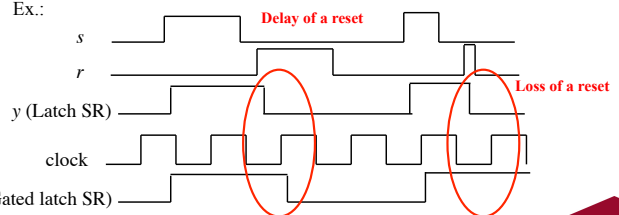

## Master-slave Flip-flop



Gated latches work well only if the clock holds 1 for a very short time.

A safer solution are the Master-slave Flip-flops (SR, for example), obtained by putting two gated latches in cascade, the first one obeying the clock, the second one obeying to the negated clock:

