


Sequential nets: Exercises
Prof. Daniele Gorla



Exercise 1:
Sequential adder

Design a sequential adder for natural numbers. Use the kind of FF that makes the resulting circuit as simple as possible.


2



Exercise 2:
sequence acceptor

Design a net that receives in input a bit sequence and returns in output 1 every time it receives the sequences "101" or "110", even with superpositions. Use FFs of kind D.

3



Exercise 3:
sequence replacement

Design a circuit that reads strings on the alphabeth $\{a,b,c\}$ and that replaces every occurrence of the substring "ab" with "ac". Use FF of kind T.

4