




 SAPIENZA

 UNIVERSITÀ DI ROMA

 DIPARTIMENTO DI INFORMATICA

Registers: Load/Unload & shifters

Prof. Daniele Gorla



 SAPIENZA

 UNIVERSITÀ DI ROMA

 DIPARTIMENTO DI INFORMATICA

Registers


A *register* is a sequence of n sorted FFs (for n fixed) where we can store a sequence of n bits.

Issues related to registers are:

- loading & unloading of infos
- functionalities provided by the register
- register interconnection

According to the type of data loading/unloading, we have:

- Parallel Input Parallel Output (PIPO)
- Serial Input Serial Output (SISO)
- Serial Input Parallel Output (SIPO)
- Parallel Input Serial Output (PISO)



 SAPIENZA

 UNIVERSITÀ DI ROMA

 DIPARTIMENTO DI INFORMATICA

Parallel Input Parallel Output

load →

clock →

D_1 →

...


D_n →


→ Q_1

→ ...

→ Q_n

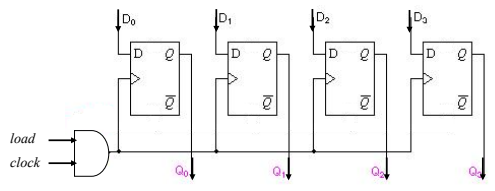Specification: it receives n data lines in input; the content of such lines is stored when the signal *load* holds 1 and when the clock is at a descending wave front (synchronous net). The stored value is unloadable after a time τ .





 SAPIENZA

 UNIVERSITÀ DI ROMA

 DIPARTIMENTO DI INFORMATICA

Serial Input Serial Output (1)


shift →


clock →

D →

→ Q

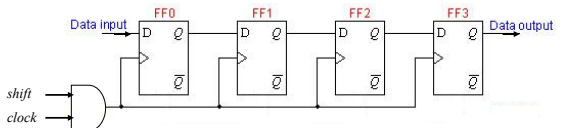
Specification: (*loading*) it receives in input one data line, whose values are progressively stored at every descending wave front of the *clock*, provided that the *shift* signal holds 1. (*unloading*) The stored n values loaded from the input are unloaded along the only output line, one for every descending wave front of the *clock* when the *shift* holds 1.




 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Serial Input Serial Output (2)


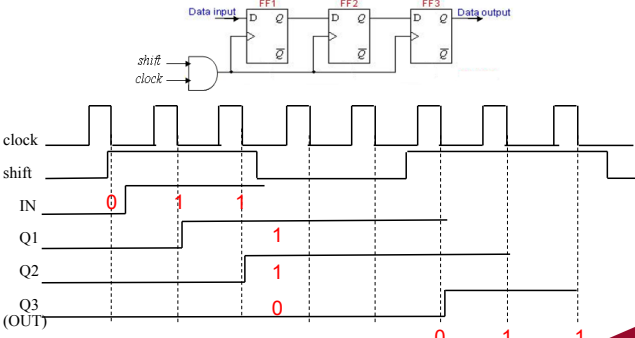
Behaviour: to store n bit, we have to keep *shift* at 1 for n descending wave fronts of the *clock*; furthermore, at every such front the input data line must provide the next bit to be stored. To unload the register, we have to keep *shift* at 1 for n wave fronts of the *clock* and retrieve bits from the output data line.




5

 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA


Serial Input Parallel Output

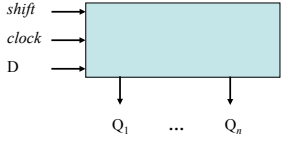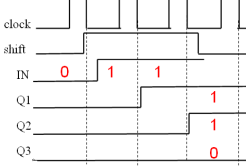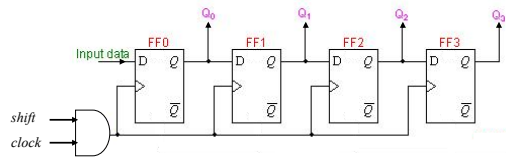
Specification: load like SISO, unload like PIPO



6


 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Parallel Input Serial Output (1)

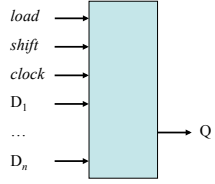


Specification: it stores the n inputs of the data lines whenever *load* holds 1 and the clock is at a descending wave front. The stored bits are unloaded whenever *shift* holds 1 (in n wave fronts of the clock).

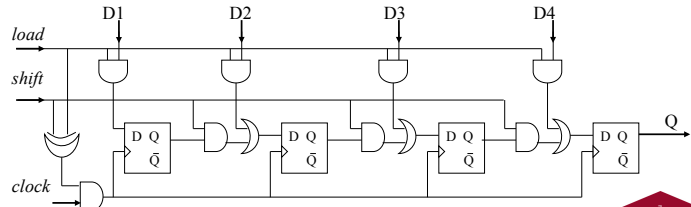REMARK: *load* and *shift* cannot both hold 1 at the same moment.




7


 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Parallel Input Serial Output (2)

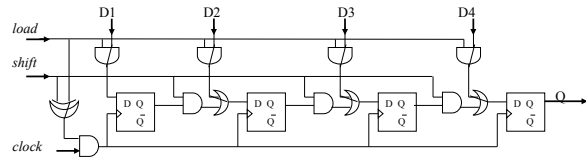- $shift = load$: their XOR is 0, so the register is in sleeping mode
- $shift = 0, load = 1$:



- $shift = 1, load = 0$:

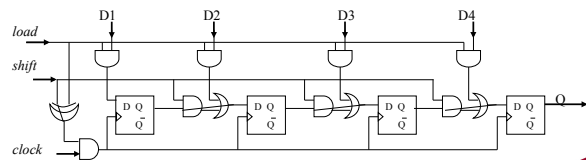

8

Registers with Operations



Independently of the kind of loading/unloading, a register can provide functionalities (operations on the stored bits).

There are 2 fundamental kinds of operations that a register can do:

- Shift
- Count

In this class we shall present the shifters, in the next one the counters.

9

Usage of shifters



Multiplication and division by 2 is very easy and efficient with shifters:

$$00001000_2 \times 10_2 = 00010000_2$$

left-shift, 1 position

$$00001000_2 \div 10_2 = 00000100_2$$

right-shift, 1 position

OBS.1: we loose the most/less signifying bit.

OBS.2: we replace the lost bit with a 0 at the opposite side of the register.


10

Basic Shifters




Right shifter:

 At every descending wave front of the *clock* when *shift* holds 1, it shifts the content of the FF *i* in the FF *i+1*, for $i \in \{1, \dots, n-1\}$



Left shifter:

 At every descending wave front of the *clock* when *shift* holds 1, it shifts the content of the FF *i* in the FF *i-1*, for $i \in \{2, \dots, n\}$




REMARK: we loose the content of FF *n* (right shifter) or of the first FF (left shifter). The first FF (right shifter) and the FF *n* (left shifter) now contain 0.

11


Bidirectional Shifter



 It behaves like a left/right-shifter according to a control bit *right*: if such a bit holds 1, we have a right shift, otherwise a left one:



12

 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Shifter with bit holding

If we work with integers in 2-complement, shifting as seen before doesn't work anymore to compute a division by 2:


$$11111110_{2\text{compl}} = -2_{10} \quad 11111111_{2\text{compl}} = -1_{10}$$

$$11111110_{2\text{compl}} \div 10_2 = 11111111_{2\text{compl}}$$

By contrast, performing a right shift of $11111110_{2\text{compl}}$ would give us $01111111_{\text{Ca}2} = 127_{10}!!$


So, when right shifting numbers in 2-complement we have to hold the most signifying bit, in the sense that we don't have to always put it at 0 but we have to keep the previous bit.

13


 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Shifter with holding


Right shifter:

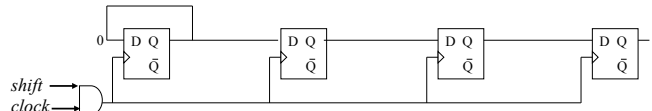


Left shifter:

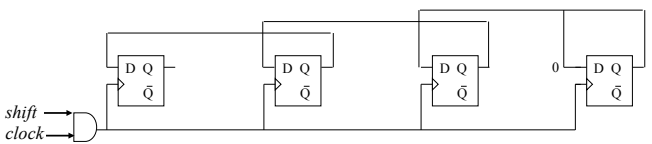


14

 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Bidirectional Shifter with holding

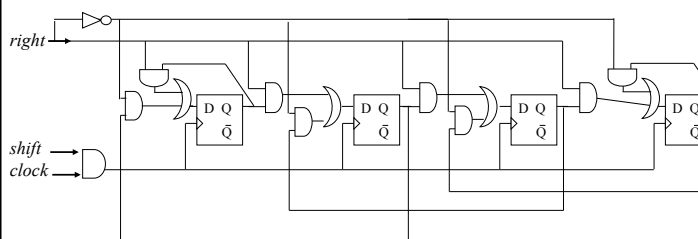


15

 **SAPIENZA**
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Shifter with/without holding


Right shifter:

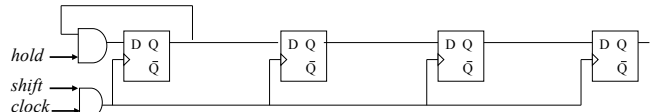

Similarly, we can design

- a left shifter with/without holding
- a bidirectional shifter with/without holding (in this case, we need both signals *hold* and *right*).


16

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA


Circular Registers

Another way not to lose the exiting bit during a shift is to store it from the other side of the register

In this way, the register is considered as circularly closed on itself:




17

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA


Counterclockwise Circular Register

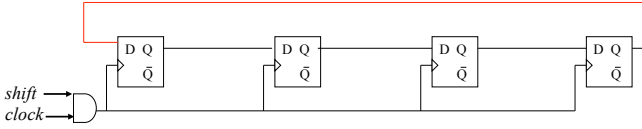Information stored in the register turns from left to right:




At every descending wave front of the *clock* when *shift* holds 1, the content of FF i is moved into FF $i+1$, for $i \in \{1, \dots, n-1\}$ and the content of FF n in the first FF.

18

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA


Clockwise Circular Register

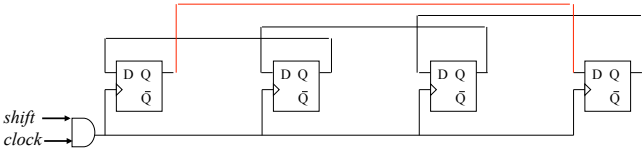Information stored in the register turns from right to left :




At every descending wave front of the *clock* when *shift* holds 1, the content of the FF i is moved into the FF $i-1$, for $i \in \{2, \dots, n\}$ and the content of the first FF into FF n .

19

 SAPIENZA
UNIVERSITÀ DI ROMA
DIPARTIMENTO DI INFORMATICA

Bidiretional Circular Register

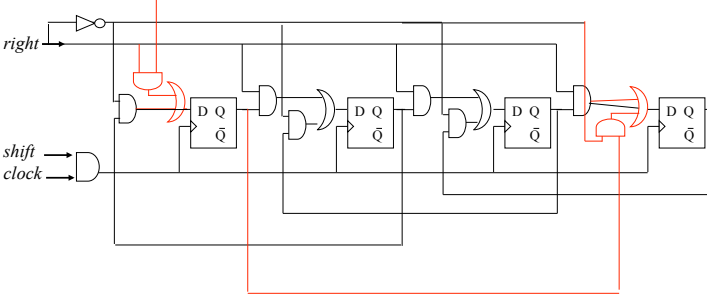

20