

CLASSWORK of COMPUTER ARCHITECTURES -- UNIT 1
January 12th, 2021

Name _____ Surname _____ Matric.numb. _____

Exercise 1 (3 points): Prove, by using axioms and laws of the Boolean algebra (and by specifying which axiom/law has been used), the following equality:

$$a b + c(\bar{a} + \bar{b}) = a b + c$$

Exercise 2 (3+1 points): Design a Mealy automaton with input alphabeth $\{X, Y, Z\}$ that accepts the sequences $XXYZ$, $XYXY$ and $XYZZ$ also with overlappings. How would the automaton change if no overlapping was allowed?

Exercise 3 (5 points): Design an interconnection net among registers R_0, R_1, R_2, R_3, R_4 and R_5 such that:

- If the value contained in R_0 is negative, then the arithmetic sum between R_0 and R_1 is moved into R_4 ; otherwise, R_4 receives the content of R_3 ;
- If R_2 is greater than R_3 , then R_1 is copied into R_5 ; otherwise, R_5 receives R_3 ;
- R_4 is copied into register R_i where i is given by the two less-signifying bits of R_5 .

The transfers are enabled only when the content of R_0 is a negative integer.

Exercise 4 (4 points): Turn into base 8 the number 339_{10} . Then, sum 267_8 to the obtained number, turn the result in base 2 and calculate the opposite of this number in 2-complement format with 12 bits.


Exercise 5 (3 points): Let $A = \langle 0;01111;00111100000 \rangle$ and $B = \langle 1;10001;00111100000 \rangle$ be two numbers in the IEEE half-precision format. Sum them and represent the result in the same format.

Exercise 6 (3+2 points): Consider the following automaton with initial state S_0 :

| | 0 | 1 |
|-------|---------|---------|
| S_0 | $S_1/1$ | $S_0/0$ |
| S_1 | $S_2/0$ | $S_3/1$ |
| S_2 | $S_1/0$ | $S_4/1$ |
| S_3 | $S_1/0$ | $S_0/0$ |
| S_4 | $S_2/0$ | $S_0/0$ |
| S_5 | $S_2/0$ | $S_3/0$ |

Minimize it and then provide (for the minimal automaton) the temporal diagram for the input 000101.

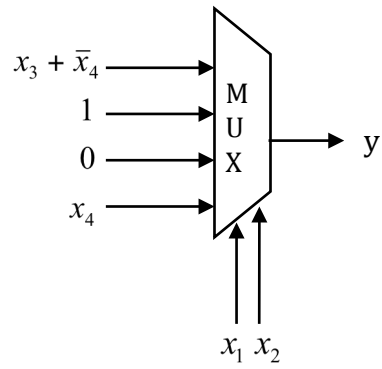Exercise 7 (2+2+2 points): Consider the following combinatorial circuit:



- Write the boolean expression associated to y and its truth table;
- Find a minimal SOP for y ;
- Turn the resulting expression in ALL-NAND form.