Computer Architecture Unit 1 – Sept. 6th, 2022

Exercise 1 (6 points) Design an automaton that takes in input binary sequences and gives in output 1 every time that the number of subsequences 01 received up to that moment equals the number of subsequence 10 received (also with overlapping), and gives 0 otherwise. Design the corresponding circuit by using FF of kind D and a ROM for the combinatorial part.

Example: IN: 01011100010 OUT: 10100011101

Exercise 2 (6 points) A control circuit receives in input the boolean values *a*, *b*, *c*, *d* and gives in output z1 e z0 such that:

- z1=1 if $a \cdot b = 1 \text{ or } \overline{b} + \overline{c} + d = 0 \text{ or } b \oplus \overline{d} = 1$
- z0=1 if $\overline{b} \cdot d = 1 \text{ or } a + \overline{c} + \overline{d} = 0 \text{ or } a \oplus c = 0$
- i. Give the truth table
- ii. Realize z1 and z0 by using a PLA
- iii. Implement z1 by a MUX 4-to-1, by using a and b as control variables.

Exercise 3 (3 points) Given values X = 3607 and Y = 6275 represented in base 10:

- turn them in base 16
- calculate Z=X+Y by working in base 16
- turn Z in base 10 and check its correctness

- turn Z in base 2

Exercise 4 (5 points) Design an interconnection between 3 source registers S1..S3 and 3 destination registers D1..D3 such that

- 1. D1 receives the content of S1, S2 or S3 according to whether, respectively, S1 is greater, smaller or equal to S2;
- 2. transfers S3 in D2, if the maximum between S2 and S3 is negative, in D3 otherwise.

All transfers are enabled if the content of D1 is multiple of 4.

Exercise 5 (4 points) Given A= -0.6875, represent it in floating point by using the IEEE half-precision standard. Calculate the sum between A and B, with B = < 1; 01111; 1100000000 >, and represent the result by using the same format. Finally, turn in hexadecimal the binary number obtained by the 16 bits of the IEEE half-precision representation of the result.

Exercise 6 (6 points) Consider the following Boolean expression:

 $(a\bar{c}\oplus\bar{b})(\overline{b+c}) + \bar{d}(a+b)(a\oplus c) + (\overline{a+\bar{c}})$

- 1. Put it in SOP normal form
- 2. Provide its truth table
- 3. Give a minimal POS expression
- 4. Provide an ALL-NOR expression