

Computer Architecture – June 7th, 2022

Exercise 1 (8 points) Design a sequential circuit with two inputs x_1 and x_0 that codify the characters A, B, C. The circuit has two outputs z_1 and z_0 such that $z_1z_0=10$ whenever it receives ABA, $z_1z_0=01$ whenever it receives ABC and $z_1z_0=00$ otherwise. Overappings are admitted. Use a PLA for the combinatorial part; use a SR FF for the most signifying bit and T FFs for the remaining bits.

Exercise 2 (5 points) Design an interconnection among registers $S_0, \dots, S_3$ and D_0, D_1 such that:

- in D_0 is moved R_i , where index i is given by the most signifying bits of D_0 and D_1
- the sum of D_0 and D_1 is moved into
 - S_0 , if both D_0 and D_1 are even,
 - S_1 , if both D_0 and D_1 are odd,
 - S_2 , if D_0 and D_1 are one even and one odd.

All movements are enabled if S_3 is not a multiple of 4.

Exercise 3 (4 points) Consider the hexadecimal number 51BB; subtract to it in base 16 the hexadecimal number A3B. Then, turn the result in a 16-bits binary number, and consider it as a rational IEEE half-precision number. Then, take $\langle 1; 10001; 1000000000 \rangle$ and multiply these two numbers in IEEE half-precision.

Exercise 4 (4 points) Given the decimal numbers $X = 94$ and $Y = 85$:

- turn them in 2-complement;
- compute $X+Y$ and $X-Y$;
- turn the results in base 10 and check their correctness.

For the 2-complement, use the minimum number of bits that make all the involved numbers representable.

Exercise 5 (3 points) Given $f = \overline{(a(a + \overline{cde}))} \oplus (\overline{b})$, turn it in POS normal form by using axioms and rules of Boolean algebra. Then, give the equivalent ALL-NOR expression.

Exercise 6 (2+1+1+2 points)

- Consider the circuit below and write the boolean expression for f
- Turn such expression in SOP normal form, by using axioms and e rules of the Boolean algebra
- Give the truth table for f
- Derive the minimal POS form of f

