

Exercises on the topics of class 14

Exercises with solutions

Ex. 1. A 4 variables BF $f(x_4, x_3, x_2, x_1)$ holds 1 if $x_4 + x_2x_1 = 0$, whereas it is not specified (don't care terms) if $x_4x_1 = 1$. Design a circuit that implements f through a PLA and a MUX.

SOLUTION:

The TT of the function is:


x_4	x_3	x_2	x_1	f
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	-
1	0	1	0	0
1	0	1	1	-
1	1	0	0	0
1	1	0	1	-
1	1	1	0	0
1	1	1	1	-

The KM is:


$x_4 x_3 \backslash x_2 x_1$	00	01	11	10
00	1	1	0	1
01	1	1	0	1
11	0	x	x	0
10	0	x	x	0

and so, the resulting minimal SOP for f is $\overline{x_2} x_1 + \overline{x_4} x_1$

From this, we can obtain the PLA:

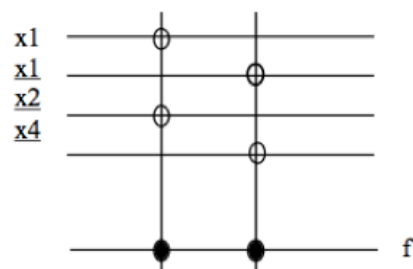

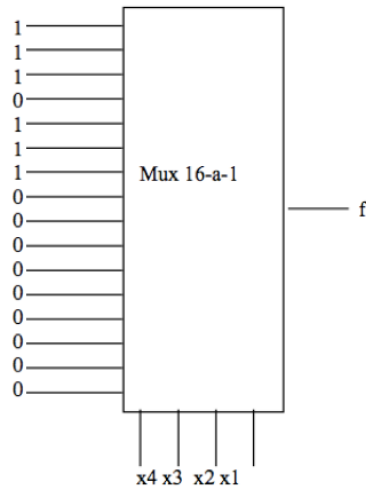For the realization with a MUX, we can choose a 16-to-1. For the don't care symbols, we can indifferently choose to put a 0 or a 1 in that entrance (in this solution, we choose 0 for all don't cares):



Ex. 2. Design a combinatorial circuit that computes function $y = x + 3$, where x is a 4-bits 2 complement integer in $[-8, 7]$ and y is codified in the same format. Put “don't care” symbols whenever y cannot be represented in the given format.


Use a PLA for the two less signifying bits of y , a ROM for all the function and a MUX 8-to-1 for the second most signifying bit.

SOLUTION:


The required function is:

X_3	X_2	X_1	X_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	-	-	-	-
0	1	1	0	-	-	-	-
0	1	1	1	-	-	-	-
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	1	1	0	1
1	0	1	1	1	1	1	0
1	1	0	0	1	1	1	1
1	1	0	1	0	0	0	0
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	0

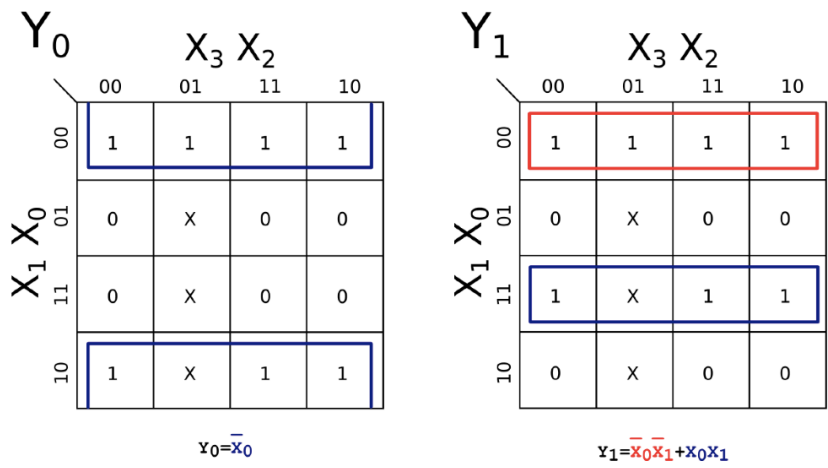
We can now compute the minimal SOP for the two less signifying bits:




and so the PLA is:

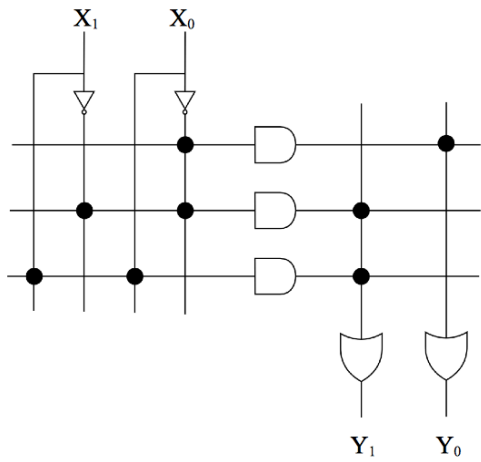

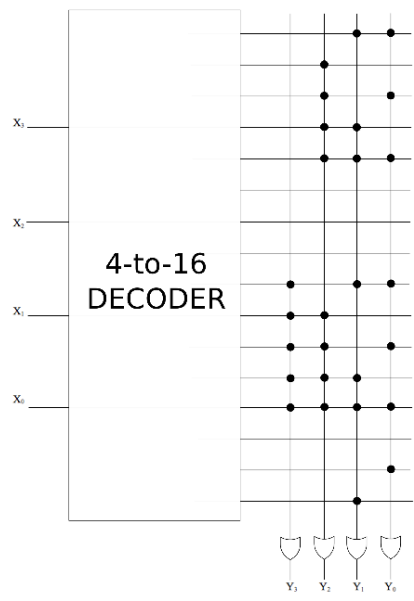The ROM is codified by looking at the TT of the function:



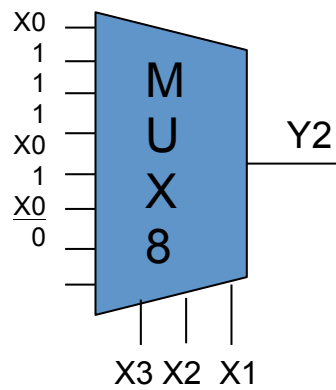For the MUX, we use as control lines X_3 , X_2 and X_1 . Don't care symbols can be freely put to 0 or 1, but in our case it turns out that all 1s is a good option. So, the resulting circuit is:



Exercises without solutions

Ex. 1. Design a PLA for the 4-variables function $f(x_3, x_2, x_1, x_0) = m_2 + m_3 + m_4 + m_9$ that is not defined (don't care) in m_0, m_1, m_6 and m_{11} .

Ex. 2. Design two 4-to-1 MUXs for the two 3-variables BFs $f(a_2, a_1, a_0) = m_0 + m_3 + m_6 + m_7$ and $g(a_2, a_1, a_0) = m_2 + m_4 + m_5 + m_6$.

Ex. 3. Consider the following BF:

x	y	z	$t1$	$t2$	$t3$	$t4$
0	0	0	0	0	0	0
0	0	1	0	1	1	0
0	1	0	1	0	0	1
0	1	1	1	1	1	0
1	0	0	1	0	0	1
1	0	1	1	1	0	0
1	1	0	1	1	0	1
1	1	1	0	0	0	1

a) Design a ROM for this BF.

b) Compute $t1$ and $t4$ through a PLA.

c) Compute $t2$ and $t3$ through a 4-to-1 MUX and a 2-to-1 MUX, respectively.