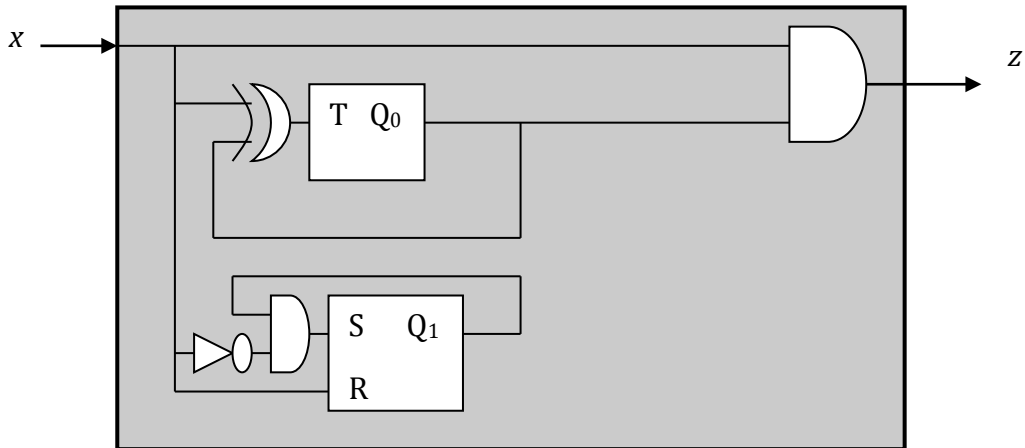


Exercises on the topic of class 20

Exercises with solutions

Ex. 1. Given the following sequential circuit:



Find the corresponding automaton, minimize it and describe its behavior at words. Assume that at the outset all FFs store 0.

SOLUTION:

The BEs are:

$$S = Q_1 \bar{x} \qquad R = x \qquad T = x \oplus Q_0 \qquad Z = x Q_0$$


And so the table of the future states is:

x	Q1	Q0	S	R	T	z (t)	Q1	Q0
(t)	(t)	(t)	(t)	(t)	(t)		(t+1)	(t+1)
0	0	0	0	0	0	0	0	0
0	0	1	0	0	1	0	0	0
0	1	0	1	0	0	0	1	0
0	1	1	1	0	1	0	1	0
1	0	0	0	1	1	0	0	1
1	0	1	0	1	0	1	0	1
1	1	0	0	1	1	0	0	1
1	1	1	0	1	0	1	0	1

From it, the automaton table (whose states are, as usual, called S0 if $Q_1Q_0 = 00$, S1 if 01, S2 if 10 and S3 if 11), with initial state S0.


	0	1
S0	S0/0	S1/0
S1	S0/0	S1/1
S2	S2/0	S1/0
S3	S2/0	S1/1

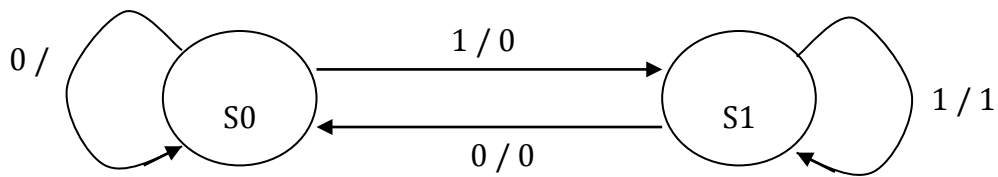Let's first observe that S2 and S3 are unreachable when the starting state is S0; it is then easy to check that the remaining automaton is minimal and can be drawn as follows:



The automaton return 1 if it reads at least two '1s' in sequence.

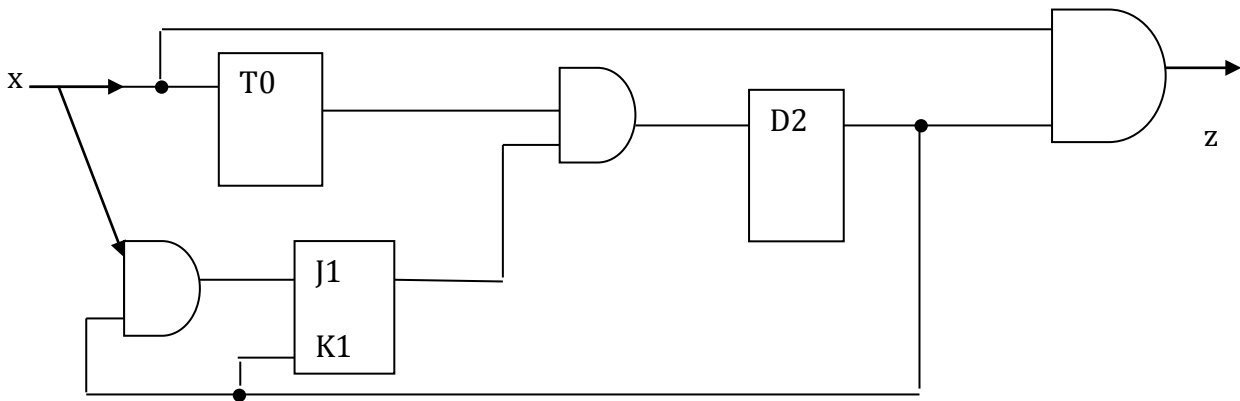Ex. 2. Analyze the following sequential circuit, by assuming that at the outset the FFs are set to $q_2 q_1 q_0 = 110$.



SOLUTION:

The BEs associated to the inputs of the FFs and to the output of the circuit are:

$$\begin{aligned}
 T0 &= x \\
 J1 &= x Q2 \\
 K1 &= Q2 \\
 D2 &= Q0 Q1 \\
 z &= x Q2
 \end{aligned}$$

From them, we can build the future states table:

<i>x</i>	<i>Q2</i>	<i>Q1</i>	<i>Q0</i>	<i>T0</i>	<i>J1</i>	<i>K1</i>	<i>D2</i>	<i>Q2'</i>	<i>Q1'</i>	<i>Q0'</i>	<i>z</i>
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	1	1	1	1	0
0	1	0	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	1	0	0	0	1	0
0	1	1	0	0	0	1	0	0	0	0	0
0	1	1	1	0	0	1	1	1	0	1	0
1	0	0	0	1	0	0	0	0	0	1	0
1	0	0	1	1	0	0	0	0	0	0	0
1	0	1	0	1	0	0	0	0	1	1	0
1	0	1	1	1	0	0	1	1	1	0	0
1	1	0	0	1	1	1	0	0	1	1	1
1	1	0	1	1	1	1	0	0	1	0	1
1	1	1	0	1	1	1	0	0	0	1	1
1	1	1	1	1	1	1	1	1	0	0	1

Since the initial configuration is the one with $Q2\ Q1\ Q0 = 110$, we obtain the following automaton (REMARK: some states are unreachable starting from 110; hence, they can be safely discarded):

	<i>0</i>	<i>1</i>
<i>110</i>	000/0	001/1
<i>000</i>	000/0	001/0
<i>001</i>	001/0	000/0


We can notice that the automaton is not minimal: we can merge 000 and 001, and obtain

	<i>0</i>	<i>1</i>
<i>S0</i>	S1/0	S1/1
<i>S1</i>	S1/0	S1/0


This circuit gives 1 upon reception of input sequences of the form 1000...0

Exercises without solutions

Ex. 1. Analyze the following sequential circuit:

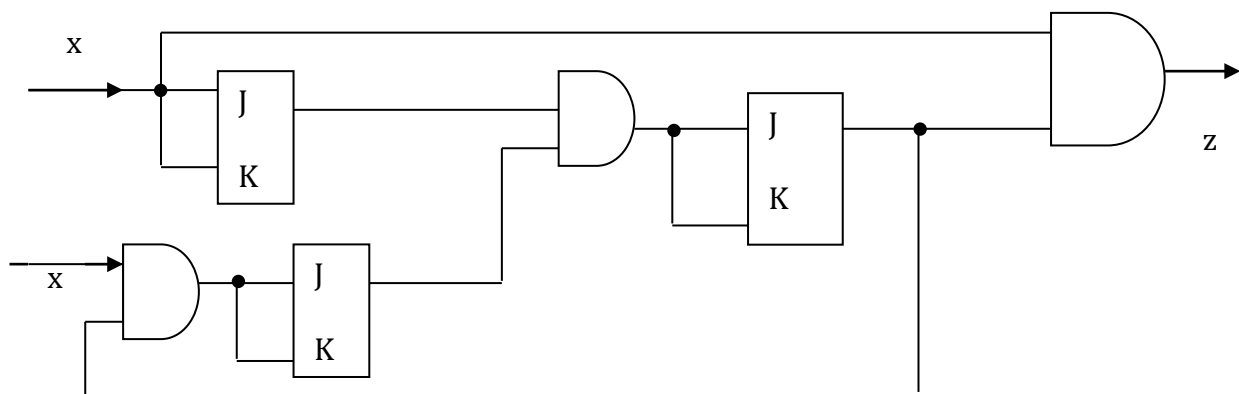

Ex. 2. Given the following circuit, analyze it by assuming that both FFs initially store 0:

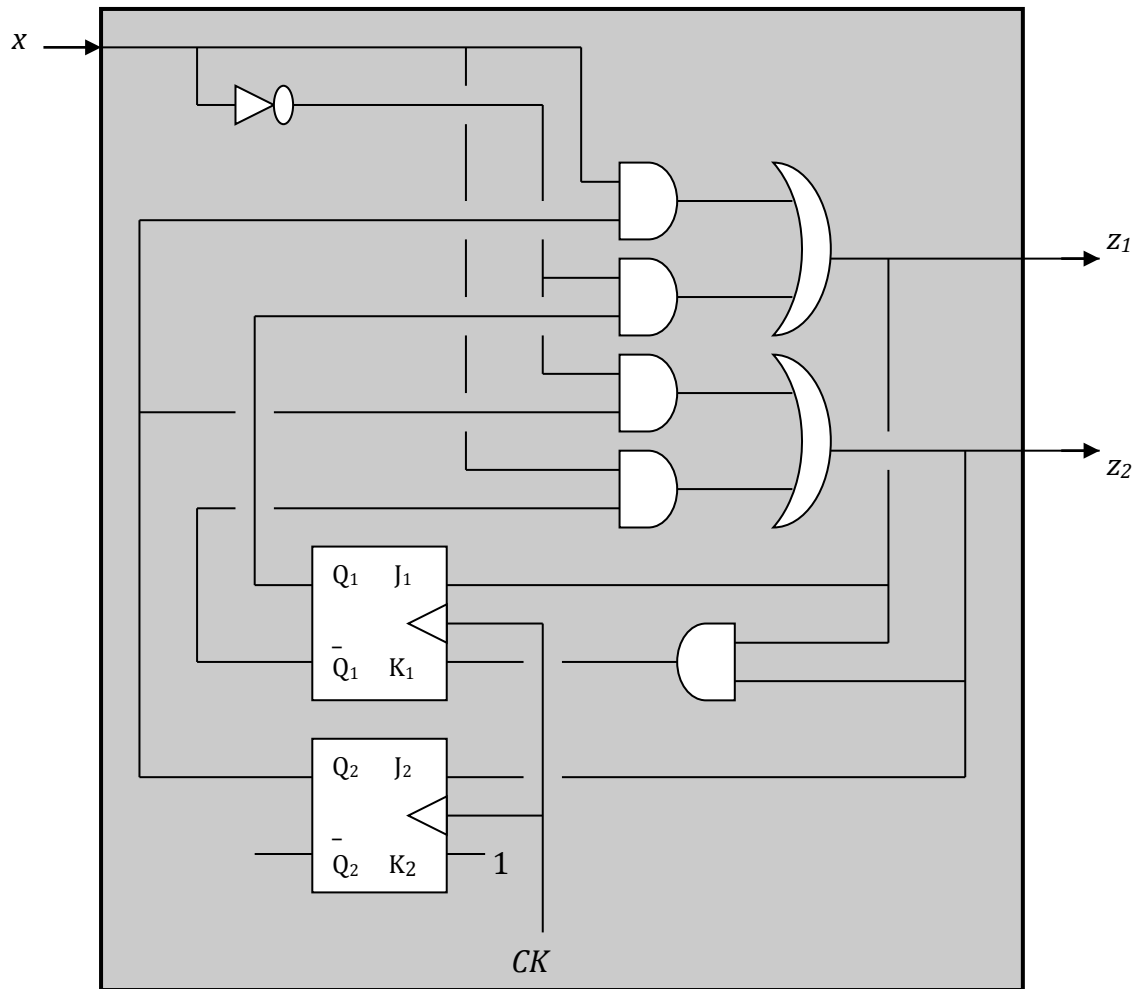

Ex. 3. Analyze the following circuit, whose FF initially stores 0:

