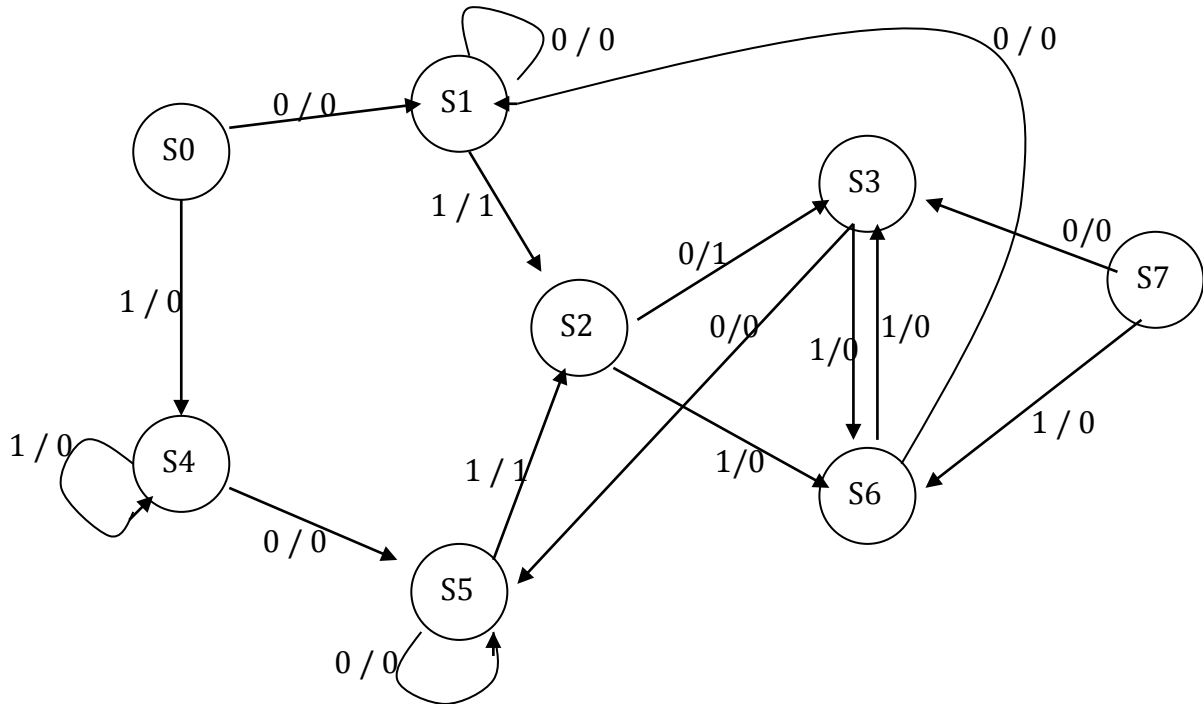


## Exercises on the topics of class 21

### Exercises with solutions

**Ex. 1.** Given the following automaton with starting state S0:



Minimize it and then, from the minimal automaton, derive the corresponding sequential net whose combinatorial part is done with a PLA and the sequential part with FFs of kind JK.

**SOLUTION:**

Notice that S7 is unreachable from S0 and so can be directly deleted. The triangular table is:

<b>S1</b>	X					
<b>S2</b>	X	X				
<b>S3</b>	1,5 4,6	X	X			
<b>S4</b>	1,5	X	X	4,6		
<b>S5</b>	X		X	X	X	
<b>S6</b>	3,4	X	X	1,5	1,5 3,4	X
	<b>S0</b>	<b>S1</b>	<b>S2</b>	<b>S3</b>	<b>S4</b>	<b>S5</b>

The resulting states are  $T_0 = \{S_0, S_3, S_4, S_6\}$ ,  $T_1 = \{S_1, S_5\}$ ,  $T_2 = \{S_2\}$ , and so the minimal automaton is:

	0	1
T0	T1 / 0	T0 / 0
T1	T1 / 0	T2 / 1
T2	T0 / 1	T0 / 0

This automaton yields the following future states table (with the encoding  $Q_1Q_0 = 00$  for T0,  $Q_1Q_0 = 01$  for T1 and  $Q_1Q_0 = 10$  for T2) :

x	Q1	Q0	Q1	Q0 (t+1)	z	J1	K1	J0	K0
0	0	0	0	1	0	0	-	1	-
0	0	1	0	1	0	0	-	-	0
0	1	0	0	0	1	-	1	0	-
0	1	1	-	-	-	-	-	-	-
1	0	0	0	0	0	0	-	0	-
1	0	1	1	0	1	1	-	-	1
1	1	0	0	0	0	-	1	0	-
1	1	1	-	-	-	-	-	-	-

With Karnaugh maps, we obtain the minimal expressions:

$$Z = \underline{x} Q_1 + x Q_0$$


$$J_1 = x Q_0$$

$$K_1 = 1$$

$$J_0 = \underline{x} Q_1$$

$$K_0 = x$$

and so the circuit is:

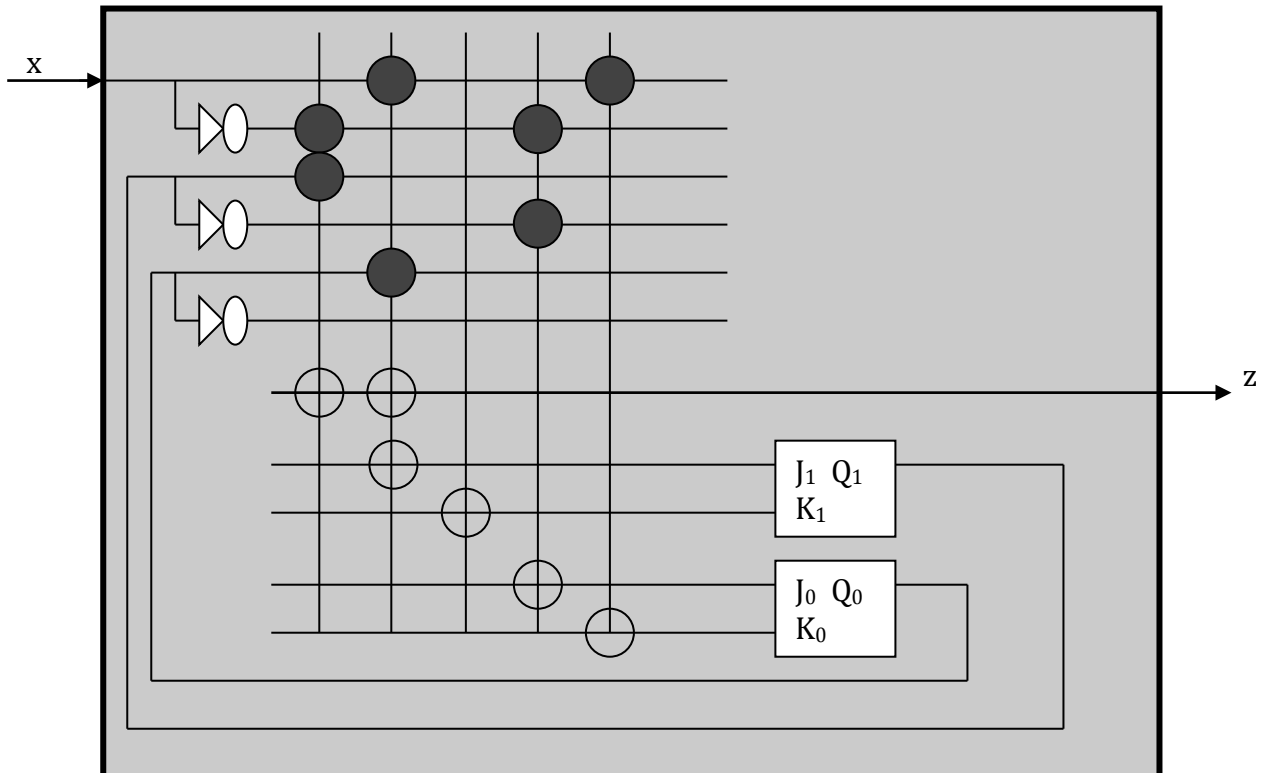

**Ex.2.** Design a circuit that receives two binary strings and gives in output 1 if and only if the sum of the values associated to the input strings received so far is a multiple of 4. Assume that the first received digit is the most significant one of the string itself stringa stessa. For example:

**Input:** 100100...


100010...

**Ouput:** 011000...

Work with the minimal automaton and with the resulting minimal expressions (obtained with gates NAND, NOR, XOR and NXOR, if possible). Use flip-flops of kind JK and don't use any module for the sum.

SOLUTION:

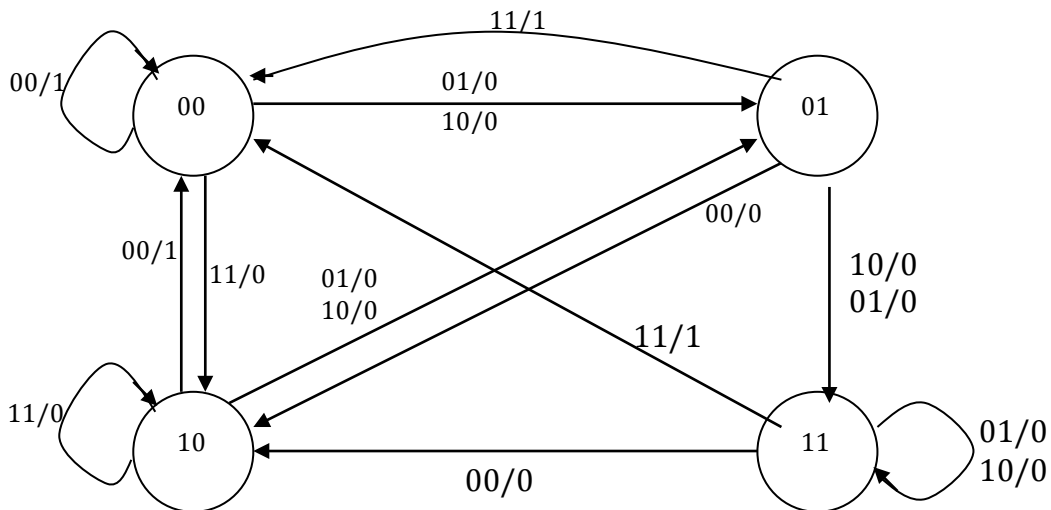States are associated to the last two bits of the binary representation of the sum of the values received so far. Hence:



Its tabular representation is

	00	01	10	11
S0	S0/1	S1/0	S1/0	S2/0
S1	S2/0	S3/0	S3/0	S0/1
S2	S0/1	S1/0	S1/0	S2/0
S3	S2/0	S3/0	S3/0	S0/1

We can easily see that it is minimizable as follows:

	00	01	10	11
T0	T0/1	T1/0	T1/0	T0/0
T1	T0/0	T1/0	T1/0	T0/1

Future states table is:

x	y	Q(t)	Q(t+1)	z	J	K
0	0	0	0	1	0	-
0	0	1	0	0	-	1
0	1	0	1	0	1	-
0	1	1	1	0	-	0
1	0	0	1	0	1	-
1	0	1	1	0	-	0
1	1	0	0	0	0	-
1	1	1	0	1	-	1

With the KMs, we have:

$$z = \underline{x}\underline{y}Q + x\underline{y}Q \quad J = \underline{x}y + x\underline{y} \quad K = xy + \underline{x}\underline{y}$$

The last two expressions can be equivalently written as

$$J = x \oplus y \quad K = x \otimes y$$

From them, we obtain the final circuit.


**Ex. 3.** Design a sequential net that, given in input a binary string, gives in output 1 if and only if the number of 1s received so far is a multiple of 3. Use flip-flops of kind T. From this, draw the net that only uses flip-flops of kind JK (REMARK: you don't have to perform another synthesis!!)

SOLUTION:

The required automaton has to check whether the number  $n$  of the 1s received so far is:

- $n = 3 \cdot k$
- $n = 3 \cdot k + 1$
- $n = 3 \cdot k + 2$

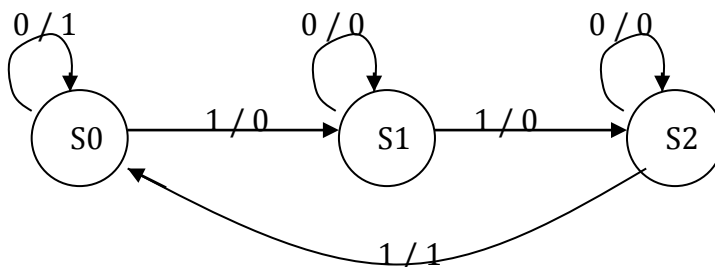for some  $k$ , and only in the first case return 1. The first condition is  $S_0$ , the second one is  $S_1$  and the third one is  $S_2$ . So, the automaton is



Let's encode  $S_0$  as  $Q_1 Q_0 = 00$ ,  $S_1$  as  $Q_1 Q_0 = 01$  and  $S_2$  as  $Q_1 Q_0 = 10$  (combination  $Q_1 Q_0 = 11$  is not used).


x	Q1 (t)	Q0 (t)	Q1 (t+1)	Q0 (t+1)	z (t)	T1 (t)	T0 (t)
0	0	0	0	0	1	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	-	-	-	-	-
1	0	0	0	1	0	0	1
1	0	1	1	0	0	1	1
1	1	0	0	0	1	1	0
1	1	1	-	-	-	-	-

By using KMs, we have that:


$$z = \bar{x} \bar{Q1} \bar{Q0} + x Q1 \quad T0 = x \bar{Q1} \quad T1 = x (Q0 + Q1)$$

REMARK: we can obtain the more compact expression  $\bar{Q0} (x \oplus Q1)$  for  $z$  by considering both don't cares as 0!

From the BEs, we draw the circuit:

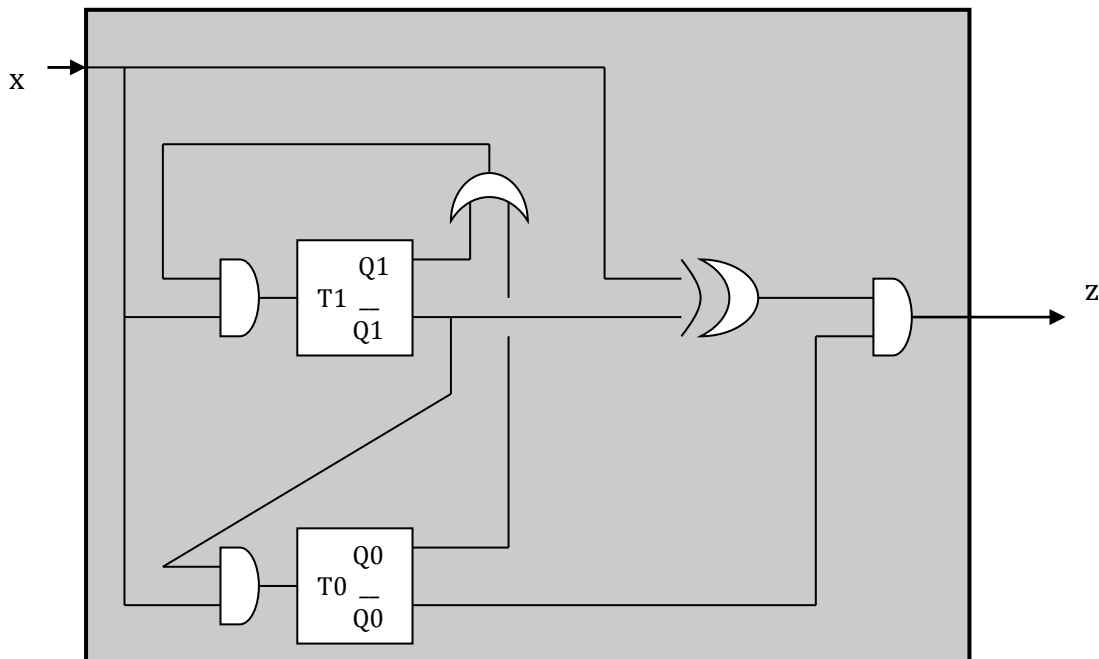

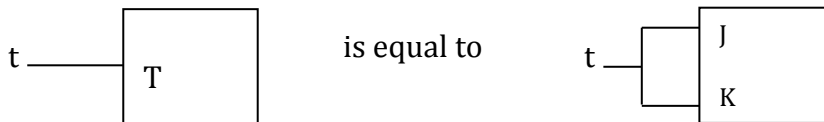To replace FFs of kind T with FFs of kind JK, it suffices to notice that



## Exercises without solutions

**Ex.1.** Design the sequential net that accepts sequences 100 and 111 by using flip-flops of kind D


- with superpositions,
- without superpositions.

**Ex. 2 (this exercise can be done AFTER studying counters).** Design the control circuit of a semaphore. It should work as follows:

- the semaphore keeps the green light on for 10 seconds;
- then, the green light is switched off and the yellow light is on for 6 seconds;
- then, the yellow light is switched off and the red one is on for 16 seconds;
- finally, the red light is switched off and start again with the green.

Assume to have a clock with frequency at 1 Herz (i.e., with one impulse every second). Use FFs of kind JK.

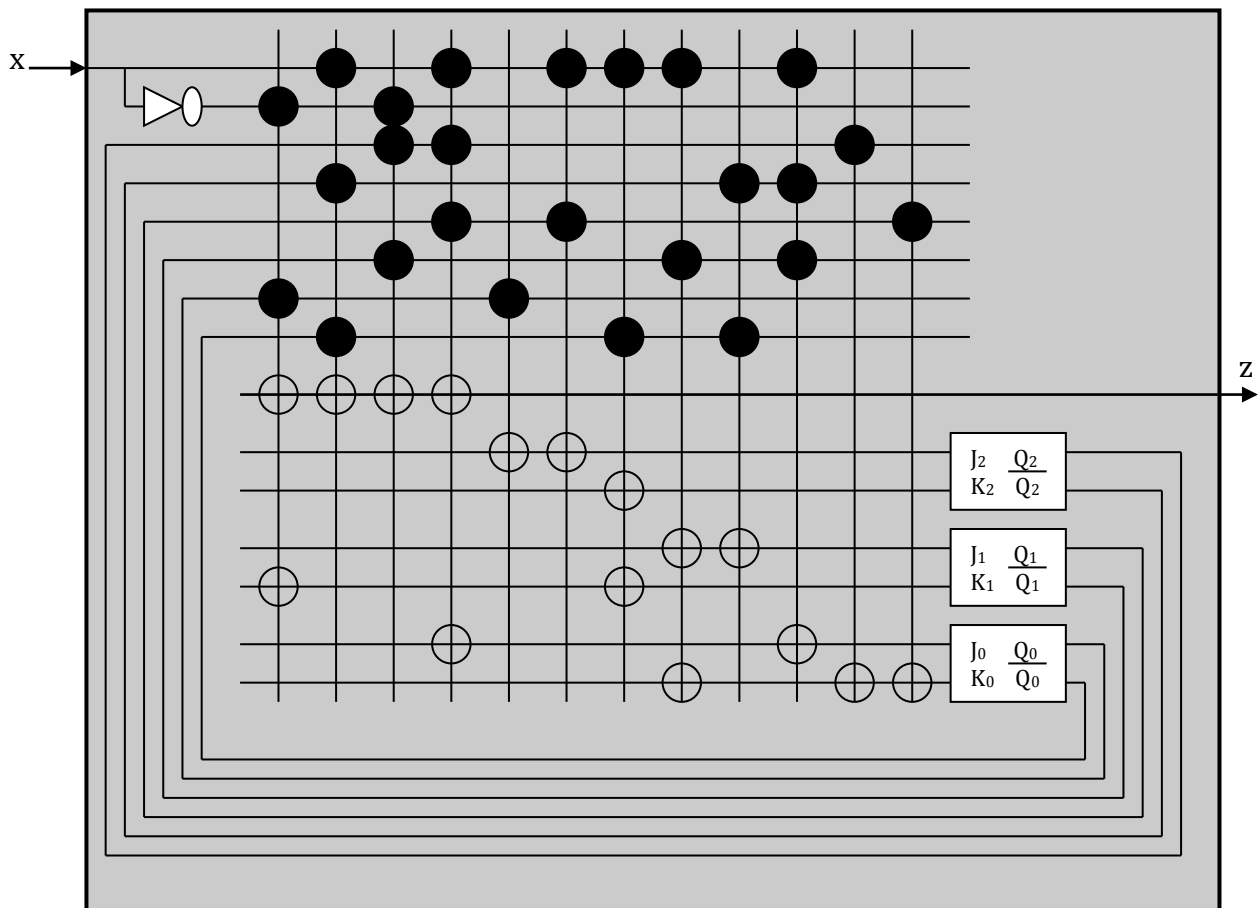**Ex. 3.** Minimize the following sequential net:



(Hint: minimize the automaton associated to the circuit – this can be obtained from an analysis procedure – and from the minimal automaton you can derive the minimal sequential net).