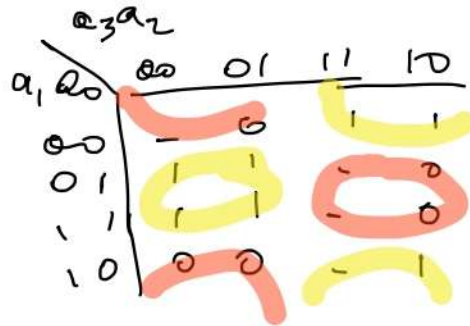


Exam of Computer Architectures – UNIT 1 - July 13th, 2021


Exercise 1 (5 points) Design a circuit that provides how many days there are in a month. The month is specified by a 4 bits input, $a_3a_2a_1a_0$. For example, with input 000 the month is January; if the input is 1100 the month is December. The circuit output Y_2 must be 1 only when the input month has 31 days; Y_1 is 1 when the month has 30 days; and Y_0 is 1 when the month has 28 days. Write the minimal SOP and POS formulae. Then, implement Y_2 with a 4-to-1 multiplexer.

$a_3 a_2 a_1 a_0$	Y_2	Y_1	Y_0
0 0 0 0	-	-	-
0 0 0 1	1	0	0
0 0 1 0	0	0	1
0 0 1 1	1	0	0
0 1 0 0	0	1	0
0 1 0 1	1	0	0
0 1 1 0	0	1	0
0 1 1 1	1	0	0
1 0 0 0	1	0	0
1 0 0 1	0	1	0
1 0 1 0	1	0	0
1 0 1 1	0	1	0
1 1 0 0	1	0	0
1 1 0 1	-	-	-
1 1 1 0	-	-	-
1 1 1 1	-	-	-




$$y_2 = \bar{a}_3 a_0 + a_3 \bar{a}_0$$

$$= (a_3 + a_0)(\bar{a}_3 + \bar{a}_0)$$

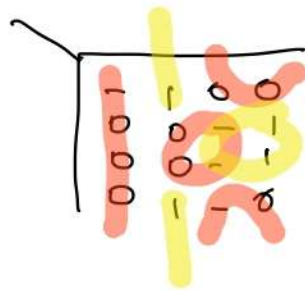


$$y_1 = \bar{a}_3 a_2 \bar{a}_0 + a_3 a_0$$
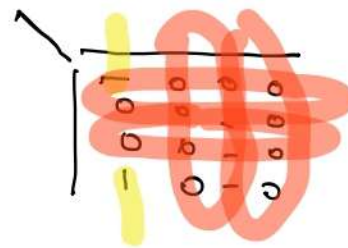
$$= (a_3 + a_2)(\bar{a}_2 + \bar{a}_0)(\bar{a}_3 + a_0)$$




$$y_0 = \bar{a}_3 \bar{a}_2 \bar{a}_0$$
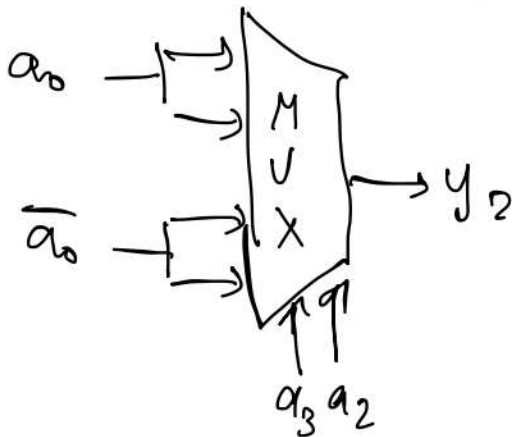
$$= a_1 \cdot \bar{a}_0 \cdot \bar{a}_2 \cdot \bar{a}_3$$



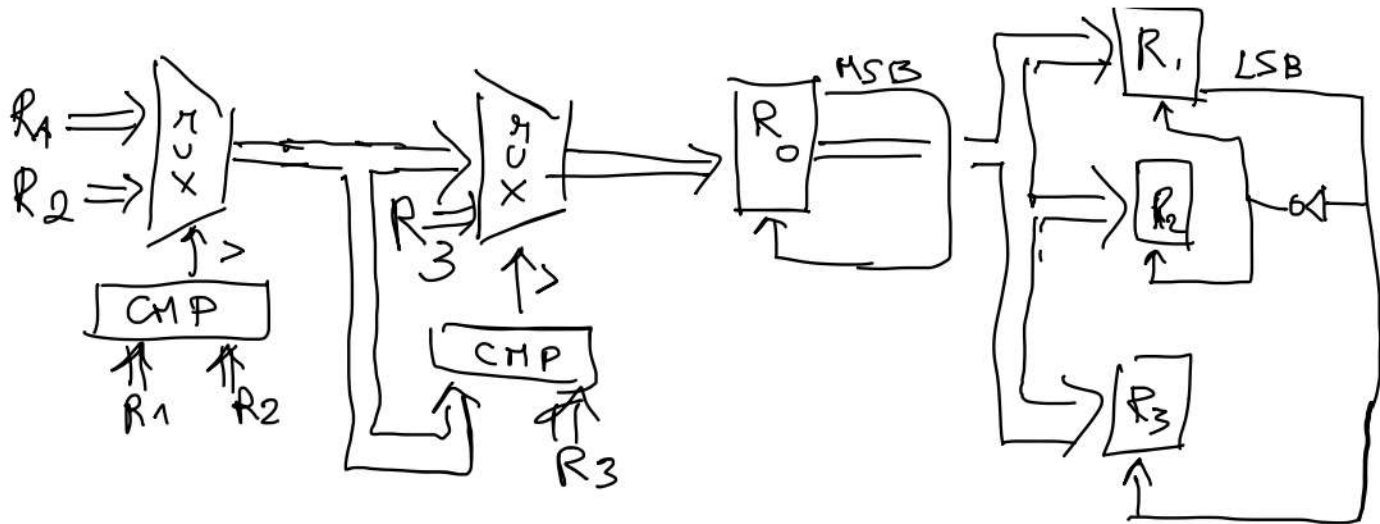Exercise 2 (5 points): Design an interconnection of 4 registers R0, ..., R3 such that:

- R0 receives the minimum value among the remaining three registers; this transfer is enabled only if R0 is positive;
- R0 is moved into R1 and R2, if R1 is even, in R3, otherwise.



Exercise 3 (4 points)

- Turn the decimal numbers $X=111$ and $Y=78$ in 2-complement with 8 bits and calculate $Z=X-Y$ and $W=X+Y$. Then, turn the results in hexadecimal.
- Sum $3EAB_{16}$ and $2E73_{16}$, turn the result in base 4 and subtract 31321_4 .

$$111 = 64 + 32 + 8 + 4 + 2 + 1 \rightarrow 01101111$$

$$78 = 64 + 8 + 4 + 2 \rightarrow 01001110 \xrightarrow{\text{Ca2}} 10110001 + 1 = 10110010$$

$$Z: \begin{array}{r} 01101111 + \\ 10110010 = \\ \hline 00100001 \\ \hline \quad 2 \quad 1 \end{array}$$

$$W: \begin{array}{r} 01101111 + \\ 01001110 = \\ \hline 10111101 \\ \hline \quad B \quad A \end{array} \leftarrow \text{overflow}$$


$$\begin{array}{r} 3EAB + \\ 2E73 = \\ \hline 6D1E \end{array}$$

$$\begin{array}{r} 6D1E \\ \wedge \wedge \wedge \wedge \\ 12310132 - \\ 31321 = \\ \hline 12212211 \end{array}$$

001 100 111


Exercise 4 (5 points): Design an automaton that receives in input x and produces in output z . The output is 1 if and only if the natural number given by the last 3 bits received so far has remainder 1 when divided by 3. You can accept overlappings. Ignore the first two outputs (that can be any value).

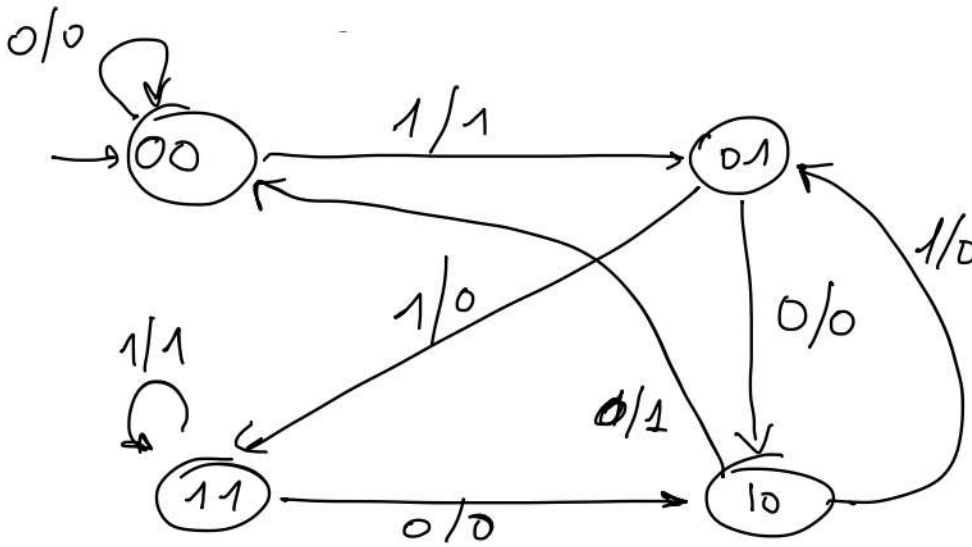Example: INPUT: 1101100011110
 OUTPUT: -- 00001010110



	0	1
00	00/0	01/1
01	10/0	11/0
10	00/1	01/0
11	10/0	11/1

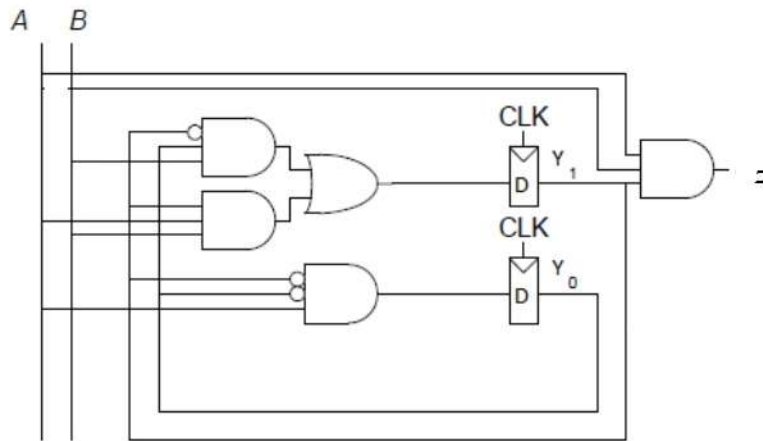Exercise 5 (4 points): Analyze the following sequential circuit and give the associated automaton.



$$D_1 = \bar{y}_1 y_0 b + y_1 a b$$

$$D_0 = \bar{y}_1 \bar{y}_0 a$$

$$z = a b y_1$$

$a b y_1 y_0$	D_1	D_0	z
0000	0	0	0
0001	0	0	0
0010	0	0	0
0011	0	0	0
0100	0	0	0
0101	1	0	0
0110	0	0	0
0111	0	0	0
1000	0	1	0
1001	0	0	0
1010	0	0	0
1011	0	0	0
1100	0	1	0
1101	1	0	0
1110	1	0	1
1111	1	0	1


	00	01	10	11
00	00 / 0	00 / 0	01 / 0	01 / 0
01	00 / 0	10 / 0	00 / 0	10 / 0
10	00 / 0	00 / 0	00 / 0	10 / 1
11	00 / 0	00 / 0	00 / 0	10 / 1

Exercise 6 (3 points) Given the expression $f = (\bar{a} + \overline{b(b + cde)}) \oplus (\bar{a} + cd)$, simplify it and write it in canonical SOP form. Then, realize f in ALL-NAND form.

$$\begin{aligned} & (\bar{a} + \overline{b(b + cde)}) \oplus (\bar{a} + cd) = (\bar{a} + \overline{b + bce}) \oplus (\bar{a} + cd) \\ & = (\bar{a} + \bar{b}) \oplus (\bar{a} + cd) = \overline{a\bar{b}} \oplus (\bar{a} + cd) = \overline{a\bar{b}(\bar{a} + cd)} + a\bar{b}(\bar{a} + cd) \\ & = (\bar{a} + \bar{b})a(\bar{c} + \bar{d}) + a\bar{b}cd = a\bar{b}(\bar{c} + \bar{d}) + a\bar{b}cd = a\bar{b}\bar{c} + a\bar{b}\bar{d} + a\bar{b}cd \\ & = \underline{a\bar{b}\bar{c}\bar{d}} + a\bar{b}\bar{c}d + \underline{a\bar{b}c\bar{d}} + a\bar{b}cd = \underline{a\bar{b}\bar{c}\bar{d}} + a\bar{b}\bar{c}d + \underline{a\bar{b}c\bar{d}} + a\bar{b}cd \end{aligned}$$

$$\begin{aligned} \text{NAND: } a\bar{b}\bar{c} + a\bar{b}\bar{d} + a\bar{b}cd &= \overline{\overline{a\bar{b}\bar{c}}} \cdot \overline{\overline{a\bar{b}\bar{d}}} \cdot \overline{\overline{a\bar{b}cd}} \\ &= \overline{a \cdot \bar{b} \cdot \bar{c} \cdot \bar{c}} \cdot \overline{a \cdot \bar{b} \cdot \bar{b} \cdot \bar{d} \cdot \bar{d}} \cdot \overline{a \cdot \bar{b} \cdot c \cdot d} \end{aligned}$$

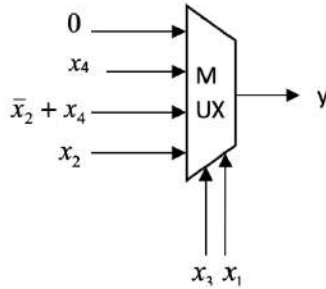Exercise 7 (4 points) Consider the following combinatorial circuit:



$$\begin{aligned} y &= \bar{x}_3 \bar{x}_1 \cdot 0 + \bar{x}_3 x_1 \cdot x_4 + x_3 \bar{x}_1 (\bar{x}_2 + x_4) + x_3 x_1 x_2 \\ &= \bar{x}_4 \bar{x}_3 x_1 + x_3 \bar{x}_2 \bar{x}_1 + x_4 x_3 \bar{x}_1 + x_3 x_2 x_1 \\ &\quad \swarrow \quad \quad \quad \searrow \quad \quad \quad \swarrow \quad \quad \quad \searrow \\ &\quad \quad \quad \bar{x}_4 (x_3 \oplus x_1) \quad \quad \quad x_3 (x_2 \otimes x_1) \end{aligned}$$