

# Exam of Computer Architectures – UNIT 1 - September 7th, 2021

Surname \_\_\_\_\_ Name \_\_\_\_\_ Matr.Numb. \_\_\_\_\_

**Exercise 1 (3 points):** Turn into base 5, by showing all steps, the following number in base 10: 120,15.

$\begin{array}{r l} 120 & 5 \\ 24 & 0 \\ 4 & 4 \\ 0 & 4 \end{array}$	$\begin{aligned} 0,15 \times 5 &= 0,75 \\ 0,75 \times 5 &= 3,75 \\ 0,75 \times 5 &= 3,75 \\ &\vdots \end{aligned}$	$\Rightarrow$	$440,0\overline{3}$
--	--	---------------	---------------------

**Exercise 2 (3 points):** Sum the following numbers in IEEE half-precision format:

$\langle 0; 01010; 1110000000 \rangle$  and  $\langle 1; 10000; 1100000000 \rangle$


↓

$\langle 0; 00000; 000001110 \rangle$

$$\begin{array}{r} 1, \overset{0}{\cancel{1}} \overset{1}{\cancel{0}} \overset{1}{\cancel{0}} \overset{1}{\cancel{0}} \overset{1}{\cancel{0}} \overset{1}{\cancel{0}} \overset{1}{\cancel{0}} \overset{2}{\cancel{0}} \overset{0}{\cancel{0}} - \\ 0, 000001110 = \\ \hline 1, 1011100010 \end{array}$$

$\langle 1; 10000; 1011100010 \rangle$

 **Exercise 3 (2 points):** Draw the circuit schema of a downwards synchronous counter modulo 32.



#### Exercise 4 (2+2+2+1 points):

a) Write the truth table of the function that, taken a 3 bits integer (in 2-complement), returns its double represented as a 4 bits integer (in 2-complement). Assume that 100 will never be received.

$x_2$	$x_1$	$x_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	0	1	1	0
1	0	0	-	-	-	-
1	0	1	1	0	1	0
1	1	0	1	1	0	0
1	1	1	1	1	1	0

b) Implement the most signifying bit of the obtained function with a MUX 2-to-1:




c) Write the minimal POS formulae associated to the two less signifying bits of the function:

$$\text{minPOS}(y_0) = 0$$




$$\text{minPOS}(y_1) = x_0$$

 d) Implement the whole function with a ROM:



**Exercise 5 (6 points):** Consider the following automaton:

	0	1
S0	S1/0	S0/0
S1	S2/0	S3/1
S2	S2/0	S3/1
S3	S1/0	S0/1
S4	S1/0	S5/0
S5	S2/0	S4/0

 

Minimize it and write down the associated sequential net that uses a JK FF for the most signifying bit and a T FF for the less signifying one.

MIN; AUT. :  $S_0 \equiv S_4 \neq S_5$   
 $S_1 \equiv S_2$

$S_{0,4,5} \Rightarrow Q_0 \rightarrow 00$   
 $S_{1,2} \Rightarrow Q_1 \rightarrow 01$   
 $S_3 \Rightarrow Q_2 \rightarrow 10$

	0	1
$Q_0$	$Q_1/0$	$Q_0/0$
$Q_1$	$Q_1/0$	$Q_2/1$
$Q_2$	$Q_1/0$	$Q_0/1$

$x y_1 y_0$	$y_1 y_0$	$z$	$J_1$	$K_1$	$T_0$
0 0 0	0 1	0	0	-	1
0 0 1	0 1	0	0	-	0
0 1 0	0 1	0	-	1	1
0 1 1	- -	-	-	-	-
1 0 0	0 0	0	0	-	0
1 0 1	1 0	1	1	-	1
1 1 0	0 0	1	-	1	0
1 1 1	- -	-	-	-	-

$x y_1$	$y_0$	00	01	11	10
0	0	0	0	1	0
1	0	0	-	1	1

$$Z = x y_1 + x y_0$$

$$= x (y_1 + y_0)$$

$x y_1$	$y_0$	00	01	11	10
0	0	1	1	0	0
1	0	0	-	1	1

$$T_0 = \bar{x} \bar{y}_2 + x y_2$$

$$= x \otimes y_2$$

$x y_1$	$y_0$	00	01	11	10
0	0	0	-	-	0
1	0	0	-	1	1

$$J_1 = x y_0$$

$x y_1$	$y_0$	00	01	11	10
0	0	-	1	1	-
1	0	-	-	-	-

$$K_1 = 1$$

**Exercise 6 (4 points):** Design an automaton that receives in input two bit sequences and gives in output 1 whenever the last three bits of the first sequence followed by the last two bits of the second sequence represent a natural number in base 2 that is a multiple of 8. The first two outputs are ignored, hence you can handle them in the way that makes the automaton simpler.

I have to store the last bit of the 1st seq. and the last two bits of the 2nd seq. (to be mult. of 8 the last 3 bits must be 000) output 1

	00	01	10	11
00	000	001	100	101
01	010	011	110	111
10	100	101	100	101
11	110	111	110	111

**Exercise 7 (5 points):** We have four source registers  $S_0, S_1, S_2$  and  $S_3$  and two destination registers  $D_0$  and  $D_1$ . Implement an interconnection such that:

- The index of the source register to be moved into  $D_0$  is given by calculating  $(S_0 + 2) \bmod 4$ ;
- $D_1$  receives the content of  $S_1$ , if  $S_0$  is greater than or equal to  $S_2$ ;  $S_3$  otherwise.

In both cases, transfers are enabled only if  $S_3$  is even.

