

Verilog

Harris & Harris, Digital Design and Computer Architecture


Ch. 4 - Hardware Description Languages

- 4.2.10 Delays
- 4.4 SEQUENTIAL LOGIC
- 4.5 MORE COMBINATIONAL LOGIC

Delays

- HDL statements may be associated with **delays**, helpful during simulation to predict how fast a circuit will work and for debugging purposes (but ignored during synthesis)
- Let's consider a previous example and its simulation waveforms

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a & ~b & c;  
endmodule
```

 

Delays

- We now add delays to the previous function
- We assume:
 - **inverters** have a delay of **1 ns**,
 - **three-input AND gates** have a delay of **2 ns**,
 - **three-input OR gates** have a delay of **4 ns**

```
module example(input  logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} = ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```


In SystemVerilog,
a **# symbol** is
used to indicate
the number of
units of delay

Delays

```
module example(input logic a, b, c,
               output logic y);
    logic ab, bb, cb, n1, n2, n3;
    assign #1 {ab, bb, cb} = ~{a, b, c};
    assign #2 n1 = ab & bb & cb;
    assign #2 n2 = a & bb & cb;
    assign #2 n3 = a & bb & c;
    assign #4 y = n1 | n2 | n3;
endmodule
```


Let's analyze and simulate this code.

Let's analyze the simulation waveform

 

Delays

```
module example(input  logic a, b, c,  
                output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
        ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 


Note that the beginning of the simulation only the variables **a**, **b**, **c** are known.

In particular **y is initially unknown**

Delays


```
module example(input  logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
             ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

After 1 ns inverters produce their outputs

Delays


```
module example(input  logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
             ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

After 2 ns *and* gates produce their outputs


Delays

```
module example(input  logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
            ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

Delays

```
module example(input  logic a, b, c,  
               output logic y);  
    logic ab, bb, cb, n1, n2, n3;  
    assign #1 {ab, bb, cb} =  
            ~{a, b, c};  
    assign #2 n1 = ab & bb & cb;  
    assign #2 n2 = a & bb & cb;  
    assign #2 n3 = a & bb & c;  
    assign #4 y = n1 | n2 | n3;  
endmodule
```

 

Sequential Logic

- SystemVerilog uses **idioms** to describe latches, flip-flops and FSMs
- Other coding styles may simulate correctly but produce incorrect hardware

Always Statement

- The majority of modern commercial systems are built with registers using positive edge-triggered D flip-flops
- In SystemVerilog **always** statements signals keep their old value until an event in the **sensitivity list** takes place that explicitly causes them to change


```
always @(sensitivity list)  
    statement;
```

- Whenever the event in **sensitivity list** occurs, **statement** is executed
- Hence, code using **always**, with appropriate sensitivity lists, can be used to describe **sequential circuits**

D Flip-Flop

- For example, the flip-flop includes only **clk** in the sensitive list
- It remembers its old value of q until the next rising edge of the **clk**, even if d changes in the interim

 
```
module flop(input  logic clk,  
            input  logic [3:0] d,  
            output logic [3:0] q);  
  
    always_ff@(posedge clk)  
        q <= d;                // pronounced "q gets d"  
endmodule
```



D Flip-Flop

- <= is called a **nonblocking assignment**
- <= is used instead of assign inside an always statement
 
```
module flop(input  logic clk,  
            input  logic [3:0] d,  
            output logic [3:0] q);  
  
    always_ff@(posedge clk)  
        q <= d;                // pronounced "q gets d"  
endmodule
```



D Flip-Flop

- **always** statements can be used to imply **flip-flops**, **latches**, or **combinational logic**, depending on the sensitivity list and statement
- To reduce the risk of common errors, SystemVerilog introduces **always_ff**, **always_latch**, and **always_comb**
- **always_ff** behaves like **always** but is used exclusively to imply flip-flops and allows tools to produce a warning if anything else is implied

Resettable registers

- When simulation begins or power is first applied to a circuit, the output of a flop or register is **unknown**
- This is indicated with **x** in SystemVerilog
- It is good practice to use **resettable registers** so that on powerup you can put your system in a **known state**
- The reset may be either **asynchronous** or **synchronous**:
 - **asynchronous reset** occurs immediately
 - **synchronous reset** clears the output only on the next rising edge of the clock

Resettable D Flip-Flop

```
module flopr(input  logic clk,  
             input  logic reset,  
             input  logic [3:0] d,  
             output logic [3:0] q);
```


```
    // synchronous reset
```

```
    always_ff @(posedge clk)  
        if (reset) q <= 4'b0;  
        else      q <= d;
```

```
endmodule
```


Posedge clk is alone in the sensitivity list thus:

 - **synchronously** resettable flops respond to reset **only on the rising edge of the clock**



Resettable D Flip-Flop
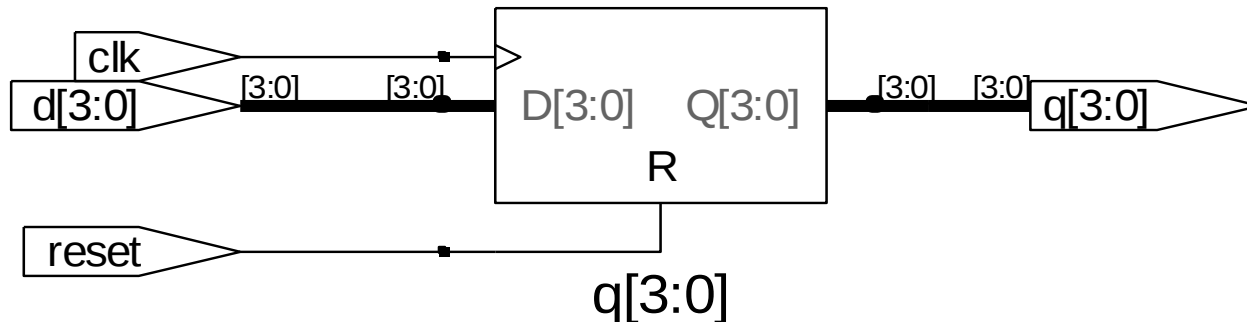
```
module flopr(input logic clk,  
             input logic reset,  
             input logic [3:0] d,  
             output logic [3:0] q);  
  
    // asynchronous reset  
    always_ff @(posedge clk, posedge reset)  
        if (reset) q <= 4'b0;  
        else      q <= d;  
  
endmodule
```



Posedge reset is in the sensitivity list only on the *asynchronously resettable flop*, thus:


- **asynchronously** resettable flops **immediately** respond to a rising edge on **reset**

D Flip-Flop with Enable

```
module flopren(input logic clk,
               input logic reset,
               input logic en,
               input logic [3:0] d,
               output logic [3:0] q);

  // enable and asynchronous reset
  always_ff @(posedge clk, posedge reset)
    if (reset) q <= 4'b0;
    else if (en) q <= d;


endmodule
```

 

- **Enabled registers** respond to the clock **only** when the **enable is asserted**
- Asynchronously resettable enabled registers retain their old value if **both reset and en are FALSE**

Latch
 
```
module latch(input  logic clk,  
             input  logic [3:0] d,  
             output logic [3:0] q);  
  
    always_latch  
        if (clk) q <= d;  
  
endmodule
```



`always_latch` is equivalent to
`always@ (clk, d):`
if `clk` is **HIGH**, `d` flows through to `q` (positive level sensitive)
otherwise, `q` keeps its old value

It is the preferred idiom for describing a SystemVerilog latch: a warning is generated if the `always_latch` block is not a latch

More combinational logic

- SystemVerilog **always** statements are used to describe sequential circuits, because they remember the old state when no new state is prescribed
- We used assignment statements to describe combinational logic behaviorally
- **always** statements can also be used to describe combinational logic behaviorally, but:
 - the **sensitivity list** MUST respond **to changes in all of the inputs**
 - all **outputs** should have **default values** or must be **assigned for every input combination**, otherwise a latch will be generated to hold the current value

Blocking vs. Nonblocking Assignment

- SystemVerilog supports **blocking** and **nonblocking** assignments in an always statement
- = is **blocking** assignment:
 - A group of **blocking** assignments are **evaluated in the order** in which they appear in the code, just as one would expect in a standard programming language
- <= is **nonblocking** assignment:
 - A group of **nonblocking** assignments are evaluated **concurrently**
 - all of the statements are evaluated before any of the signals on the left hand sides are updated

Blocking vs. Nonblocking Assignment

```
module inv(input  logic [3:0] a,  
           output logic [3:0] y);  
    always_comb  
        y = ~a;  
endmodule
```

- **always_comb** reevaluates the statements inside the **always** statement any time any of the signals on the right hand side of **<=** or **=** in the **always** statement change
- In this case, it is equivalent to **always @(a)**, but is better because it avoids mistakes if signals in the always statement are renamed or added
- If the code inside the always block is not combinational logic, SystemVerilog will report a warning

Blocking vs. Nonblocking Assignment

```
module fulladder(input  logic a, b, cin,
                  output logic s, cout);

    logic p, g;
    always_comb
    begin
        p = a ^ b;           // blocking
        g = a & b;           // blocking
        s = p ^ cin;         // blocking
        cout = g | (p & cin); // blocking
    end
endmodule
```

- In this case, `always@ (a,b,cin)` would have been equivalent to `always_comb` but `always_comb` is better because it avoids missing signals in the sensitivity list
- this example uses **blocking assignments**, first computing `p`, then `g`, then `s`, and finally `cout`, that are better for combinational logic

Other Behavioral Statements

- **case** and **if** statements are convenient for modeling more complicated combinational logic
- **case** and **if** statements MUST appear within **always** statements
- **case** statement
 - performs different actions depending on the value of its input
 - implies **combinational** logic **only if** all possible input combinations described
 - need to use **default** statement, **otherwise** it implies **sequential** logic, because the output will keep its old value in the undefined cases

Combinational Logic using case

```
module sevenseg(input  logic [3:0] data,
                output logic [6:0] segments);

    always_comb
        case (data)
            //                abc_defg
            0: segments =      7'b111_1110;
            1: segments =      7'b011_0000;
            2: segments =      7'b110_1101;
            3: segments =      7'b111_1001;
            4: segments =      7'b011_0011;
            5: segments =      7'b101_1011;
            6: segments =      7'b101_1111;
            7: segments =      7'b111_0000;
            8: segments =      7'b111_1111;
            9: segments =      7'b111_0011;
            default: segments = 7'b000_0000; //required
        endcase
    endmodule
```

- The **case** statement checks the value of data and performs the action after the colon
- The **default** clause is used to define the output for all cases not explicitly listed, guaranteeing combinational logic

Other Behavioral Statements

- **always** statements may also contain **if** statements
- The if statement may be followed by an **else** statement
- If **all possible input** combinations are handled, the statement implies **combinational** logic; **otherwise**, it produces **sequential** logic

```
module priorityckt(input  logic [3:0] a,  
                   output logic [3:0] y);  
    always_comb  
        if (a[3]) y = 4'b1000;  
        else if (a[2]) y = 4'b0100;  
        else if (a[1]) y = 4'b0010;  
        else if (a[0]) y = 4'b0001;  
        else y = 4'b0000;  
endmodule
```

priority circuit:
N-input priority circuit sets the output bit TRUE that corresponds to the most significant input that is TRUE

Combinational Logic using casez

- Truth tables may include **don't care**'s to allow simplification
- A priority circuit can be defined using don't cares
- The **casez** statement acts like a case statement but it also **recognizes ? as don't care**

```
module priority_casez(input  logic [3:0] a,  
                     output logic [3:0] y);
```

```
  always_comb
```

```
    casez (a)
```

```
      4'b1???: y = 4'b1000; // ?=don't care
```

```
      4'b01?: y = 4'b0100;
```

```
      4'b001?: y = 4'b0010;
```

```
      4'b0001: y = 4'b0001;
```

```
      default: y = 4'b0000;
```

```
    endcase
```

```
endmodule
```

